

Chapter V-2 - Loudspeakers

H. Lissek

Fall 2024

Exercise 1. Measurement of loudspeaker small-signal parameters (Thiele-Small)


a. Loudspeaker on a screen

$$Z_{hp} = R_e + \frac{(B\ell)^2}{j\omega M_{ms} + R_{ms} + \frac{1}{j\omega C_{ms}}}$$

— Equivalent acoustic scheme :

We introduce the acoustic equivalent R_{ae} of the dc electric resistance R_e $R_{ae} = \frac{(B\ell)^2}{S_d^2 R_e}$, and the acoustic equivalent (R_{as}, M_{as}, C_{as}) of the mechanical components (R_{ms}, M_{ms}, C_{ms}) :

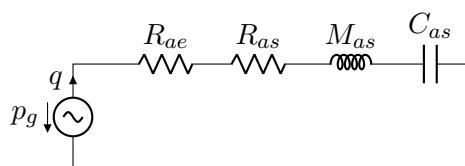
$$R_{as} = \frac{R_{ms}}{S_d^2}, \quad M_{as} = \frac{M_{ms}}{S_d^2} \quad \text{and} \quad C_{as} = C_{ms} S_d^2.$$



Equivalent electric scheme :

We also introduce the electrical equivalent (R_s, C_s, L_s) of the mechanical components (R_{ms}, M_{ms}, C_{ms}) :
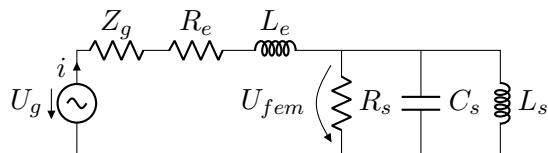
$$R_s = \frac{(B\ell)^2}{R_{ms}}, \quad C_s = \frac{M_{ms}}{(B\ell)^2} \quad \text{and} \quad L_s = C_{ms} (B\ell)^2$$



— If we introduce the equivalent electric impedance $R_s = \frac{(B\ell)^2}{R_{ms}}$:

$$Z_{hp} = R_e + \frac{R_s}{Q_{ms}} \frac{\left(\frac{j\omega}{\omega_s}\right)}{\left(\frac{j\omega}{\omega_s}\right)^2 + \frac{1}{Q_{ms}} \left(\frac{j\omega}{\omega_s}\right) + 1}$$

- $R_e = 5.6\Omega$
- $\widehat{Z}_{hp}(f_s) = R_e + R_s = R_e + \frac{(B\ell)^2}{R_{ms}}$. We miss one other equation to retried $B\ell$ and R_{ms} .

- We chose to find the roots of the following equation $|Z_{hp}(f_{1,2})| = r_1 R_e = \sqrt{1 + \frac{R_s}{R_e}} R_e$ which yields :

$$|Z_{hp}(f_{1,2})|^2 = R_e^2 \left(1 + \frac{R_s}{R_e}\right) \text{ then} \\ \left(\frac{f_{1,2}}{f_s}\right)^4 - \left(2 + \frac{1}{Q_{ms}^2}(1 + \frac{R_s}{R_e})\right) \left(\frac{f_{1,2}}{f_s}\right)^2 + 1 = 0$$

It yields :

$$\left(\frac{f_{1,2}}{f_s}\right)^2 = \frac{1}{2} \left[\left(2 + \frac{1}{Q_{ms}^2}(1 + \frac{R_s}{R_e})\right) \pm \sqrt{\left(2 + \frac{1}{Q_{ms}^2}(1 + \frac{R_s}{R_e})\right)^2 - 4} \right]$$

then :

$$f_1^2 f_2^2 = \frac{1}{4} f_s^4 \left[\left(2 + \frac{1}{Q_{ms}^2}(1 + \frac{R_s}{R_e})\right)^2 - \left(\left(2 + \frac{1}{Q_{ms}^2}(1 + \frac{R_s}{R_e})\right)^2 - 4\right) \right]$$

and finally, after simplifications : $f_1 f_2 = f_s^2$

- $f_s = \sqrt{f_1 f_2} = 40.4 \text{ Hz.}$

- We can notice that $\left(\frac{f_2 - f_1}{f_s}\right)^2 = \left(\frac{f_2}{f_s}\right)^2 + \left(\frac{f_1}{f_s}\right)^2 - 2 \frac{f_1 f_2}{f_s^2} = \left(\frac{f_2}{f_s}\right)^2 + \left(\frac{f_2}{f_s}\right)^2 - 2$

$$\text{Since } \left(\frac{f_2}{f_s}\right)^2 + \left(\frac{f_2}{f_s}\right)^2 = 2 + \frac{1}{Q_{ms}^2}(1 + \frac{R_s}{R_e}) = 2 + \frac{1}{Q_{ms}^2} r_0$$

$$\text{with } r_0 = 1 + \frac{R_s}{R_e}$$

$$\text{Then } Q_{ms}^2 \left(\frac{f_2 - f_1}{f_s}\right)^2 = r_0 \text{ and finally } Q_{ms} = \frac{f_s}{f_2 - f_1} \sqrt{r_0}$$

- $Q_{es} = Q_{ms} \frac{R_e}{R_s} = \frac{Q_{ms}}{r_0 - 1}$

- $r_0 = 65/5.6 = 11.6 \rightarrow Q_{ms} = 4.12, Q_{es} = 0.38 \text{ and } Q_{ts} = 0.35$

b. Loudspeaker with an additional mass

The measurement gives the two new frequencies $f'_1 = 22 \text{ Hz}$ and $f'_2 = 40.7 \text{ Hz}$.

- $f'_s = \sqrt{f'_1 f'_2} \approx 29.9 \text{ Hz}$

- We remind that without the mass, $f_s = \frac{1}{2\pi\sqrt{C_{ms}M_{ms}}}$

With the added mass, the resonance frequency becomes : $f'_s = \frac{1}{2\pi\sqrt{C_{ms}(M_{ms} + M_{add})}}$

By processing $\frac{f_s}{f'_s} = \sqrt{\frac{M_{ms} + M_{add}}{M_{ms}}}$ we obtain $\frac{f_s^2}{f'^2_s} = 1 + \frac{M_{add}}{M_{ms}}$

- Thanks to the last relationship, we deduce $M_{ms} = \frac{M_{add}}{\frac{f_s^2}{f_s'^2} - 1} \approx 11g$

$$C_{ms} = \frac{1}{4\pi^2 f_s^2 M_{ms}} \approx 1.4 \text{ mm.N}^{-1}$$

- $Q_{ms} = \frac{1}{\omega_s R_{ms} C_{ms}} \rightarrow R_{ms} = \frac{1}{\omega_s Q_{ms} C_{ms}} = 0.67 \text{ N.m}^{-1} \cdot \text{s}$
 $R_s = \frac{(B\ell)^2}{R_{ms}} \rightarrow B\ell = \sqrt{R_{ms} R_s} = 6.9 \text{ T.m}$, where $R_s = 65 - 5.6 = 59.4 \Omega$

- c. Loudspeaker with a closed-box cabinet We now remove the masse M_{add} and close the rear face of the loudspeaker with a sealed cabinet of volume $V_b = 20 \text{ L}$. We do once again the same measurement, which gives :

We introduce the compliance factor $\alpha = \frac{C_{as}}{C_{ab}}$, where $C_{ab} = \frac{V_b}{\rho c^2}$

- The new acoustic compliance of the closed-box loudspeaker is $C_{ac} = \frac{C_{ab} C_{as}}{C_{ab} + C_{as}}$, where $C_{as} = C_{ms} S_d^2$ and then

$f_c = \frac{1}{2\pi\sqrt{M_{ac} C_{ac}}} \approx \frac{1}{2\pi\sqrt{M_{as} C_{ac}}}$ if we consider the radiation acoustic mass in the cabinet M_{ab} is the same as the screen-mounted radiation acoustic mass M_{ar} .

We can also notice that $C_{ac} = \frac{C_{as}}{1 + \alpha}$, then $f_c = \sqrt{1 + \alpha} f_s$

- $Q_{ec} = \frac{1}{2\pi f_c C_{ac} R_{ae}}$, if we introduce $R_{ae} = \frac{(B\ell)^2}{S_d^2 R_e}$ the acoustical equivalent of the dc electrical resistance R_e .

Then, since $Q_{es} = \frac{1}{2\pi f_s C_{as} R_{ae}}$ and $C_{ac} = \frac{C_{as}}{1 + \alpha}$, we deduce $Q_{ec} = \sqrt{1 + \alpha} Q_{es}$

- After the 2 preceding expressions, we deduce $Q_{ec} f_c = (1 + \alpha) Q_{es} f_s$, then $\alpha = \frac{Q_{ec} f_c}{Q_{es} f_s} - 1$

If we repeat the same procedure as in the 2 preceding questions, we first observe the values f_{1c} and f_{2c} of f for which $Z_{hp} = \sqrt{r_0 R_e}$: $f_{1c} = 46.74 \text{ Hz}$ and $f_{2c} = 76.89 \text{ Hz}$ yields

$f_c = 59.95 \text{ Hz}$ and $Q_{ec} = 0.639$ (once again here, $r_0 = 65/5.6 = 11.6$).

Then $\alpha = 1.4413$, then $V_{as} = \alpha V_b = 28.8 \text{ L}$

- We can also deduce $S_d : C_{ms} = \frac{V_{as}}{\rho c^2 S_d^2} \rightarrow S_d = \sqrt{\frac{V_{as}}{\rho c^2 C_{ms}}} = 121 \text{ cm}^2$