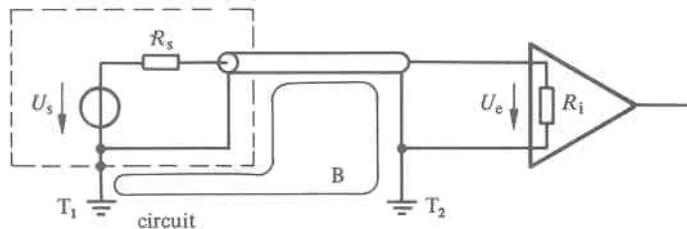


Electromagnetic Compatibility Problem Set 5


Problem 1: Common mode induced voltage

a) Determine the expression of the induced voltage at the input of the amplifier, due to a common-mode disturbing voltage U_T between the two groundings T_1 and T_2 .


Numerical application: $U_T=100 \text{ mV}$, equivalent resistance between T_1 and T_2 : $R_T=0.01 \Omega$, resistance of the internal conductor $R_c=1 \Omega$, resistance of the shield $R_b=1 \Omega$, $R_s=500 \Omega$, $R_i=10 \text{ k}\Omega$.



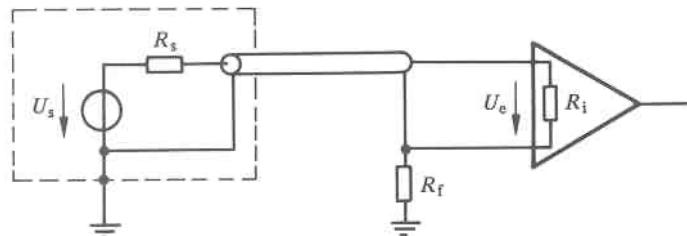b) We insert a resistor $R_f=10 \Omega$ between the amplifier and the ground (see figure). Calculate the value of the resulting voltage at the input of the amplifier.




c) Is it appropriate to use a floating source, as shown in the figure below ?

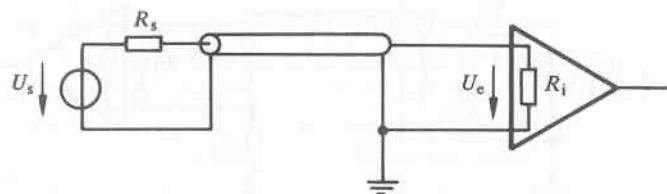

Problem 2 : Use of a Differential Amplifier


We replace the amplifier in Problem 1 with a differential (balanced) amplifier. Calculate the induced voltage at the input of the amplifier. $R_{i1}=R_{i2}=R_i/2$.

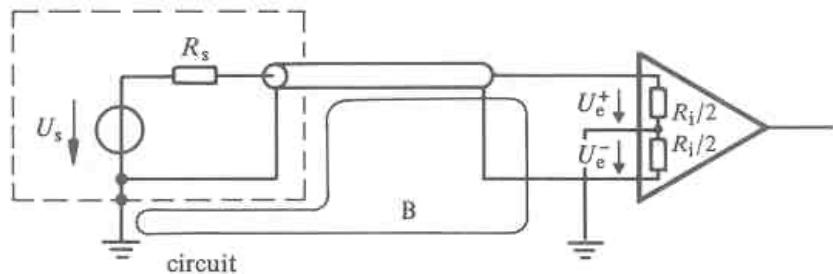

Problem 3 : Common-Mode Rejection Ratio

Consider the circuit shown below in which we have an unbalanced load resistance.


1. Calculate the expression for the Common-Mode Rejection Ratio (CMRR) as a function of source and load impedances.
2. Simplify the obtained expression for $RL \gg RS$.
3. Calculate CMRR in dB for $RS = 100 \Omega$, $RL = 10 \text{ k}\Omega$, and $\Delta RL = 100\Omega$.

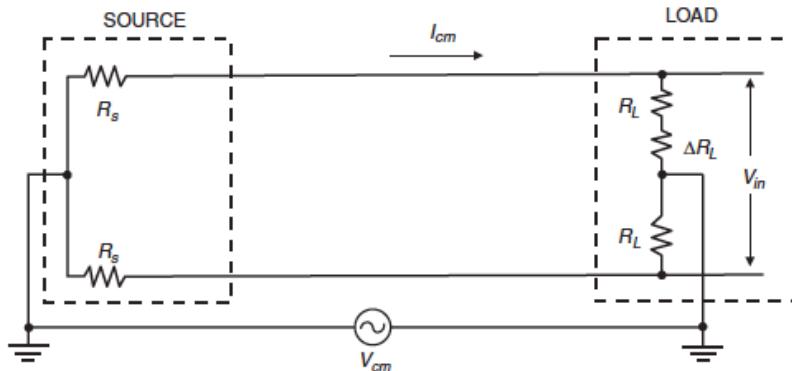

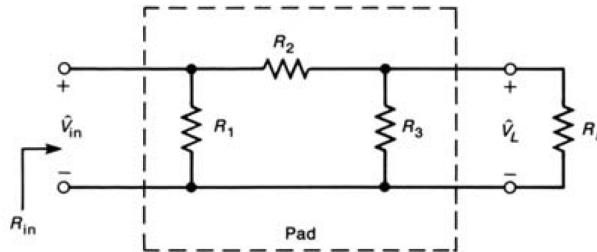
Problem 4 : Insertion Loss of a Pad

A pad is a resistive network whose input impedance remains fairly constant regardless of its termination impedance.

A typical topology of a pad is the “Pi” structure shown in the figure below. It is also possible to choose other structures such as the “tee” (T) structure. Being resistive circuits, these pads provide matching over wide frequency ranges but they also give an insertion loss.



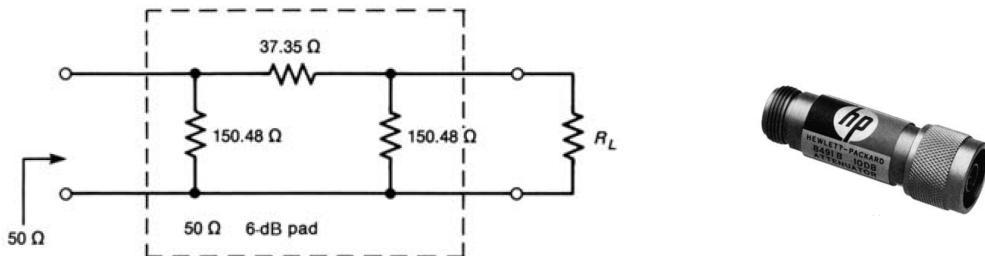The resistor values and schematic of a $50\text{-}\Omega$, 6-dB pad are shown in the figure below. A photograph of a commercially available pad is also shown.



1. Calculate the input impedance of the pad for extreme values of termination impedances: open circuit and short circuit.
2. Calculate the insertion loss of the pad for a source with an internal impedance of 50 Ohms.