
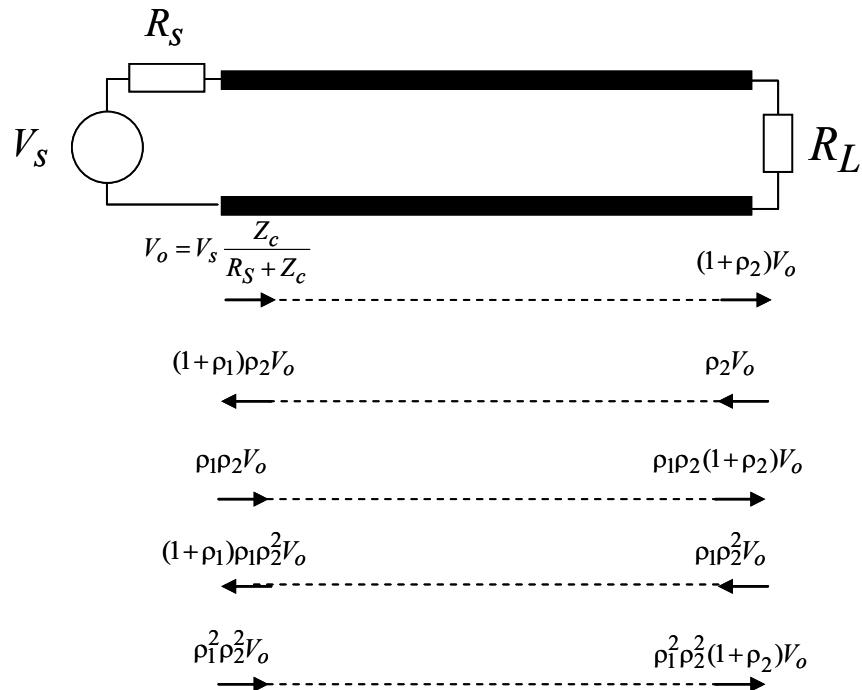


Electromagnetic Compatibility Problem Set II – Solutions


1.

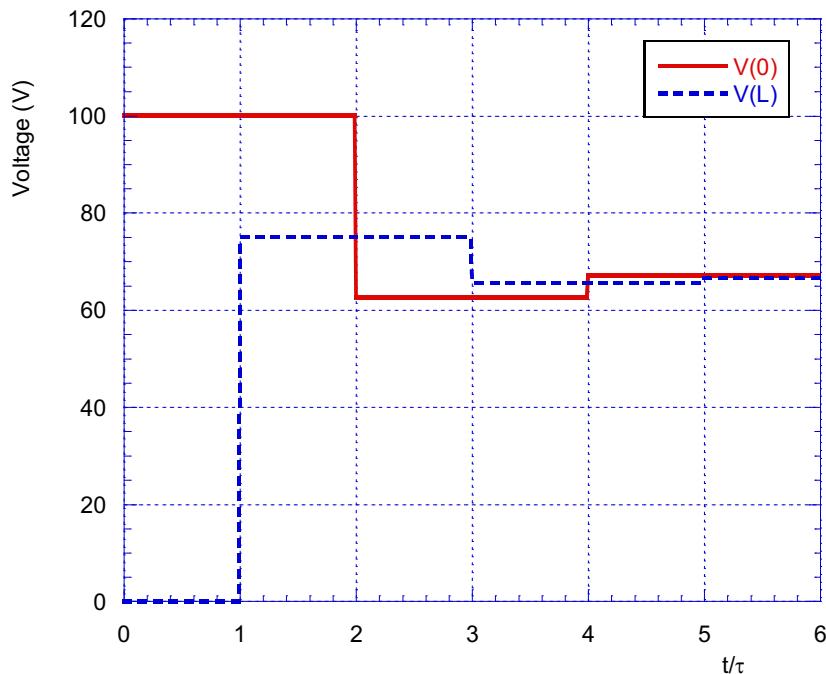

$$\rho_1 = \frac{R_s - Z_c}{R_s + Z_c} = 0.5 \quad \rho_2 = \frac{R_L - Z_c}{R_L + Z_c} = -0.25$$



Bergeron's diagram:

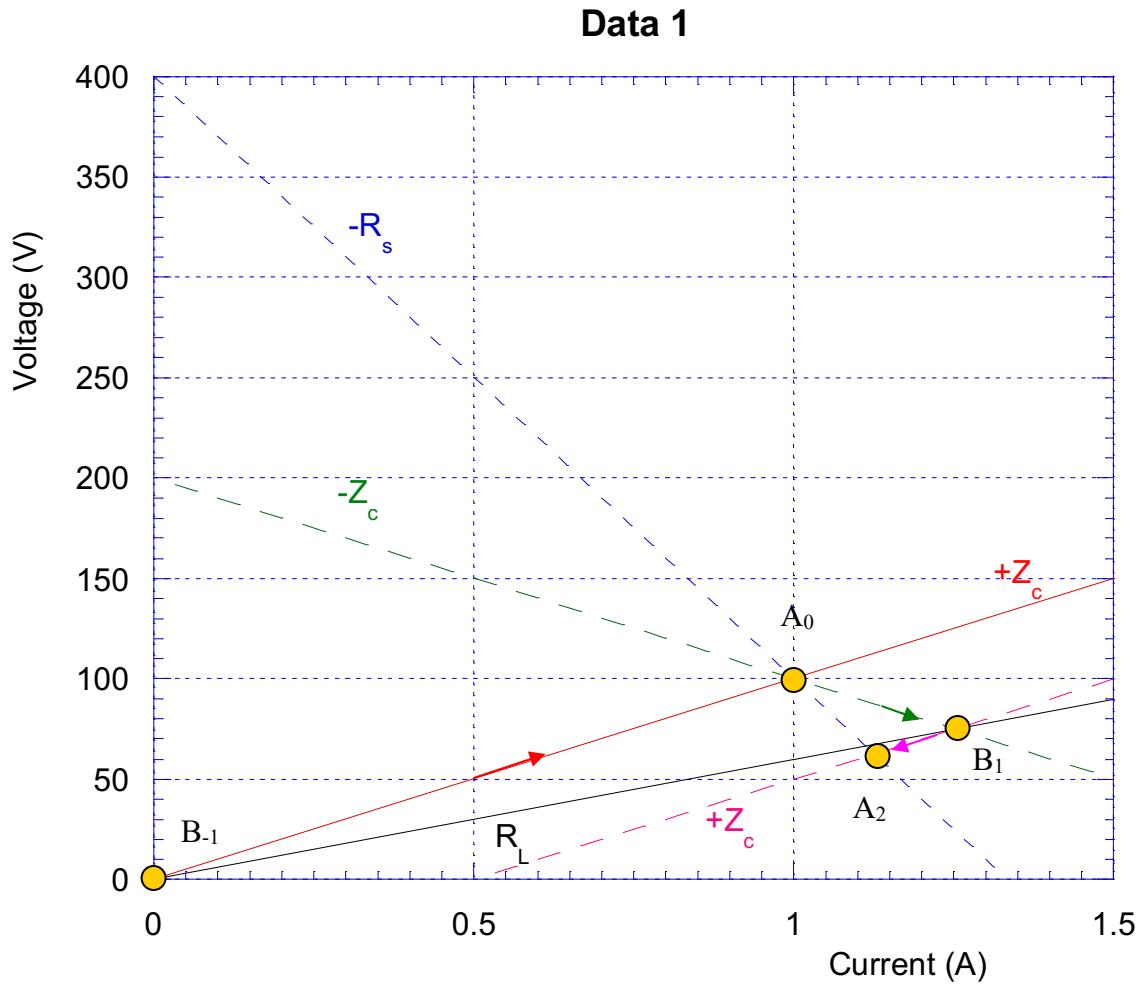

$$2. Z_c = 50 \Omega, R_s = 50 \Omega.$$

$$v = \frac{c}{\sqrt{\epsilon_r}} = 2 \cdot 10^8 \text{ m/s}, 2\tau = 6 \mu\text{s} \Rightarrow \tau = 3 \mu\text{s}$$

$$L = v\tau = 600 \text{ m}$$

$$V_s = 200 \text{ V}$$


$$\rho_2 = 0.2 = \frac{R_L - 50}{R_L + 50} \Rightarrow R_L = 75 \Omega$$

$$3. Z_c = \frac{12}{0.150} = 80 \Omega$$

$$\rho_1 = -1, \rho_2 = \frac{R_L - Z_c}{R_L + Z_c}$$

$$-160 \text{ mA} = 150 \text{ mA}(-\rho_2)(1 - \rho_1) \Rightarrow \rho_2 = 0.53 \Rightarrow R_L = 260.4 \Omega$$

4.

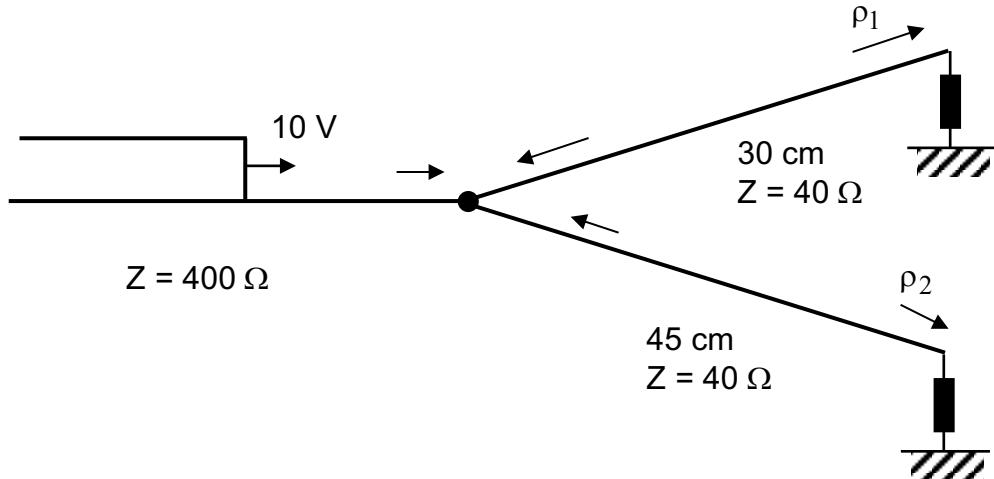

$$\rho_o = \frac{20 - 400}{20 + 400} = -0.9$$

$$\rho_1 = -1$$

$$\rho_2 = \frac{20 - 40}{20 + 40} = -0.33$$


$$\rho_3 = \rho_4 = \frac{36.36 - 40}{36.36 + 40} = -0.05$$

$$\tau_1 = 1 \text{ ns}, \quad \tau_2 = 1.5 \text{ ns}$$

$$V_o = (1 + \rho_o)10 = 1 \text{ V}$$

$$\Delta V_1 = \rho_1(1 + \rho_3)V_o = -0.95 \text{ V}$$
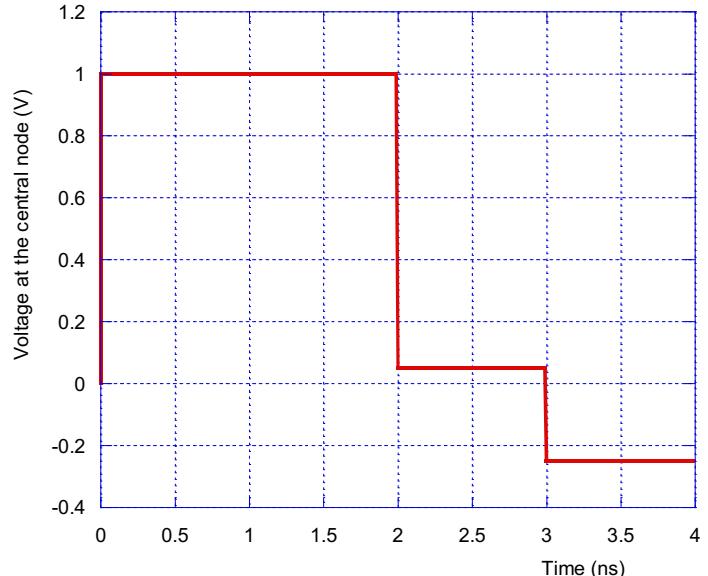
$$\Delta V_2 = \rho_2(1 + \rho_3)V_o = -0.3 \text{ V}$$



Note that ρ_o , ρ_3 , and ρ_4 are the 'initial' reflection coefficients seen by the front of the initial wave.

5. a

$$V = V^+ + V^- \quad V = V^{++}$$

$$I^+ + I^- = I_c + I^{++} \Leftrightarrow \frac{V^+}{Z_c} - \frac{V^-}{Z_c} = I_c + \frac{V^{++}}{Z_c} \Leftrightarrow V^+ - V^- = Z_c I_c + V^{++} \quad (1)$$

$$V^+ + V^- = V^{++} \quad (2)$$

$$I_c = C \frac{dV^{++}}{dt} \quad (3)$$

$$(2)-(1): V^- = -\frac{Z_c I_c}{2}$$

$$(2)+(1), \text{ taking into account (3): } \frac{dV^{++}}{dt} + \frac{2}{Z_c C} V^{++} = \frac{2V^+}{Z_c C}$$

General solution:

$$V^{++}(t) = V^+ (1 - e^{-t/\tau}), \quad \tau = \frac{Z_c C}{2}$$

$$0.9 = 1 - e^{-t/\tau} \Rightarrow t = 1.15 Z_c C = 57.5 \text{ ps}$$

5.b

$$I^{++} = I^+ + I^- \Leftrightarrow \frac{V^{++}}{Z_c} = \frac{V^+}{Z_c} - \frac{V^-}{Z_c} \Leftrightarrow V^{++} = V^+ - V^- \quad (1)$$

$$V^+ + V^- = L \frac{dI^{++}}{dt} + V^{++} = \frac{L}{Z_c} \frac{dV^{++}}{dt} + V^{++} \quad (2)$$

$$(1)+(2): 2V^+ = \frac{L}{Z_c} \frac{dV^{++}}{dt} + V^{++} \Leftrightarrow \frac{dV^{++}}{dt} + \frac{2Z_c}{L} V^{++} = \frac{2Z_c}{L} V^+$$

$$\text{General Solution: } V^{++}(t) = V^+ (1 - e^{-t/\tau}), \quad \tau = \frac{L}{2Z_c}$$

$$0.9 = 1 - e^{-t/\tau} \Rightarrow t = 1.15 \frac{L}{Z_c} = 57.5 \text{ ps}$$