

Electromagnetic Compatibility Problem Set 1 solutions

1.a $v(x + \Delta x, t) - v(x, t) = -L' \Delta x \frac{\partial}{\partial t} \left\{ i(x, t) - C' \frac{\Delta x}{2} \frac{\partial v(x, t)}{\partial t} \right\}$

$$i(x + \Delta x, t) - i(x, t) = - \left\{ C' \frac{\Delta x}{2} \frac{\partial v(x, t)}{\partial t} + C' \frac{\Delta x}{2} \frac{\partial v(x + \Delta x, t)}{\partial t} \right\}$$

Dividing by Δx and taking the limit $\Delta x \rightarrow 0$:

$$\frac{\partial v(x, t)}{\partial x} = -L' \frac{\partial i(x, t)}{\partial t}$$

$$\frac{\partial i(x, t)}{\partial x} = -C' \frac{\partial v(x, t)}{\partial t}$$

1.b $v(x + \Delta x, t) - v(x, t) = -L' \frac{\Delta x}{2} \frac{\partial i(x, t)}{\partial t} - L' \frac{\Delta x}{2} \frac{\partial i(x + \Delta x, t)}{\partial t}$

$$i(x + \Delta x, t) - i(x, t) = -C' \Delta x \frac{\partial}{\partial t} \left\{ v(x, t) - L' \frac{\Delta x}{2} \frac{\partial i(x, t)}{\partial t} \right\}$$

Dividing by Δx and taking the limit $\Delta x \rightarrow 0$:

$$\frac{\partial v(x, t)}{\partial x} = -L' \frac{\partial i(x, t)}{\partial t}$$

$$\frac{\partial i(x, t)}{\partial x} = -C' \frac{\partial v(x, t)}{\partial t}$$

2. $f = 250 \text{ kHz}, Z_c = 93 \Omega, \beta = 96.28 \cdot 10^{-3} \text{ rad/m}$

$$Z_c = \sqrt{\frac{L'}{C'}}, \beta = \omega \sqrt{L' C'}$$

$$\rightarrow C' = \frac{\beta}{\omega Z_c} = 0.659 \text{ nF/m} \quad \text{and} \quad L' = \frac{\beta^2}{\omega^2 C'^2} = 5.7 \mu\text{H/m}$$

3.

$$\begin{aligned} \gamma &= \sqrt{(R' + j\omega L')(G' + j\omega C')} \\ &= \sqrt{L' \left(\frac{R'}{L'} + j\omega \right) C' \left(\frac{G'}{C'} + j\omega \right)} \\ &= \sqrt{L' C'} \sqrt{\left(\frac{R'}{L'} + j\omega \right) \left(\frac{G'}{C'} + j\omega \right)} \end{aligned}$$


Posing $\frac{R'}{L'} = \frac{G'}{C'} = k$, the propagation constant becomes :

$$\gamma = \sqrt{L' C'} (k + j\omega)$$

With

$$\alpha = k \sqrt{L' C'}, \quad \beta = \omega \sqrt{L' C'} \quad \text{and} \quad v = \frac{\omega}{\beta} = \frac{1}{\sqrt{L' C'}}$$

4.

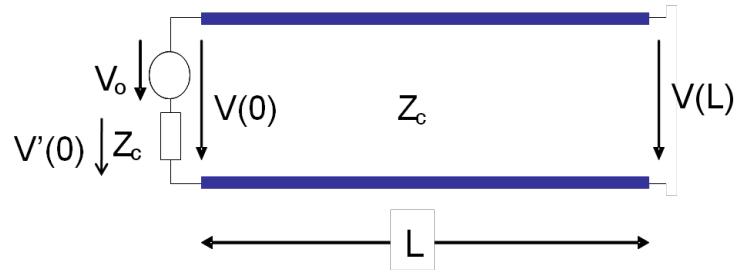

Inserting into the general frequency domain solutions of a two-wire transmission line the following values:

$$\rho_1 = 0, \rho_2 = 1, I_o = 0, x_s = 0$$

It results for the voltage across the left terminal impedance:

$$V'(0) = \frac{\exp(-\gamma L)}{2} [-(\exp(\gamma L) - \exp(-\gamma L))V_o] = -\frac{1}{2} [1 - \exp(-2\gamma L)]V_o$$

And the voltages $V(0)$ and $V(L)$ are given by

$$V(0) = V'(0) + V_o = \frac{V_o}{2} [1 + \exp(-2\gamma L)]$$

$$V(L) = \exp(-\gamma L)V_o$$

For a lossless line, the above equations reduce to

$$V(0) = \frac{V_o}{2} [1 + \exp(-2j\omega L/c)]$$

$$V(L) = \exp(-j\omega L/c)V_o$$

which can be converted into the time domain:

$$v(0, t) = \frac{v_o(t)}{2} + \frac{v_o(t - 2L/c)}{2}$$

$$v(L, t) = v_o(t - L/c)$$

5. a) $\rho = \frac{510-457}{510+457} = 0.055$

Transmission coefficient: $\tau = 1 + \rho = 1.055$

b) $V_{tot} = V_{inc} + V_{ref} = (1 + \rho)V_{inc} = 10.55 \text{ kV}$

c) $V_{trans} = V_{tot} = (1 + \rho)V_{inc} = \tau V_{inc} = 10.55 \text{ kV}$

$$V_{ref} = \rho V_{inc} = 0.55 \text{ kV}$$


d) $I_{ref} = -\frac{V_{ref}}{Z_{c1}} = -1.2 \text{ A}$

$$I_{trans} = \frac{V_{trans}}{Z_{c2}} = 20.7 \text{ A}$$

6.

A. We choose the Agrawal et al. formulation. In this case, the coupling is represented using two lumped sources at the two line extremities.

Equivalent circuit for the coupling:

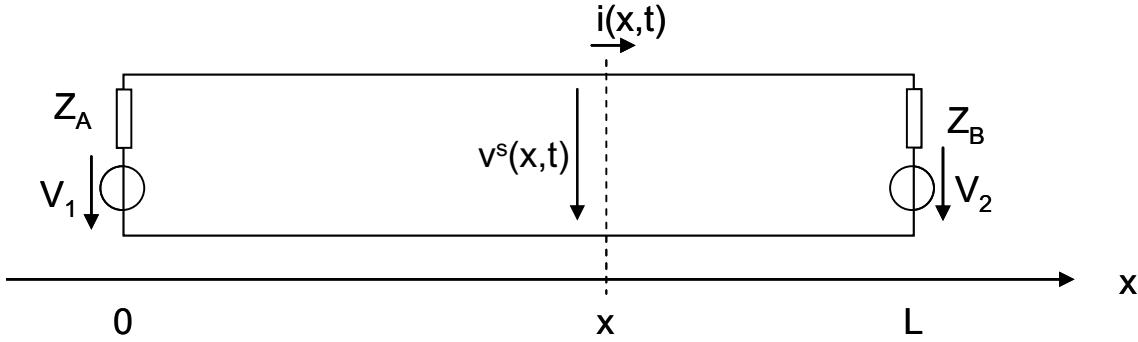

B. The expressions for the sources $V1$ and $V2$ are given by:

$$V_1(t) = \int_0^h E^e(0, t) dz = E^e(0, t)h$$

$$V_2(t) = \int_0^h E^e(L, t) dz = \int_0^h E^e(0, t) dz = E^e(0, t)h$$

The induced current at an arbitrary position x along the line reads :

$$i(x, t) = \frac{h}{2Z_c} E^e(0, t - x/c) - \frac{h}{2Z_c} E^e(0, t - (L-x)/c)$$


And the scattered voltage is given by:

$$v^s(x, t) = \frac{h}{2} E^e(0, t - x/c) + \frac{h}{2} E^e(0, t - (L-x)/c)$$

The total voltage can be obtained as follows :

$$\begin{aligned} v(x, t) &= v^s(x, t) - \int_0^h E^e(x, t) dz = v^s(x, t) - E^e(x, t)h = v^s(x, t) - E^e(0, t)h \\ &= \frac{h}{2} E^e(0, t - x/c) + \frac{h}{2} E^e(0, t - (L-x)/c) - hE^e(0, t) \\ &= -hE^e(0, t) + \frac{h}{2} E^e(0, t - x/c) + \frac{h}{2} E^e(0, t - (L-x)/c) \end{aligned}$$

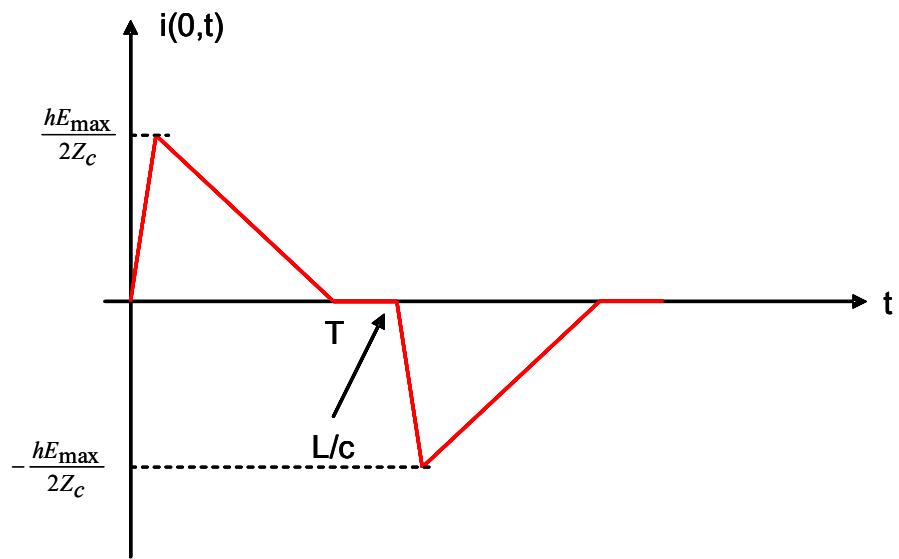C. Representation of the current $i(0, t)$ for the given exciting field :



D. The currents and voltages will tend to zero.

7. Arrangement c.