


Electrotechnique-II

MICRO-101: week 5



- Three-phase systems:
 - Delta and Y-networks
 - Dissipated power
 - Instantaneous power

- What you should know after the class:
 - Currents and voltages in Delta and Y-networks
 - Time-dependency of powers


Balanced Y-network

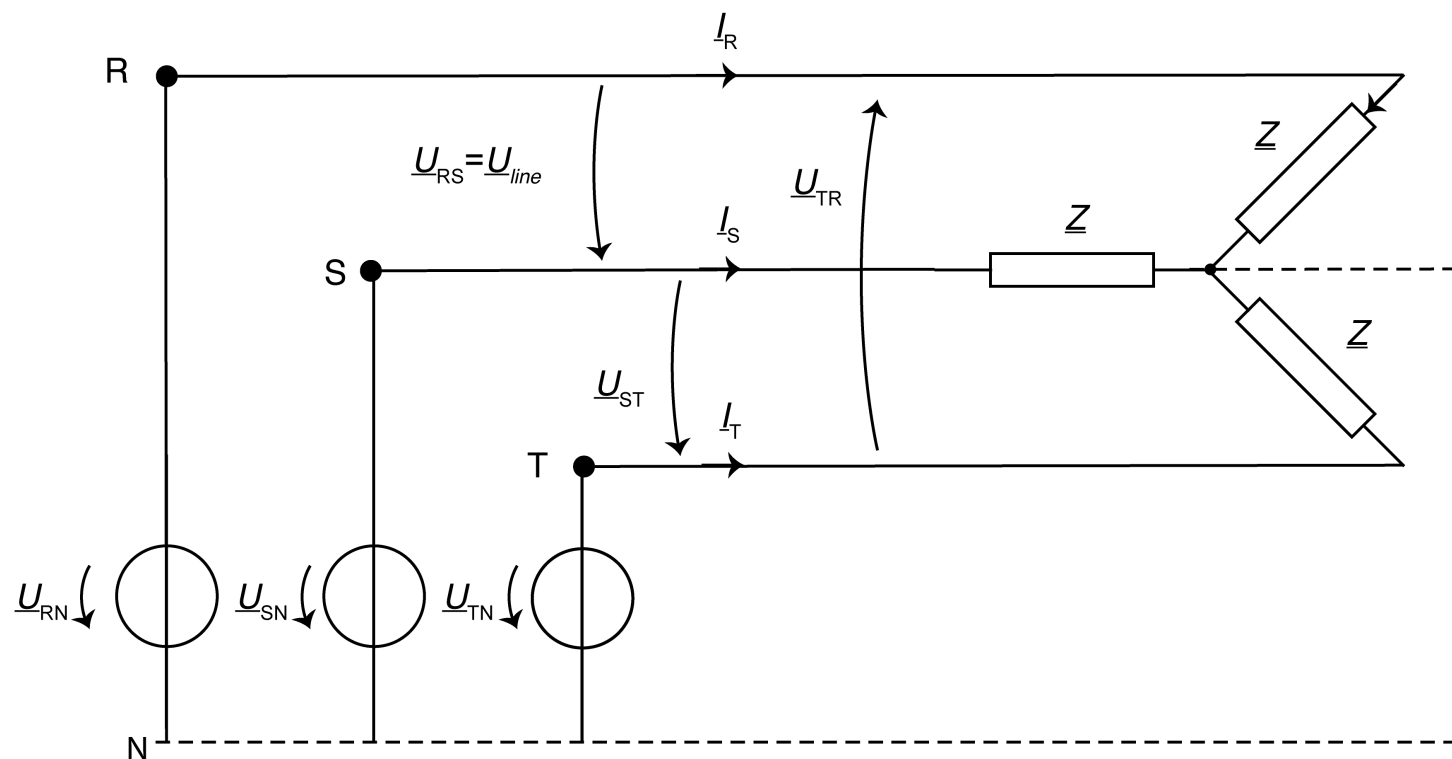



Balanced Y-network

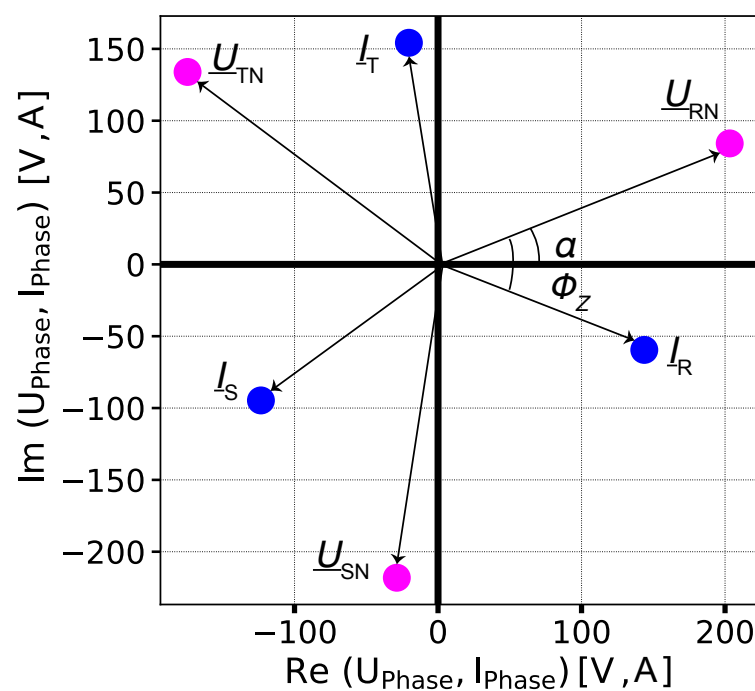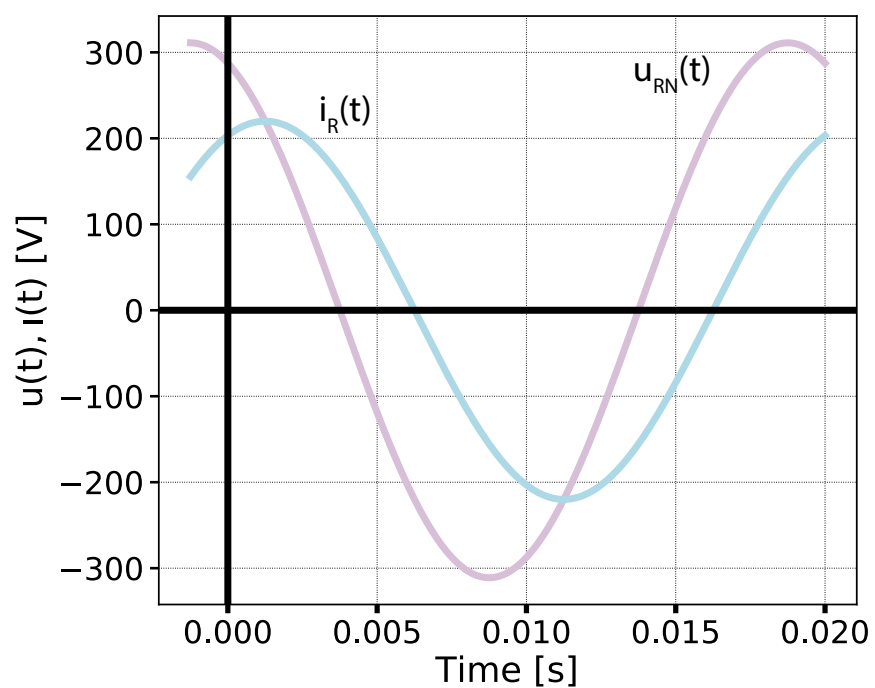

Balanced Δ -network

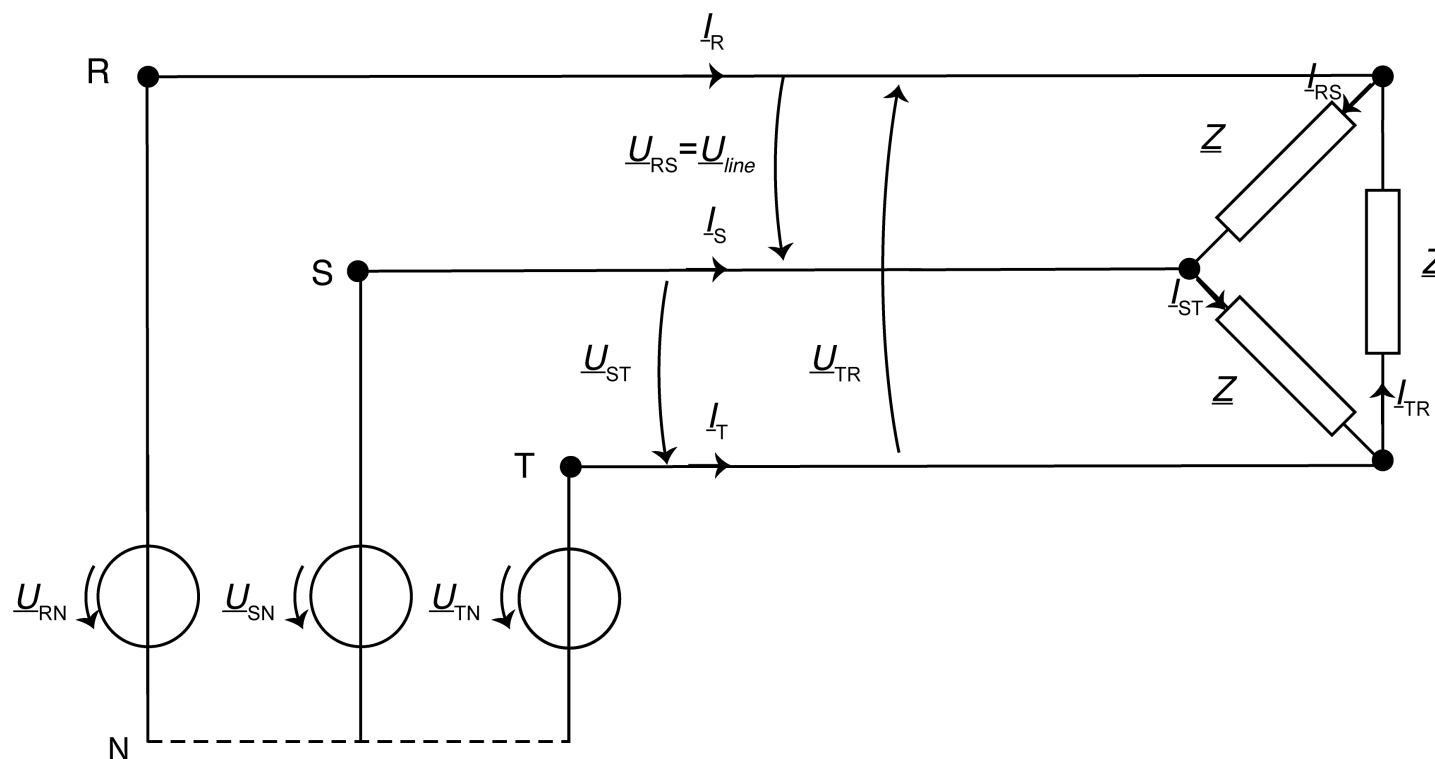

Balanced Δ -network

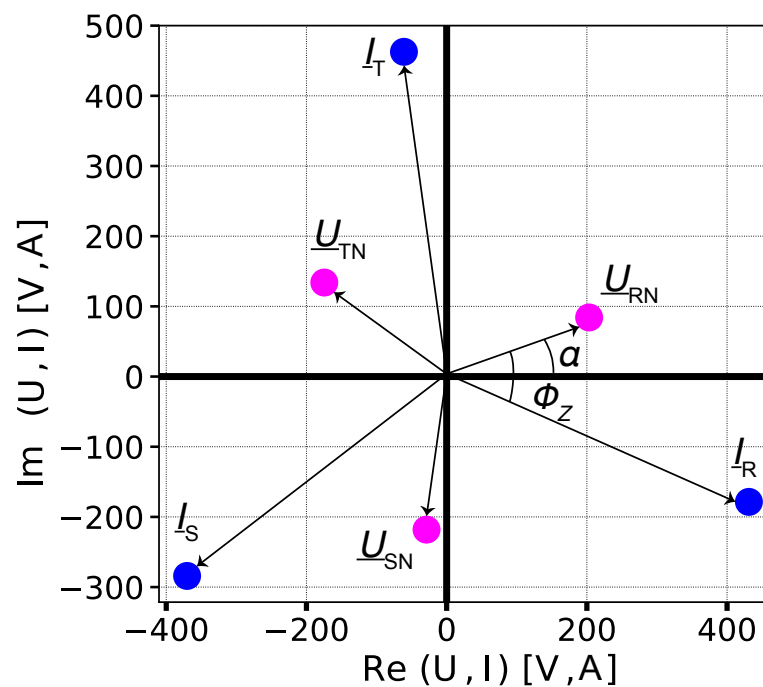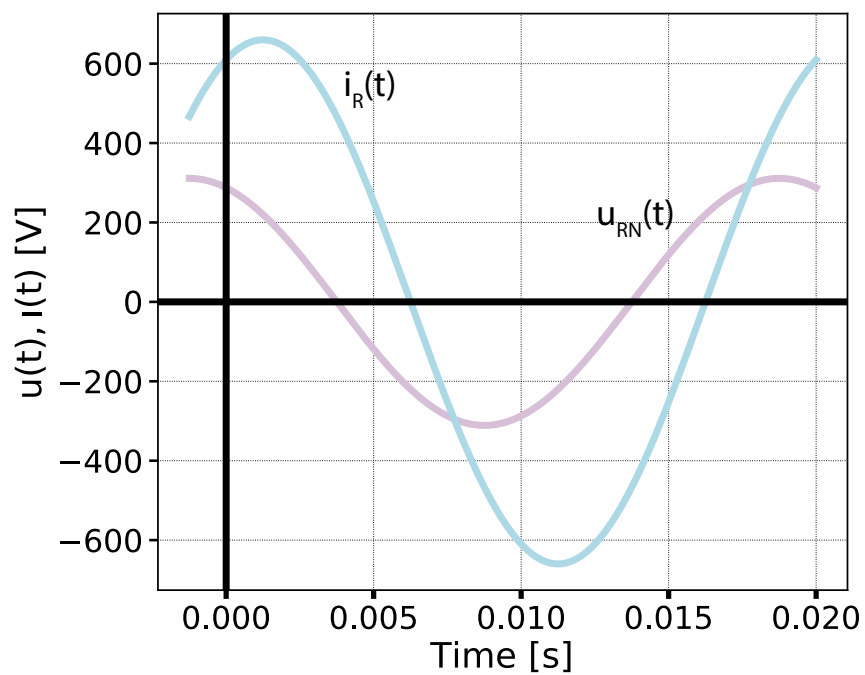

Summary

	Y-network	Δ -network
Phase voltages	$\underline{U}_{RN} = U e^{j\alpha}$ $\underline{U}_{SN} = U e^{j\alpha} e^{-j\frac{2\pi}{3}}$ $\underline{U}_{TN} = U e^{j\alpha} e^{-j\frac{4\pi}{3}}$	$\underline{U}_{RS} = \sqrt{3} U e^{j\alpha} e^{j\frac{\pi}{6}}$ $\underline{U}_{ST} = \sqrt{3} U e^{j\alpha} e^{j\frac{\pi}{6}} e^{-j\frac{2\pi}{3}}$ $\underline{U}_{TR} = \sqrt{3} U e^{j\alpha} e^{j\frac{\pi}{6}} e^{-j\frac{4\pi}{3}}$
Line voltages	$\underline{U}_{RS} = \sqrt{3} \underline{U}_{RN} e^{j\frac{\pi}{6}} = \sqrt{3} U e^{j(\alpha + \frac{\pi}{6})}$ $\underline{U}_{ST} = \sqrt{3} \underline{U}_{SN} e^{j\frac{\pi}{6}} = \sqrt{3} U e^{j(\alpha + \frac{\pi}{6})} e^{-j\frac{2\pi}{3}}$ $\underline{U}_{TR} = \sqrt{3} \underline{U}_{TN} e^{j\frac{\pi}{6}} = \sqrt{3} U e^{j(\alpha + \frac{\pi}{6})} e^{-j\frac{4\pi}{3}}$	same as for Y-network
Phase currents	$\underline{I}_R = \frac{\underline{U}_{RN}}{Z} = \frac{U}{Z} e^{j(\alpha - \phi_z)}$ $\underline{I}_S = \frac{\underline{U}_{SN}}{Z} = \frac{U}{Z} e^{j(\alpha - \phi_z)} e^{-j\frac{2\pi}{3}}$ $\underline{I}_T = \frac{\underline{U}_{TN}}{Z} = \frac{U}{Z} e^{j(\alpha - \phi_z)} e^{-j\frac{4\pi}{3}}$	$\underline{I}_{RS} = \frac{\underline{U}_{RS}}{Z} = \frac{\sqrt{3} U}{Z} e^{j(\alpha + \frac{\pi}{6} - \phi_z)}$ $\underline{I}_{ST} = \frac{\underline{U}_{ST}}{Z} = \frac{\sqrt{3} U}{Z} e^{j(\alpha + \frac{\pi}{6} - \phi_z)} e^{-j\frac{2\pi}{3}}$ $\underline{I}_{TR} = \frac{\underline{U}_{TR}}{Z} = \frac{\sqrt{3} U}{Z} e^{j(\alpha + \frac{\pi}{6} - \phi_z)} e^{-j\frac{4\pi}{3}}$
Line currents	$\underline{I}_R = \frac{\underline{U}_{RN}}{Z} = \frac{U}{Z} e^{j(\alpha - \phi_z)}$ $\underline{I}_S = \frac{\underline{U}_{SN}}{Z} = \frac{U}{Z} e^{j(\alpha - \phi_z)} e^{-j\frac{2\pi}{3}}$ $\underline{I}_T = \frac{\underline{U}_{TN}}{Z} = \frac{U}{Z} e^{j(\alpha - \phi_z)} e^{-j\frac{4\pi}{3}}$	$\underline{I}_R = 3 \frac{\underline{U}_{RN}}{Z} = \frac{3U}{Z} e^{j(\alpha - \phi_z)}$ $\underline{I}_S = \frac{3 \underline{U}_{SN}}{Z} = \frac{3U}{Z} e^{j(\alpha - \phi_z)} e^{-j\frac{2\pi}{3}}$ $\underline{I}_T = \frac{3 \underline{U}_{TN}}{Z} = \frac{3U}{Z} e^{j(\alpha - \phi_z)} e^{-j\frac{4\pi}{3}}$
Power	$\underline{S}_Y = 3 \frac{U^2}{Z} e^{j\phi_z}$	$\underline{S}_\Delta = 9 \frac{U^2}{Z} e^{j\phi_z}$