

Electrotechique-II


MICRO-101: week 9

- What you have seen last time:
 - Time-response of L (ch. 6.2.3.), RL circuits (ch. 6.3.2)
- Today:
 - Wrap up RL circuits (ch. 6.3.2)
 - Transient behavior of AC-powered RL circuits (ch. 6.4)
 - Solving of past exam (during exercise class)
- Next weeks
 - Lab work

1-slide recap of last week

RL circuit (Ch. 6.3.2)

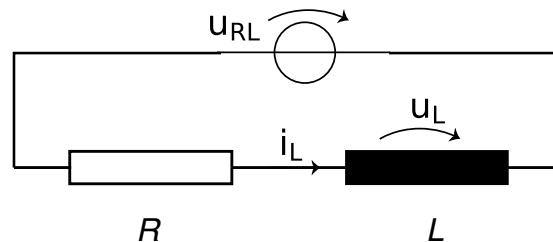- Rule 1: In real systems (with non-zero resistance) – **the current flowing through an inductor can not change suddenly (no current jump)**



- Boundary conditions:

$$t < 0$$

$$i_L = 0$$

$$u_L = 0$$

$$t \geq 0$$

$$i_L = \frac{u_0}{R} \left(1 - e^{-\frac{tR}{L}}\right)$$


$$u_L = L \frac{di_L}{dt} = u_0 e^{-\frac{tR}{L}}$$

- Rule 2: at $t = \infty$, the inductor behaves like a short circuit

Today



RL circuit (Ch. 6.3.2)

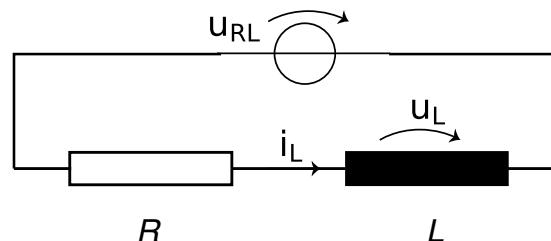- Rule 1: In real systems (with non-zero resistance) – the current flowing through an inductor can not change suddenly (no current jump) $t \geq 0$




$$i_L = \frac{u_0}{R} \left(1 - e^{-\frac{tR}{L}}\right)$$
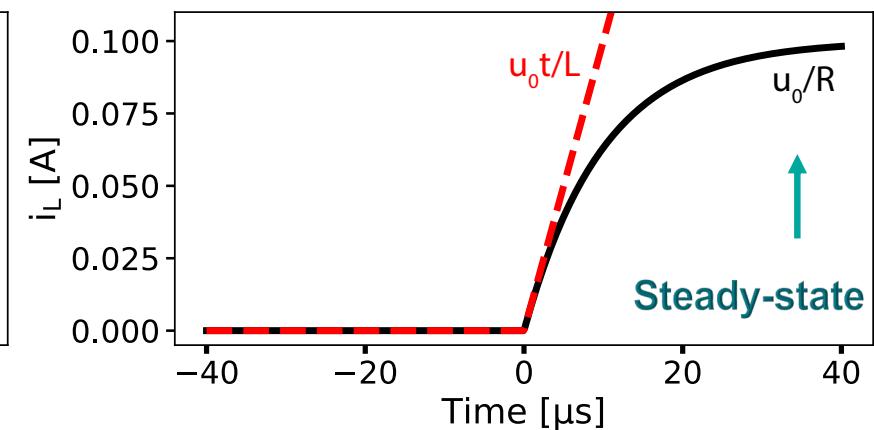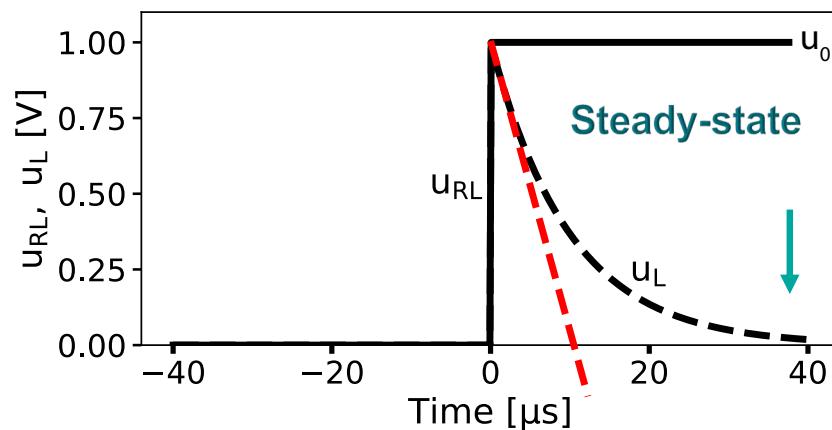
$$u_L = L \frac{di_L}{dt} = u_0 e^{-\frac{tR}{L}}$$



RL circuit (Ch. 6.3.2)

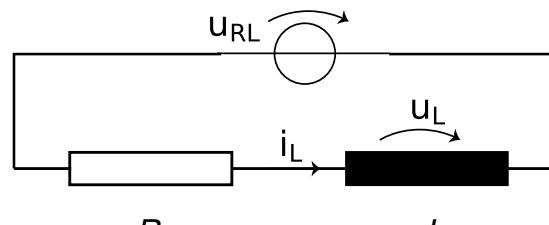- Rule 2: In real systems (with non-zero resistance) – **the current flowing through an inductor can not change suddenly (no current jump)**



$$t \geq 0$$

$$i_L = \frac{u_0}{R} \left(1 - e^{-\frac{tR}{L}}\right)$$

$$u_L = L \frac{di_L}{dt} = u_0 e^{-\frac{tR}{L}}$$

We find that the current ramps up with a characteristic time constant $\tau_{RL} = \frac{L}{R}$. The RL time constant can be reduced for example by decreasing L.

At $t = 0$, the voltage spikes to a value of $u_L(t = 0) = u_0$ after which it decreases again with the same slope as the current. We note that for $L \rightarrow 0$ we find back the case of the resistor connected to a voltage source which is switched on.


Summary: RC versus RL circuit

- RC
 - No voltage jump
 - at $t = \infty$, the capacitor behaves like an open circuit
- You can use these rules to compute steady-state values
- RL
 - No current jump
 - at $t = \infty$, the inductor behaves like a short circuit
- You can use these rules to compute steady-state values

AC-powered RL circuit (ch. 6.4.)

- Applied voltage source is alternating at frequency ω with peak value \hat{U} and phase offset α :
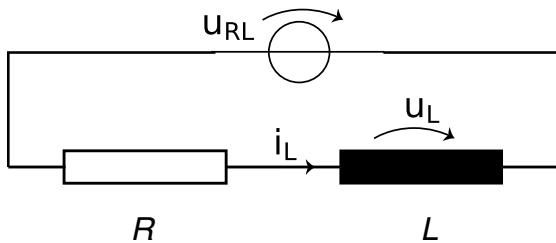
$$u_{RL} = \hat{U} \cos(\omega t + \alpha) h(t)$$



(solving at the blackboard)

- Boundary conditions

$$t < 0$$


$$i_L = 0$$

$$u_L = 0$$

AC-powered RL circuit (ch. 6.4.)

- Applied voltage source is alternating at frequency ω with peak value \hat{U} and phase offset α :
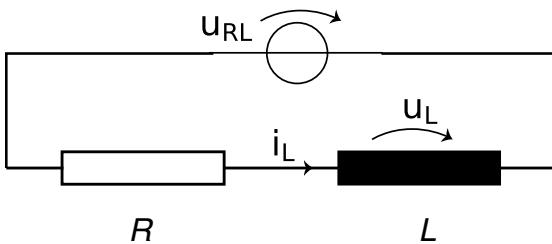
$$u_{RL} = \hat{U} \cos(\omega t + \alpha) h(t) \quad \longrightarrow \quad t \geq 0 :$$



$$\hat{U} \cos(\omega t + \alpha) = i_L R + L \frac{di_L}{dt}$$

Find solution to the homogeneous diff. eq. i_h and a particular solution i_p

- Boundary conditions

$$t < 0$$


$$i_L = 0$$

$$u_L = 0$$

AC-powered RL circuit (ch. 6.4.)

- Applied voltage source is alternating at frequency ω with peak value \hat{U} and phase offset α :
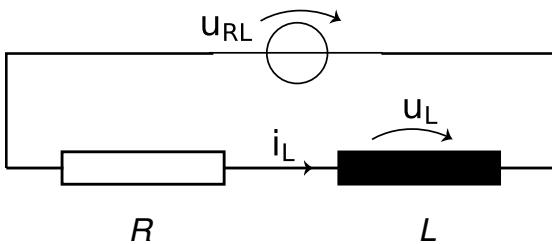
$$u_{RL} = \hat{U} \cos(\omega t + \alpha) h(t) \quad \longrightarrow \quad t \geq 0 :$$



$$\hat{U} \cos(\omega t + \alpha) = i_L R + L \frac{di_L}{dt}$$

Find solution to the homogeneous diff. eq. i_h and a particular solution i_p

$$i_h = i_0 e^{-\frac{tR}{L}}$$


$$i_p = \frac{\hat{U}}{Z} \cos(\omega t + \alpha - \phi_Z) = \frac{\hat{U}}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \alpha - \arctan \frac{\omega L}{R})$$

$$i_L = i_p + i_h = \frac{\hat{U}}{Z} \cos(\omega t + \alpha - \phi_Z) + i_0 e^{-\frac{tR}{L}}$$


$$i_0 = -\frac{\hat{U}}{Z} \cos(\alpha - \phi_Z)$$

AC-powered RL circuit (ch. 6.4.)

- no current jump but voltage jump!

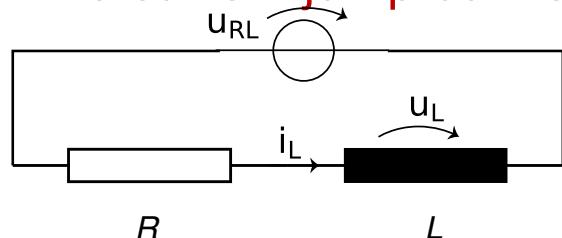

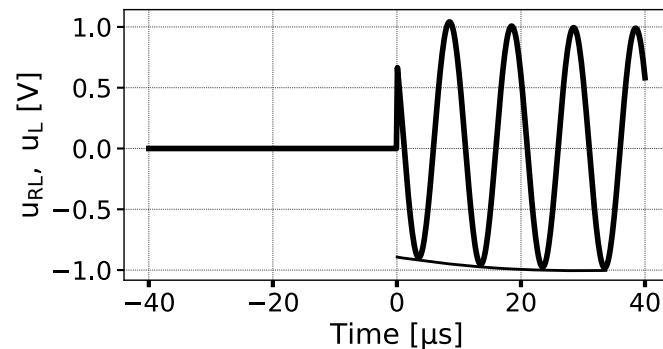
$$u_L = u_{RL} - i_L R = \hat{U} \cos(\omega t + \alpha) - \frac{\hat{U} R}{Z} (\cos(\omega t + \alpha - \phi_Z) - \cos(\alpha - \phi_Z) e^{-\frac{tR}{L}})$$



$$i_L = \frac{\hat{U}}{Z} (\cos(\omega t + \alpha - \phi_Z) - \cos(\alpha - \phi_Z) e^{-\frac{tR}{L}})$$
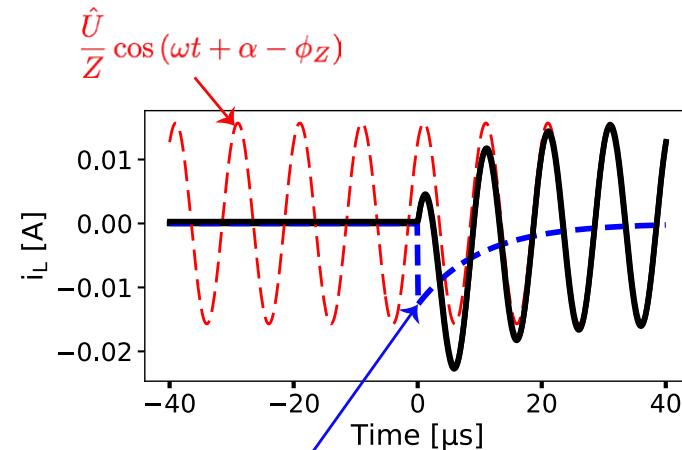
$$u_L = \hat{U} \cos(\omega t + \alpha) - \frac{\hat{U} R}{Z} (\cos(\omega t + \alpha - \phi_Z) - \cos(\alpha - \phi_Z) e^{-\frac{tR}{L}})$$



Written exam

- Counts 80% of final grade (TP counts 20%)
- You can bring along any **printed** material (script, books, notes)
- **No electronics** allowed (no cell phone, no smart watch, no tablets etc). Only **exception**: calculator without internet functionality.
- Exam duration: 3 hours
- Seat map sent out 1 week before exam
- Students who took the TP in spring 2024 have the choice between:
 - re-register for the TP and retake TP exam (counts 20% of the grade)
 - or keep last year's TP grade.