

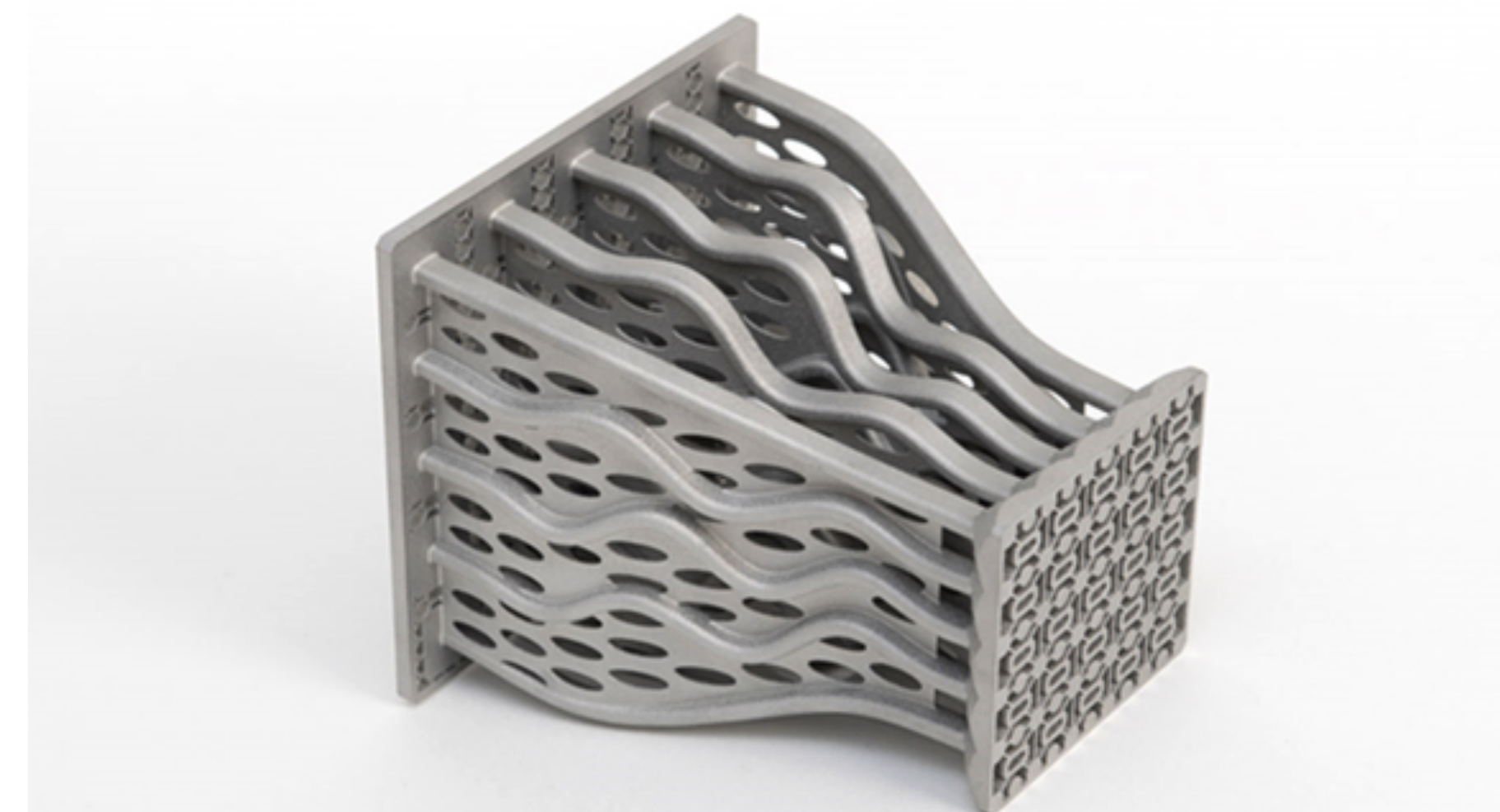
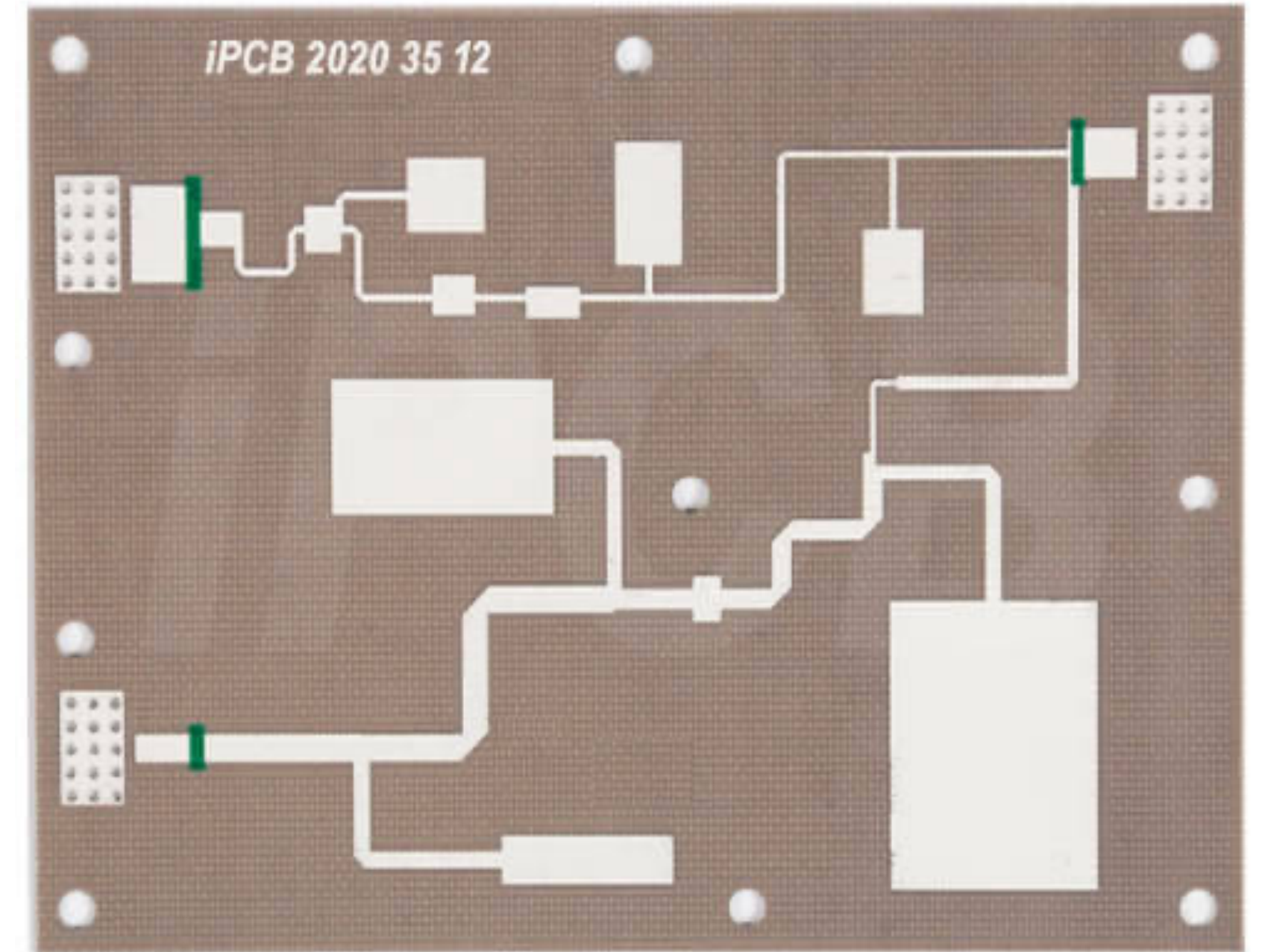
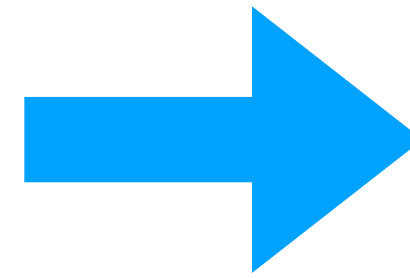


Microwave engineering in physics 2025: key topics & notions

From wires to transmission lines

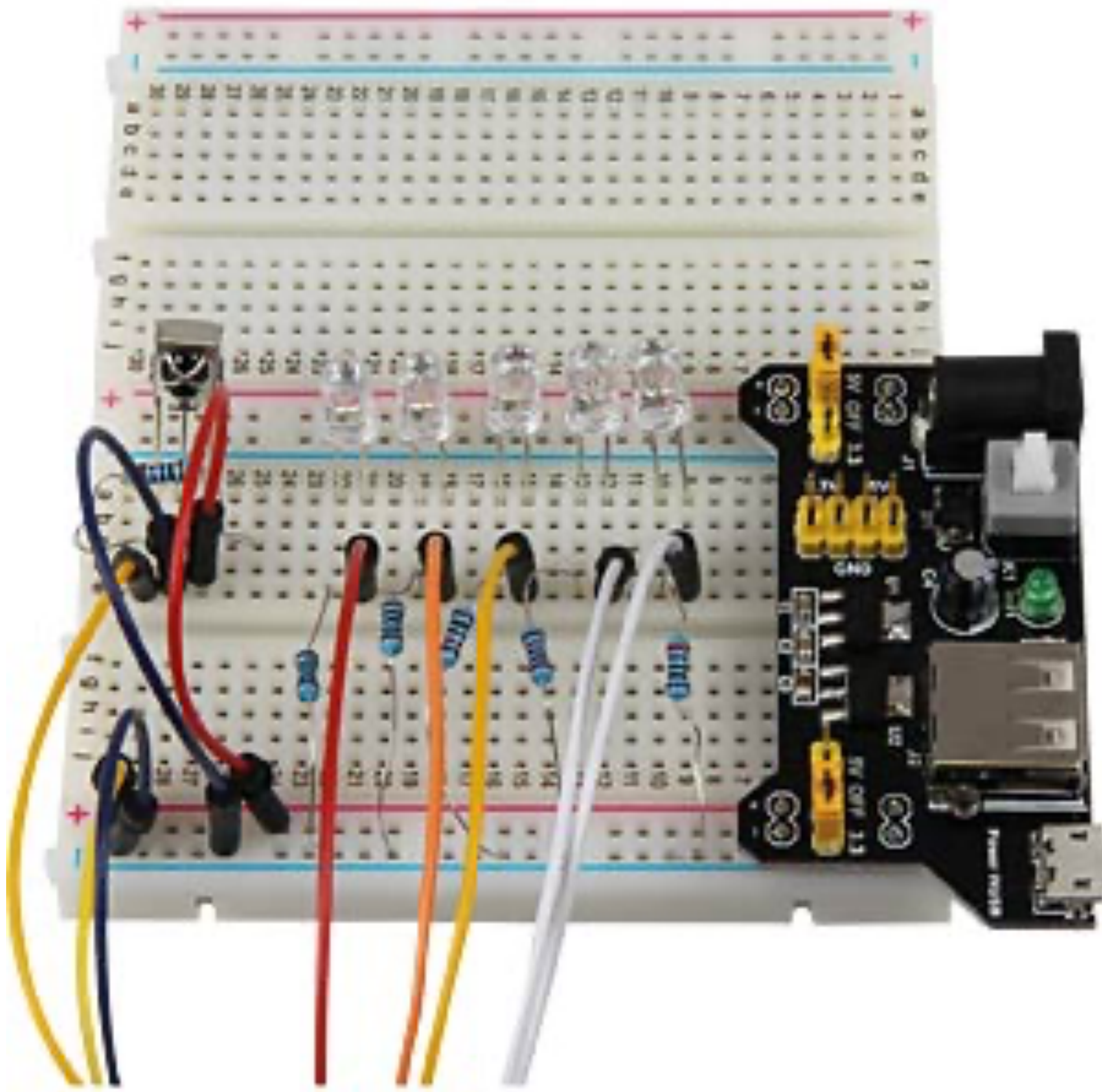


Waves in a TEM transmission lines

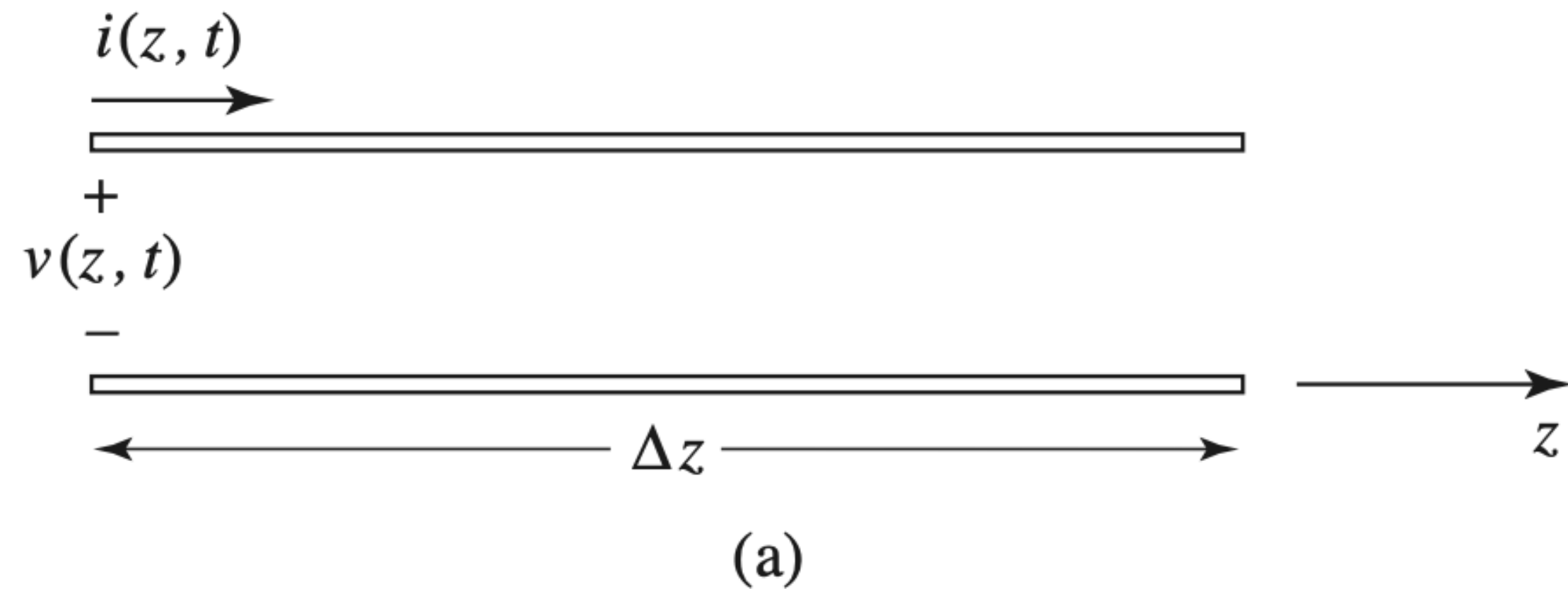

$$V(z) = V_o^+ e^{-\gamma z} + V_o^- e^{\gamma z},$$

$$I(z) = I_o^+ e^{-\gamma z} + I_o^- e^{\gamma z},$$
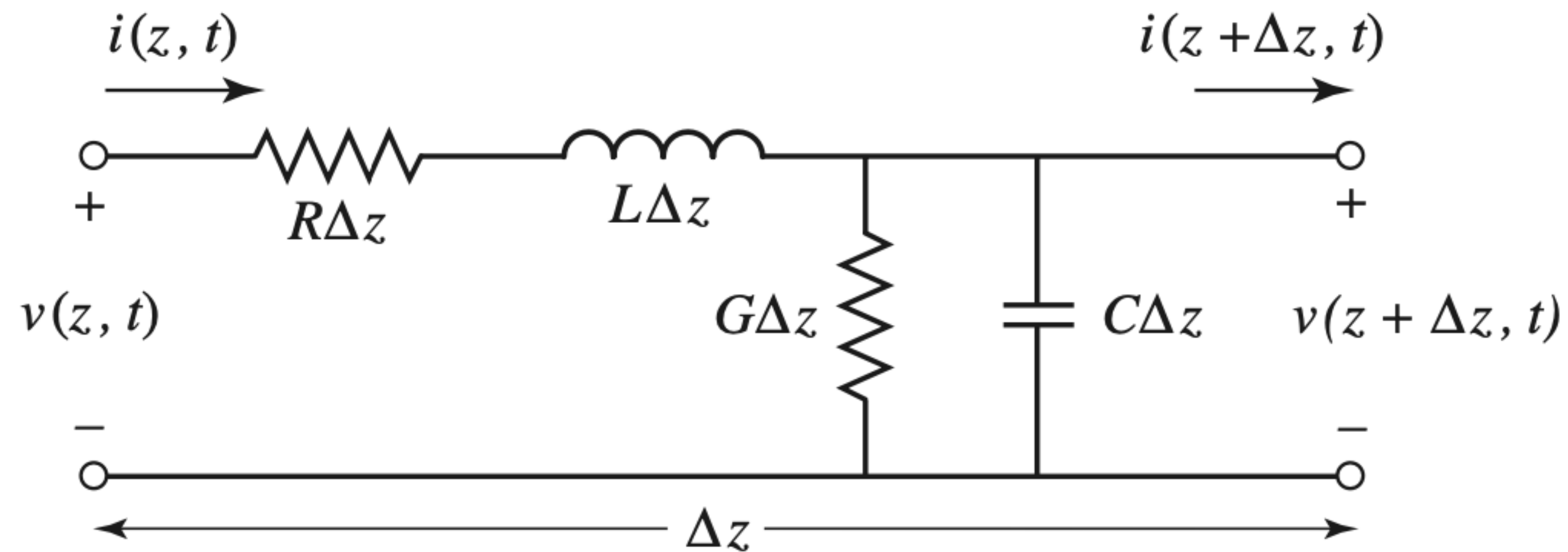
$$\frac{V_o^+}{I_o^+} = Z_0 = \frac{-V_o^-}{I_o^-}$$



$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

dispersion

loss


$$Z_0 = \frac{R + j\omega L}{\gamma} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

wave impedance

Frequency dependence of L or C generally leads to dispersion

engineering notation $j = \sqrt{-1}$

Reflectometry and input impedance

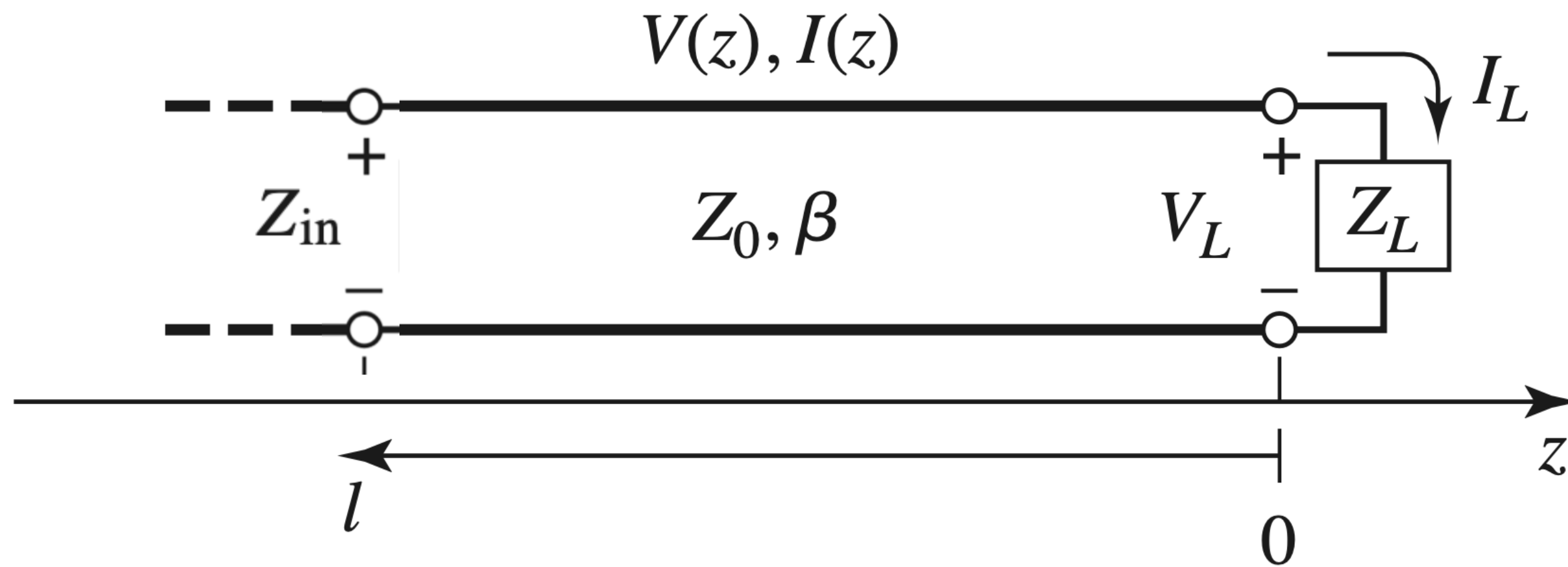

$$V(z) = V_o^+ e^{-\gamma z} + V_o^- e^{\gamma z}$$

Reflection coefficient

$$\Gamma = \frac{V_o^-}{V_o^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$


Input impedance

$$Z_{\text{in}} = \frac{V(-l)}{I(-l)} = \frac{V_o^+ (e^{j\beta l} + \Gamma e^{-j\beta l})}{V_o^+ (e^{j\beta l} - \Gamma e^{-j\beta l})} Z_0 = \frac{1 + \Gamma e^{-2j\beta l}}{1 - \Gamma e^{-2j\beta l}} Z_0$$

Matching

$$Z_L = Z_0$$

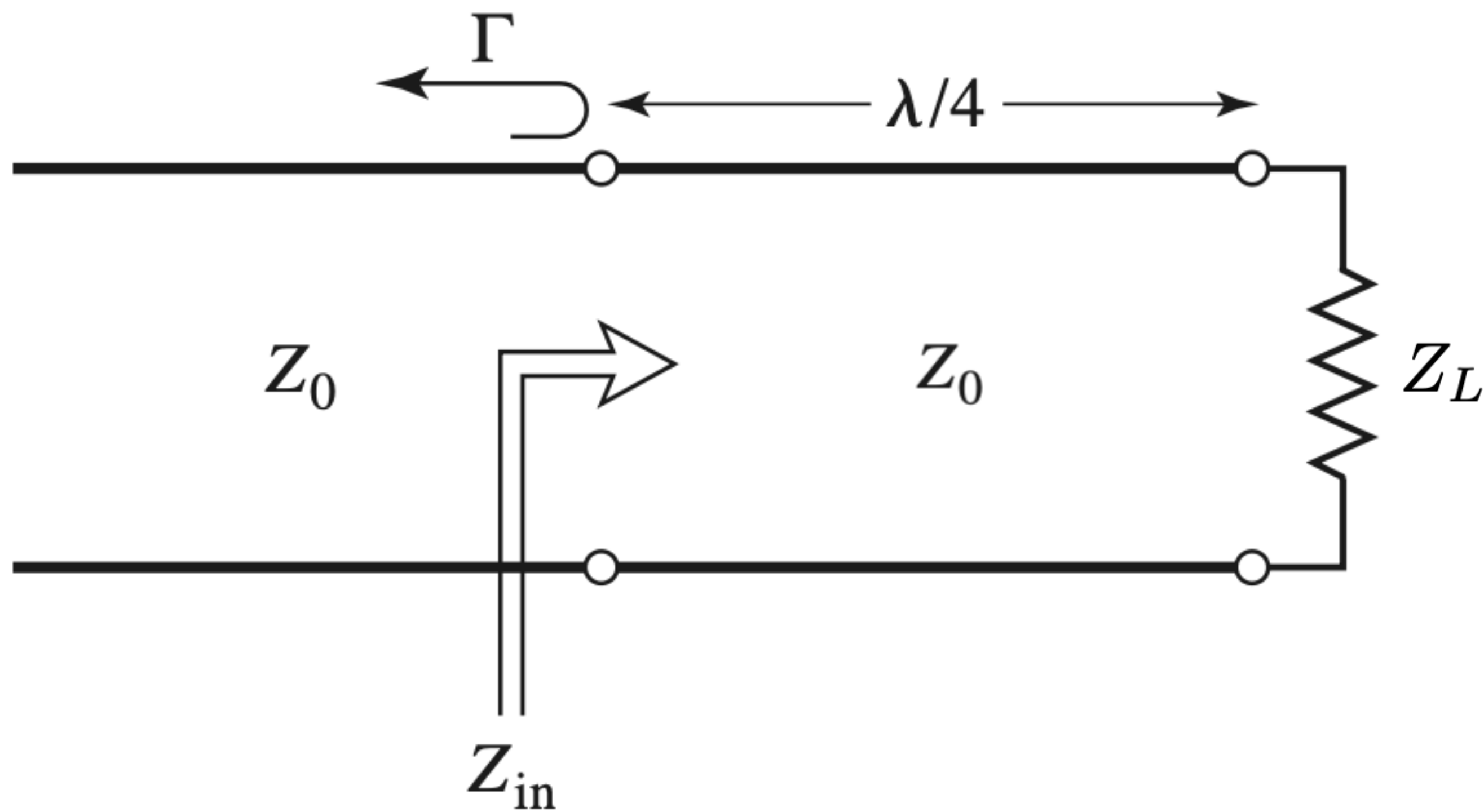
Elementary impedance matching: 1/4-wave transformer



on-resonance



$$Z_{in} = Z_0^2 / Z_L$$

transformation-bandwidth tradeoff

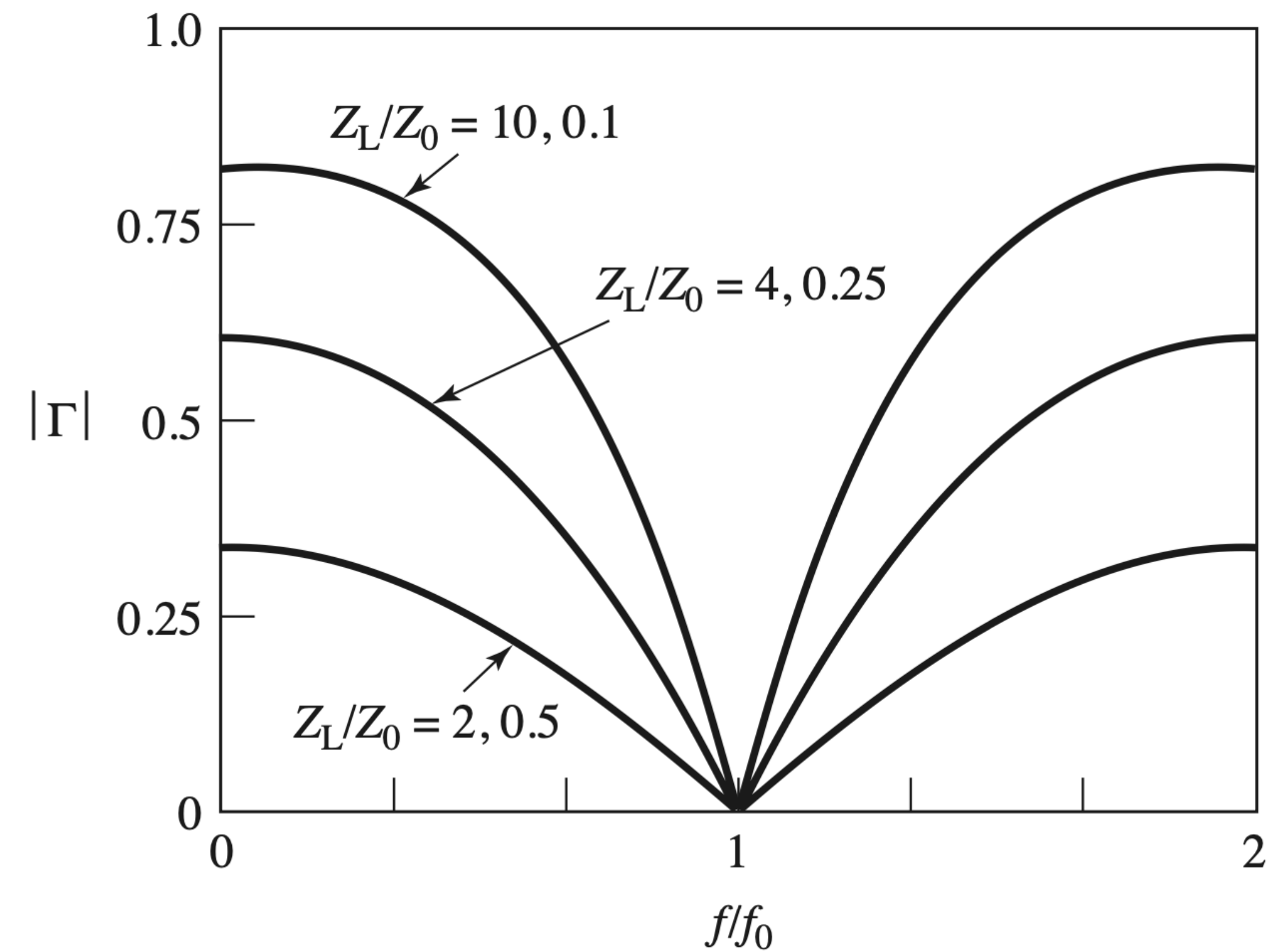


Reflection of a resonator: internal and external loss
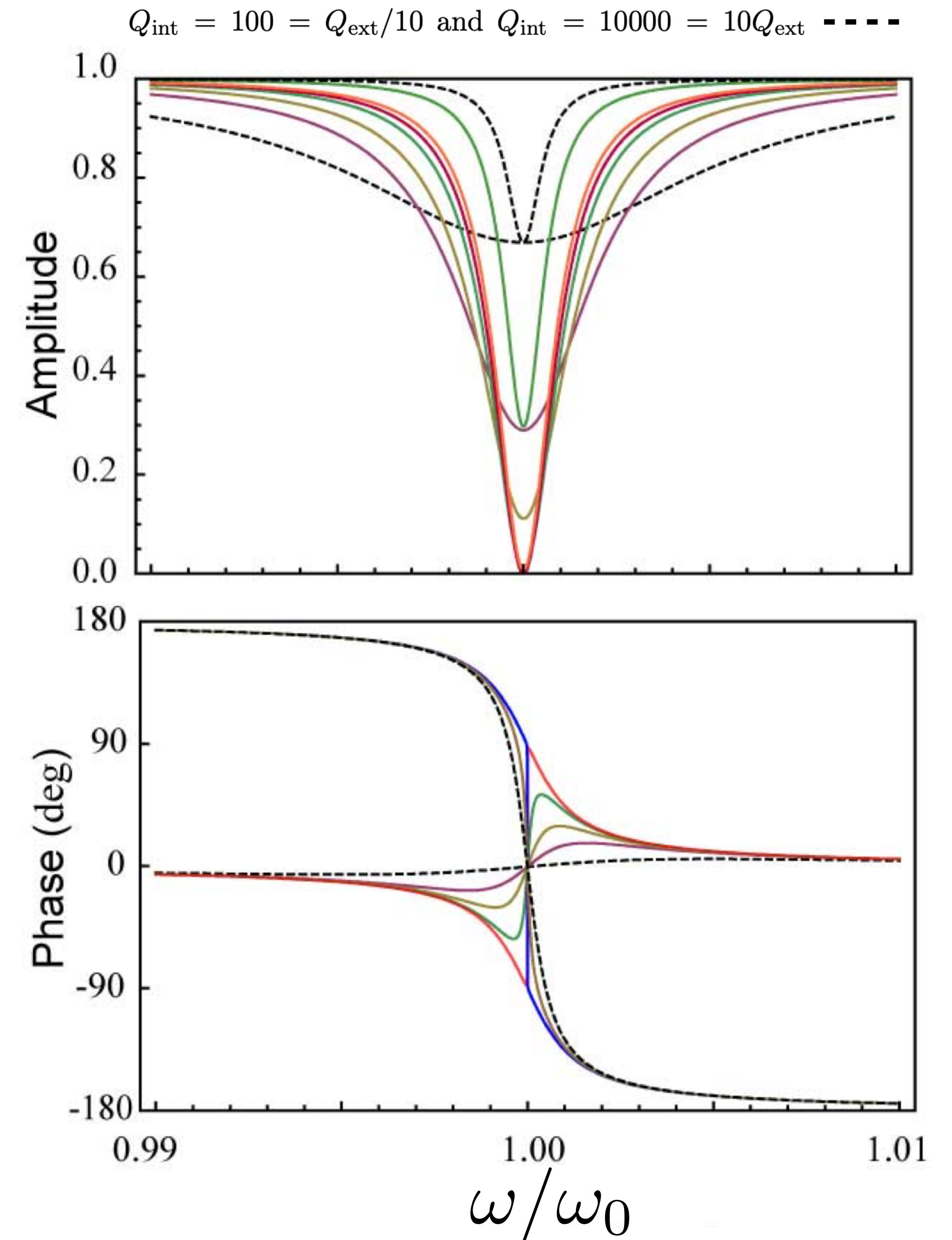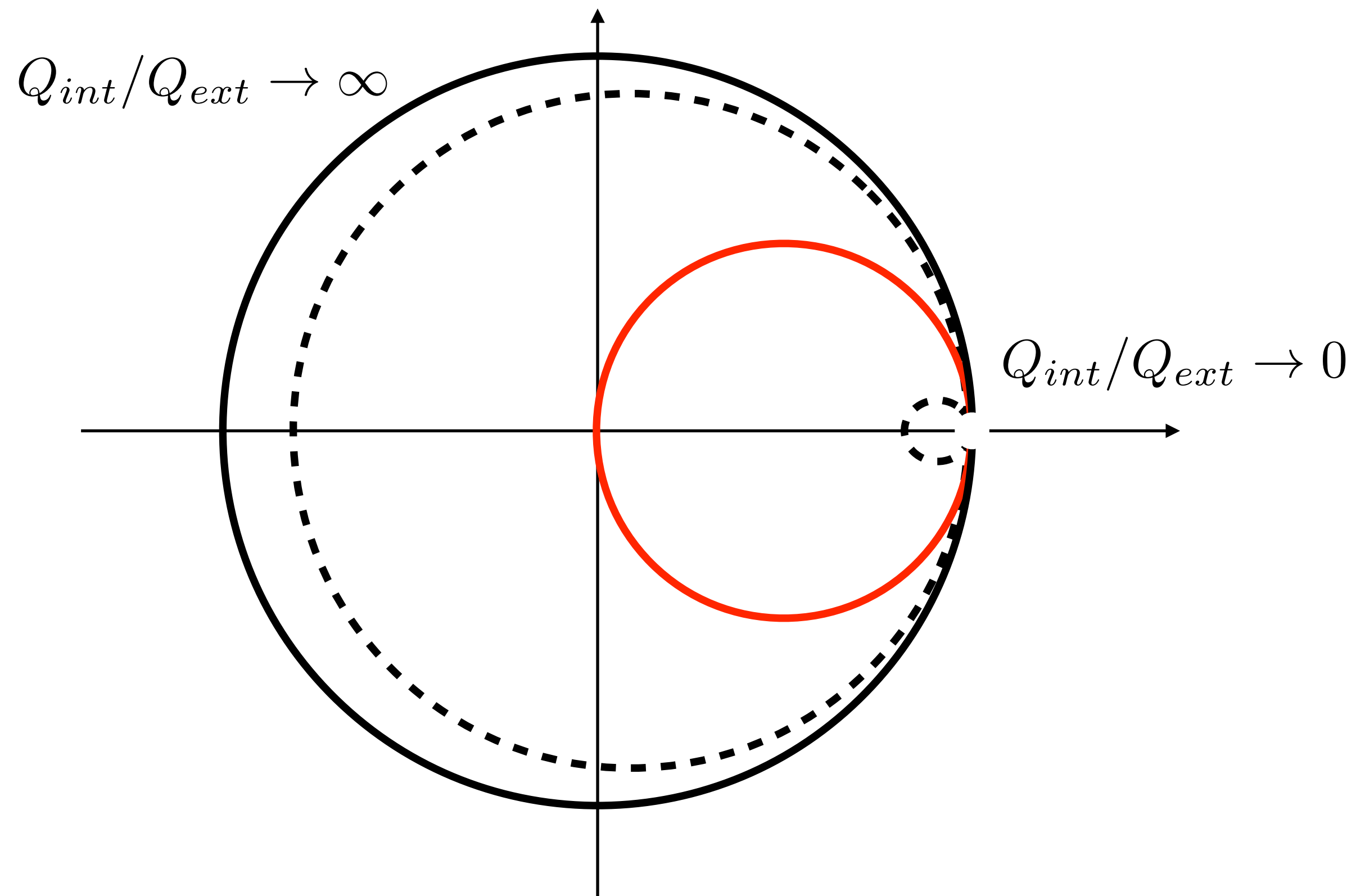
$$\Gamma(\omega, \omega_0) = \frac{2i\left(\frac{\omega - \omega_0}{\omega_0}\right) - Q_{\text{ext}}^{-1} + Q_{\text{int}}^{-1}}{2i\left(\frac{\omega - \omega_0}{\omega_0}\right) + Q_{\text{ext}}^{-1} + Q_{\text{int}}^{-1}}$$





TE/TM waveguides with a propagation cut-off


TE_{10}

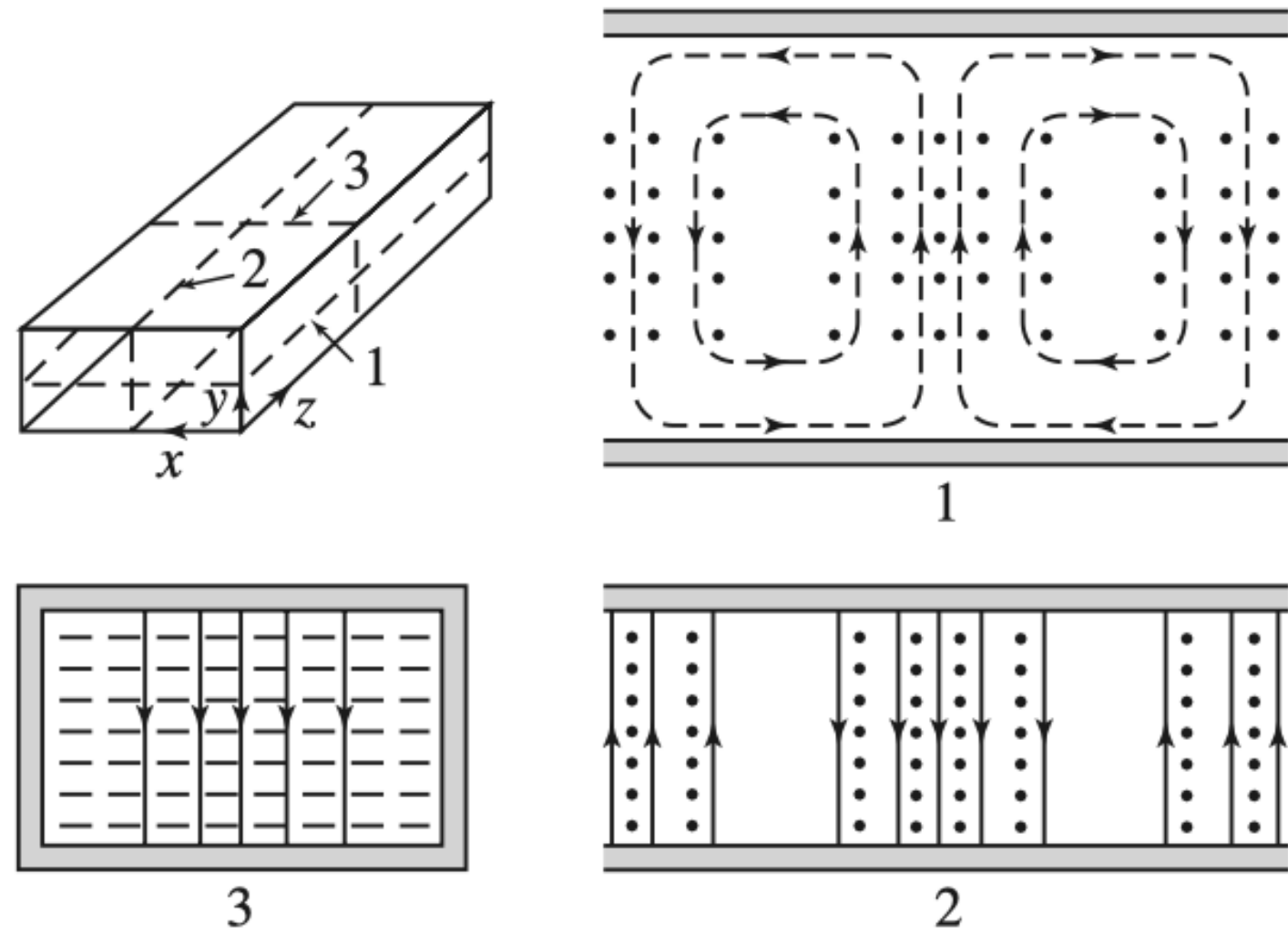

TE_{20}

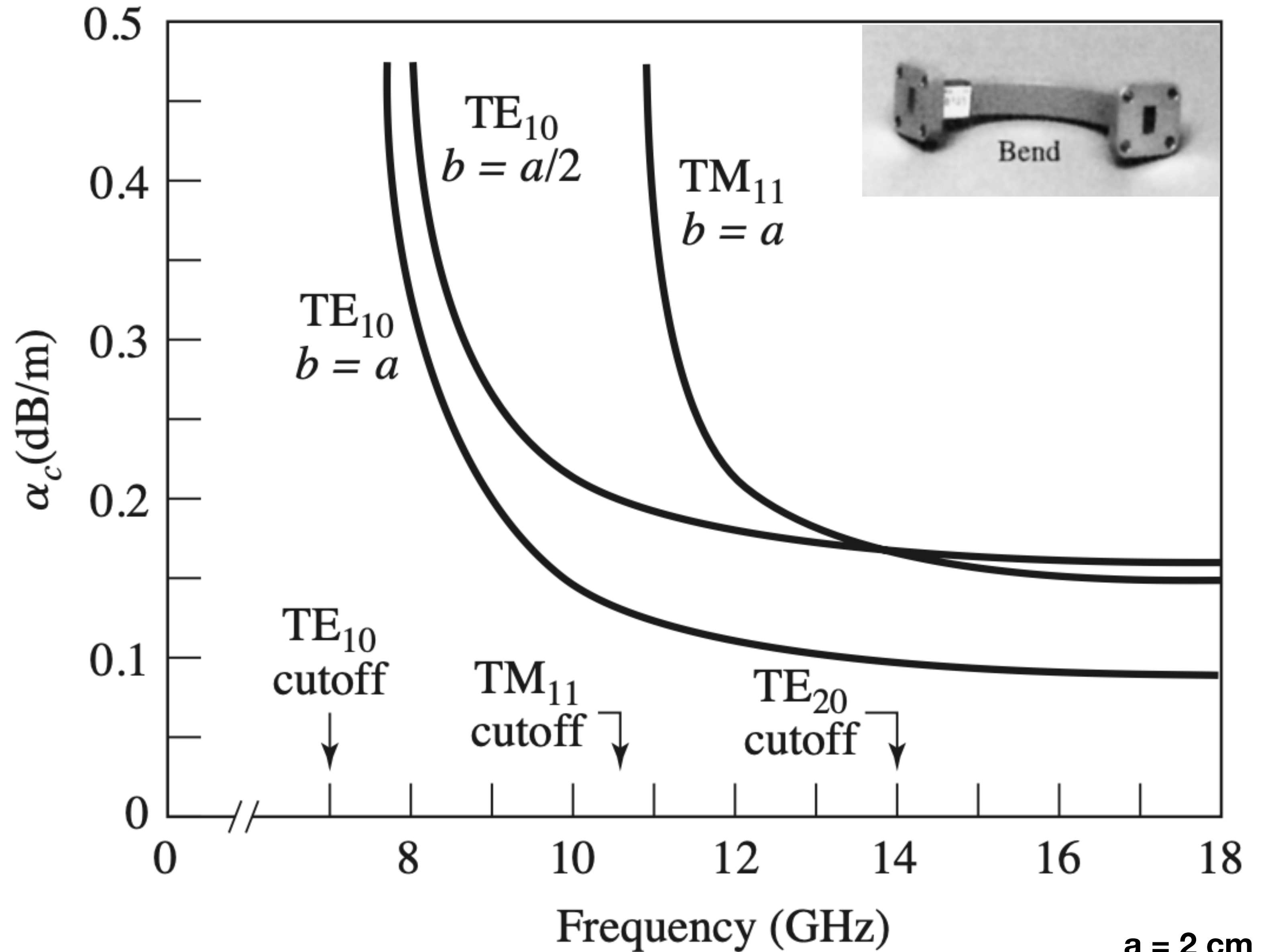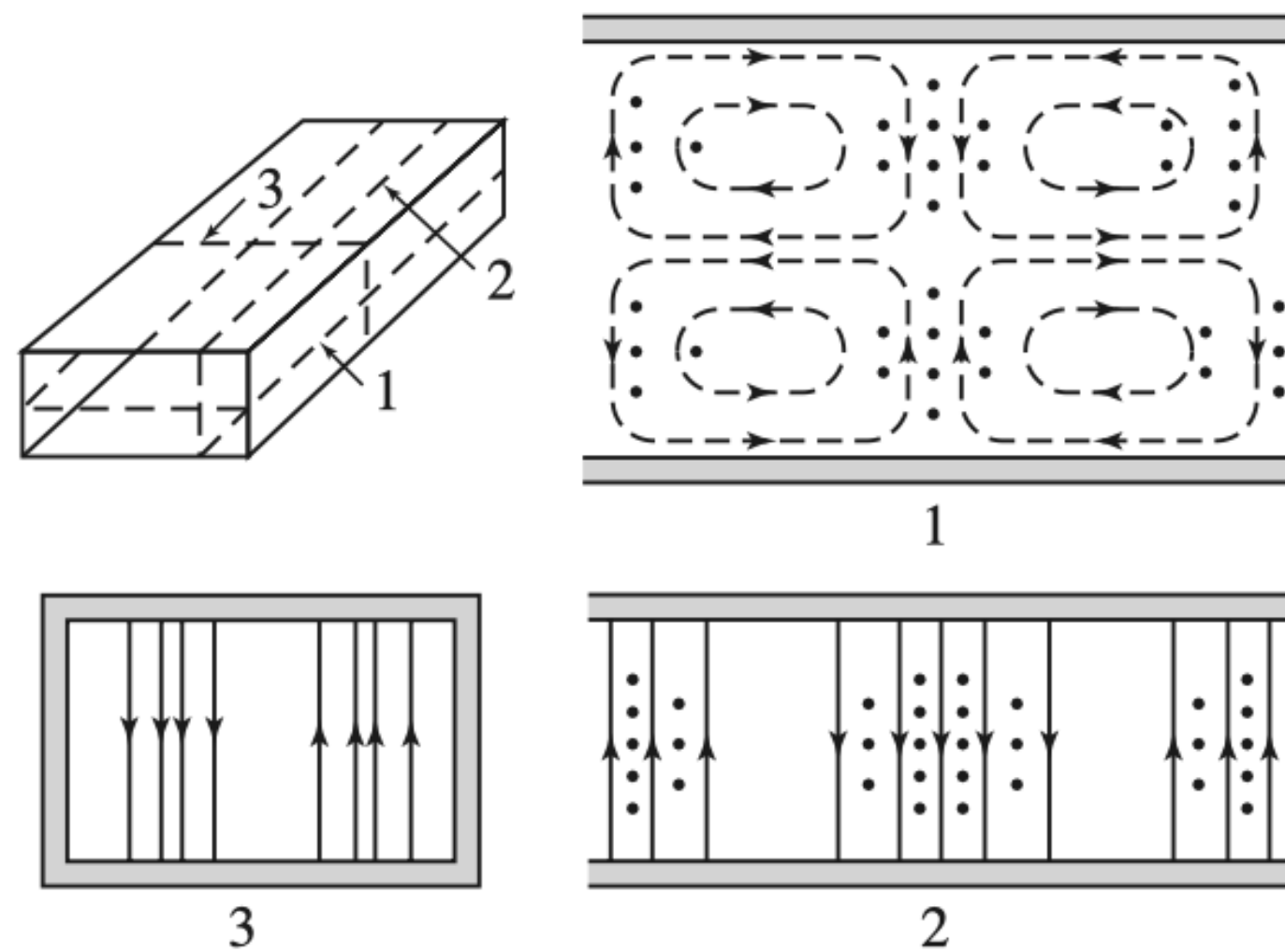

Microwave network analysis

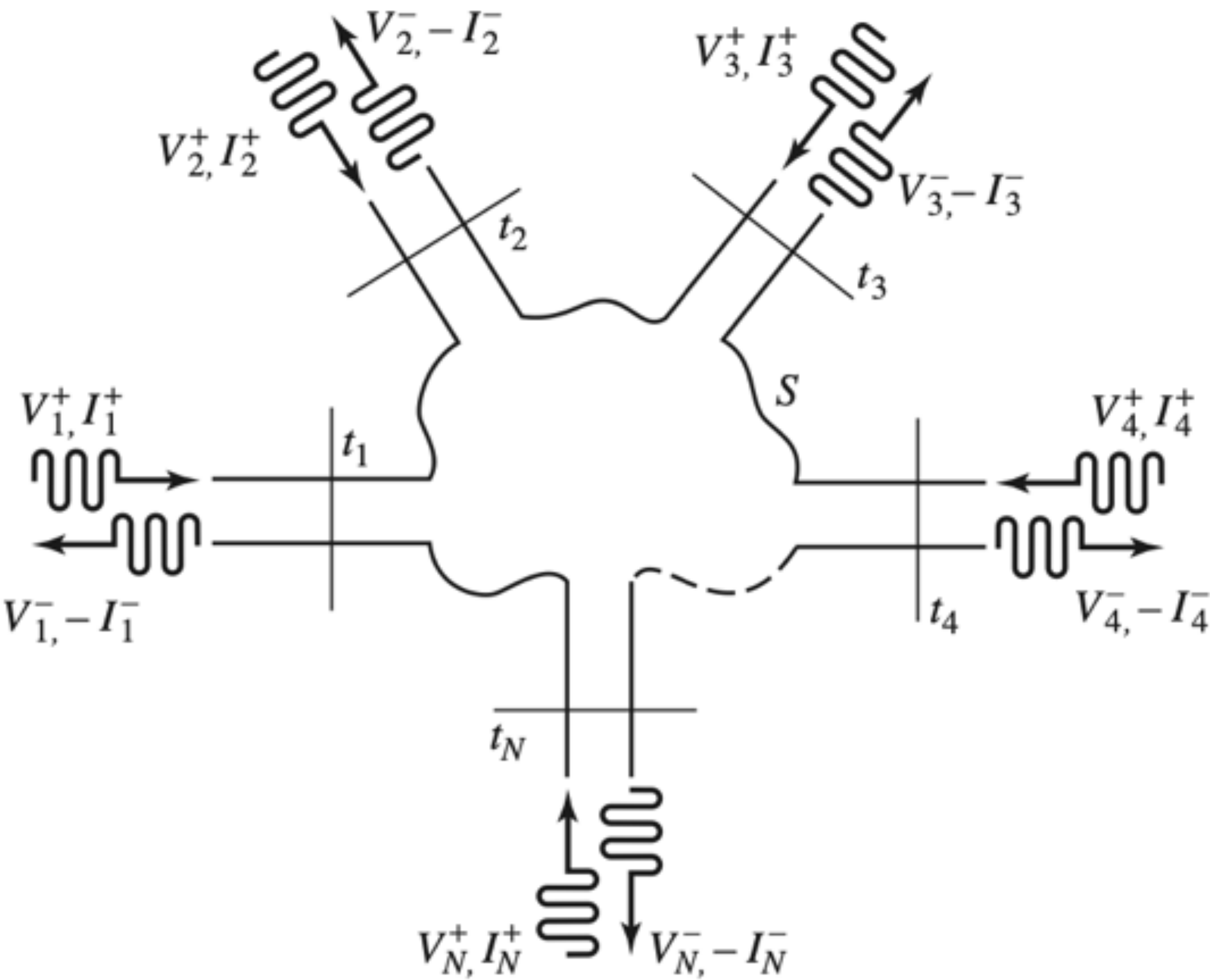

Z-matrix


$$\begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & \cdots & Z_{1N} \\ Z_{21} & & & \vdots \\ \vdots & & & \vdots \\ Z_{N1} & \cdots & \cdots & Z_{NN} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_N \end{bmatrix}$$

S-matrix


$$\begin{bmatrix} V_1^- \\ V_2^- \\ \vdots \\ V_N^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & \cdots & S_{1N} \\ S_{21} & & & \vdots \\ S_{N1} & \cdots & & S_{NN} \\ \vdots & & & \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \\ \vdots \\ V_N^+ \end{bmatrix}$$

$$\hat{S} = (\hat{Z} + Z_0 \hat{I})^{-1} (\hat{Z} - Z_0 \hat{I})$$

From T-matrix to S-matrix

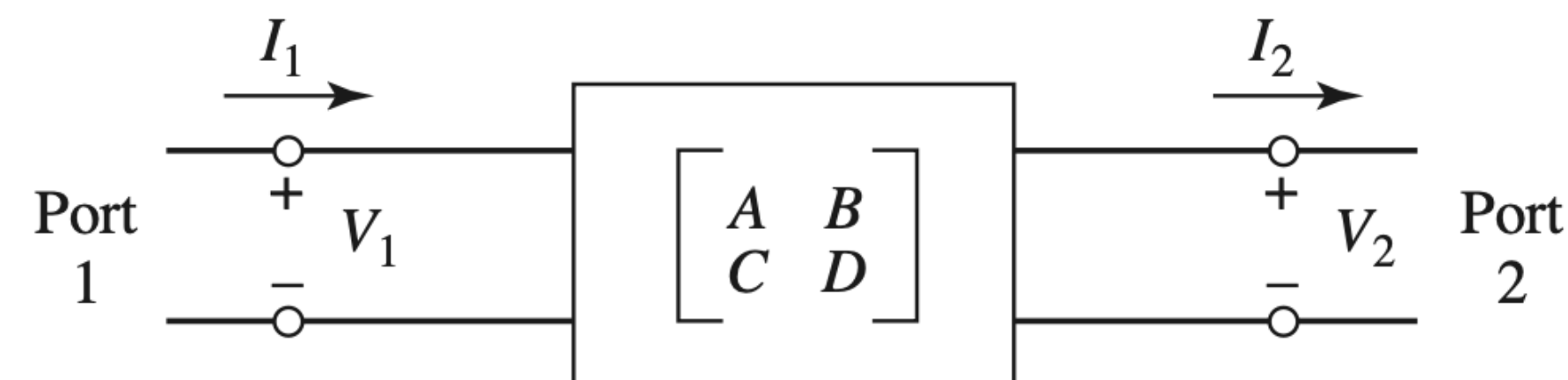

(a)

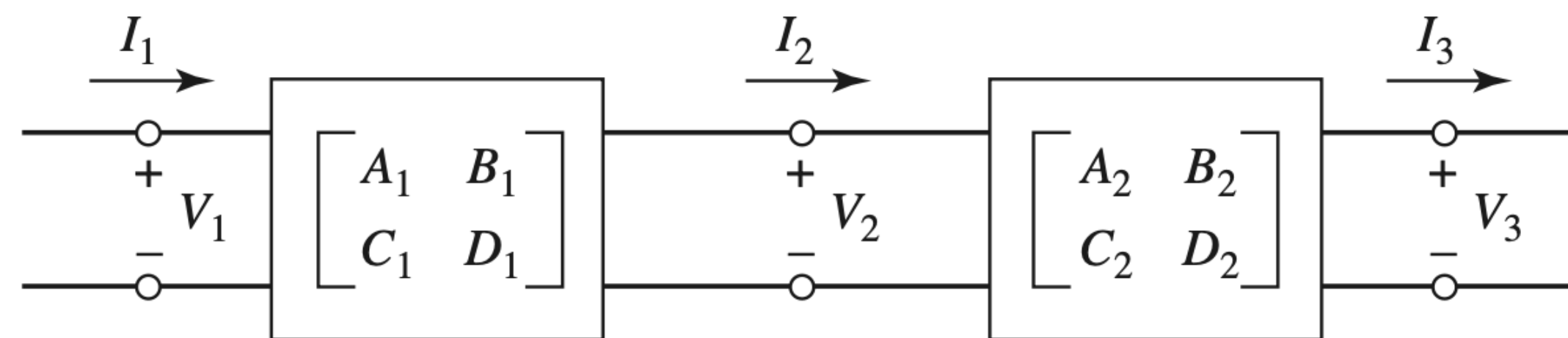

Circuit	ABCD Parameters	
	$A = 1$ $C = 0$	$B = Z$ $D = 1$
	$A = 1$ $C = Y$	$B = 0$ $D = 1$
	$A = \cos \beta \ell$ $C = jY_0 \sin \beta \ell$	$B = jZ_0 \sin \beta \ell$ $D = \cos \beta \ell$

S_{11}

S_{12}


S_{21}

S_{22}

$=$

$\frac{A + B/Z_0 - CZ_0 - D}{A + B/Z_0 + CZ_0 + D}$
 $\frac{2(AD - BC)}{A + B/Z_0 + CZ_0 + D}$
 $\frac{2}{A + B/Z_0 + CZ_0 + D}$
 $\frac{-A + B/Z_0 - CZ_0 + D}{A + B/Z_0 + CZ_0 + D}$


Arbitrary non-reciprocal 2-port circuit

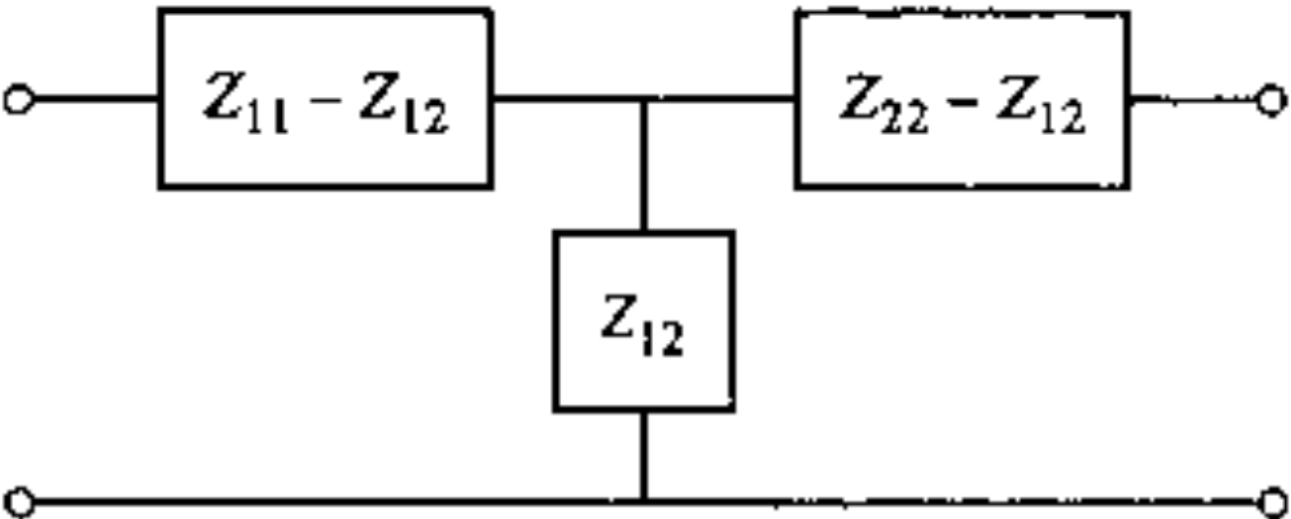

Three-port devices


$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{bmatrix}$$

**Lossless divider
(R,L)**

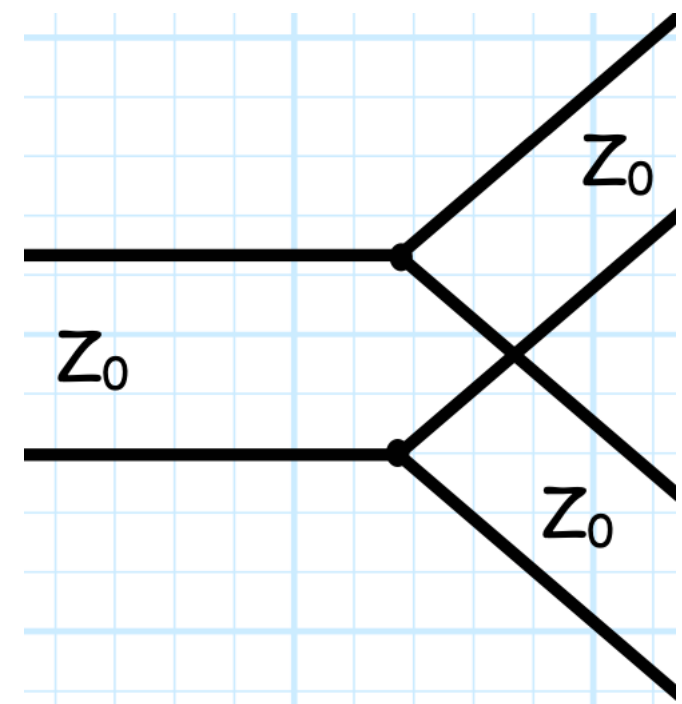

$$S = \begin{bmatrix} -1/3 & 2/3 & 2/3 \\ 2/3 & -1/3 & 2/3 \\ 2/3 & 2/3 & -1/3 \end{bmatrix}$$

**Resistive divider
(R,M)**

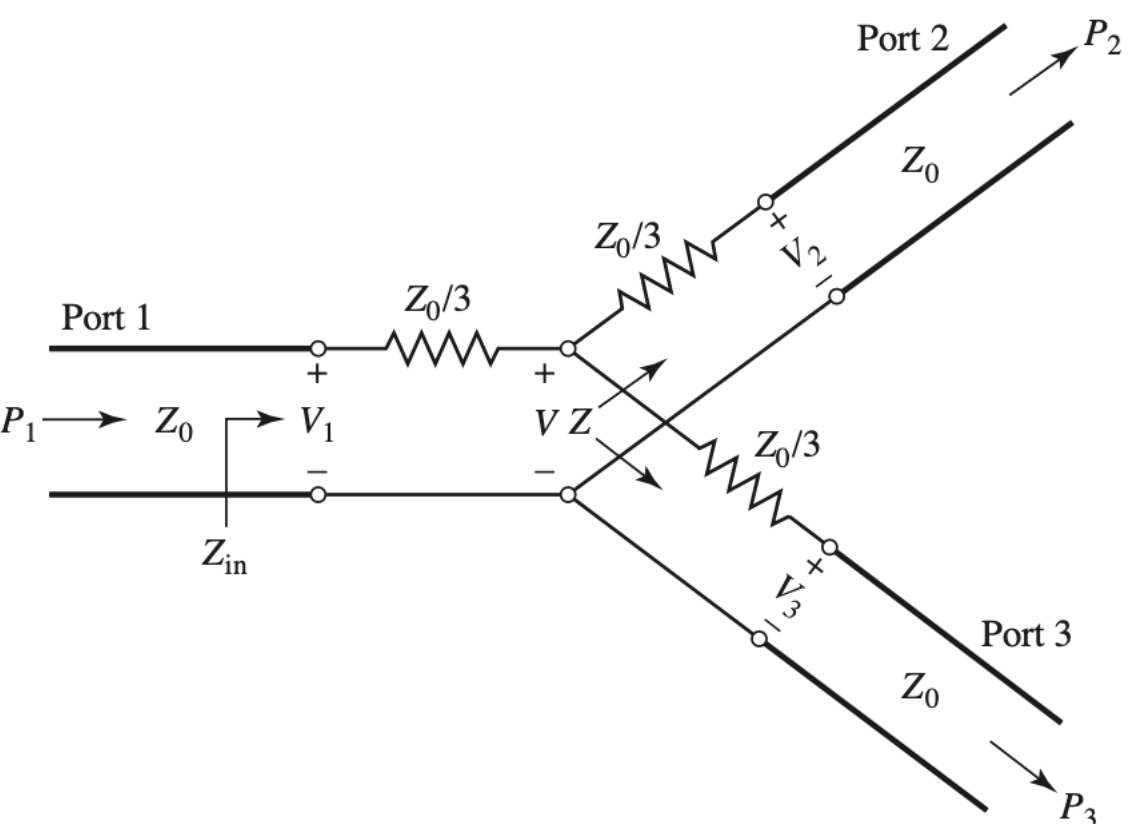

$$[S] = \frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$$


Matched $S_{nn} = 0$

Reciprocal $S = S^T$


Lossless $S^T S^* = I$

**Circulator
(M, L)**


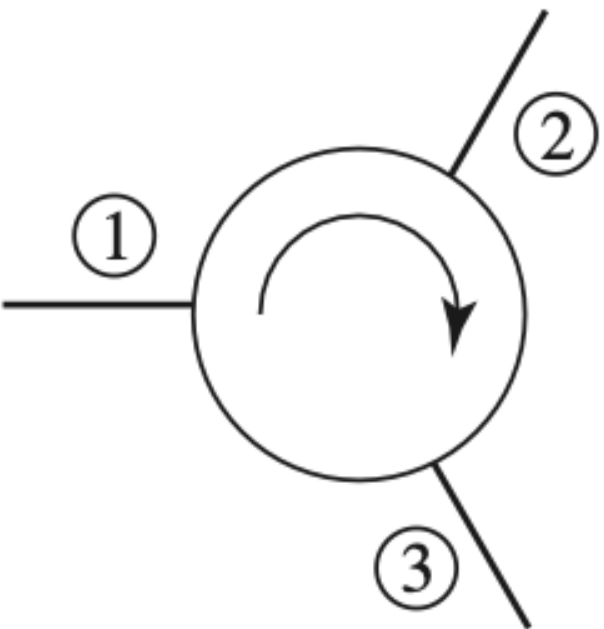
$$[S] = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$


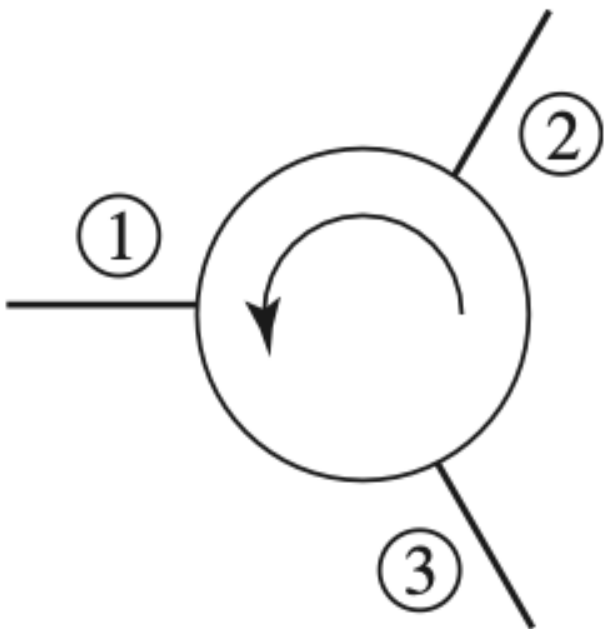
$$[S] = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \end{bmatrix}$$



Nyquist-Johnson noise

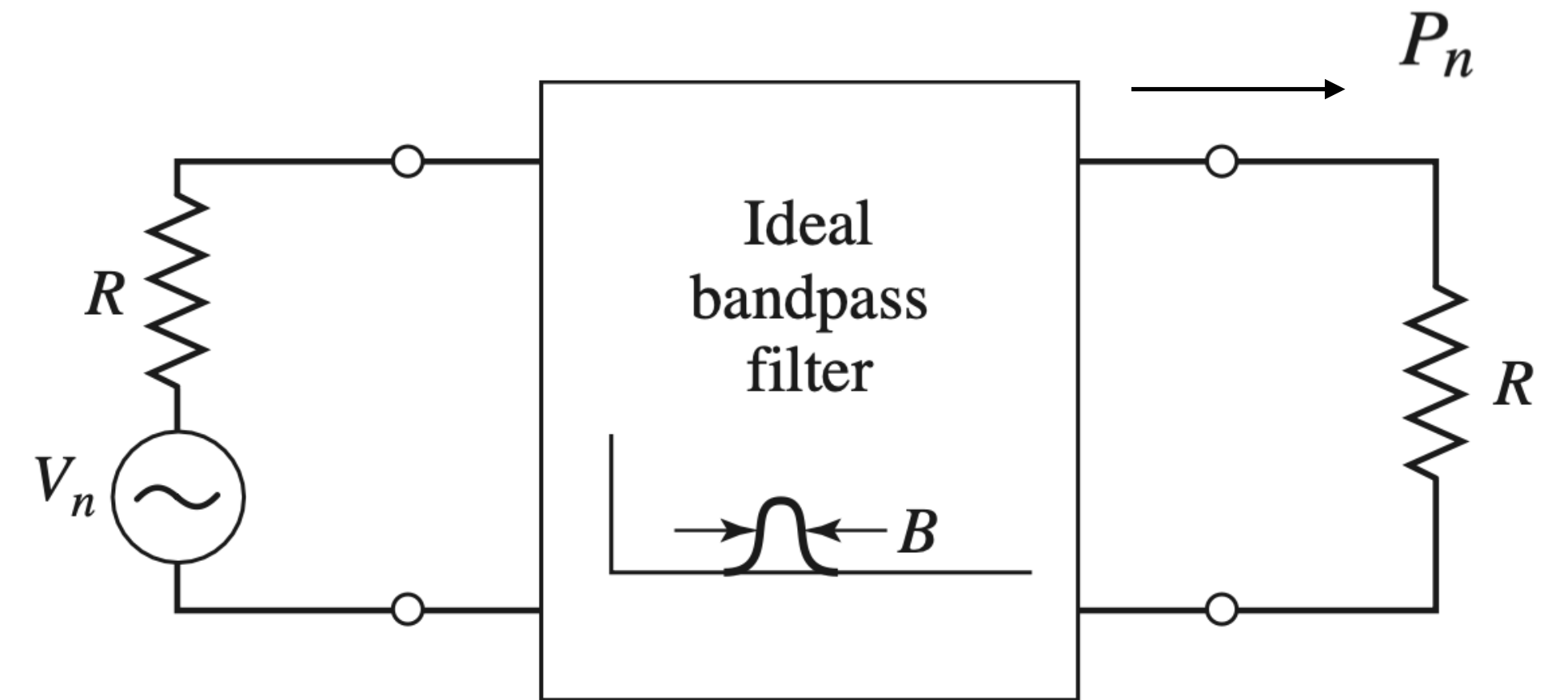
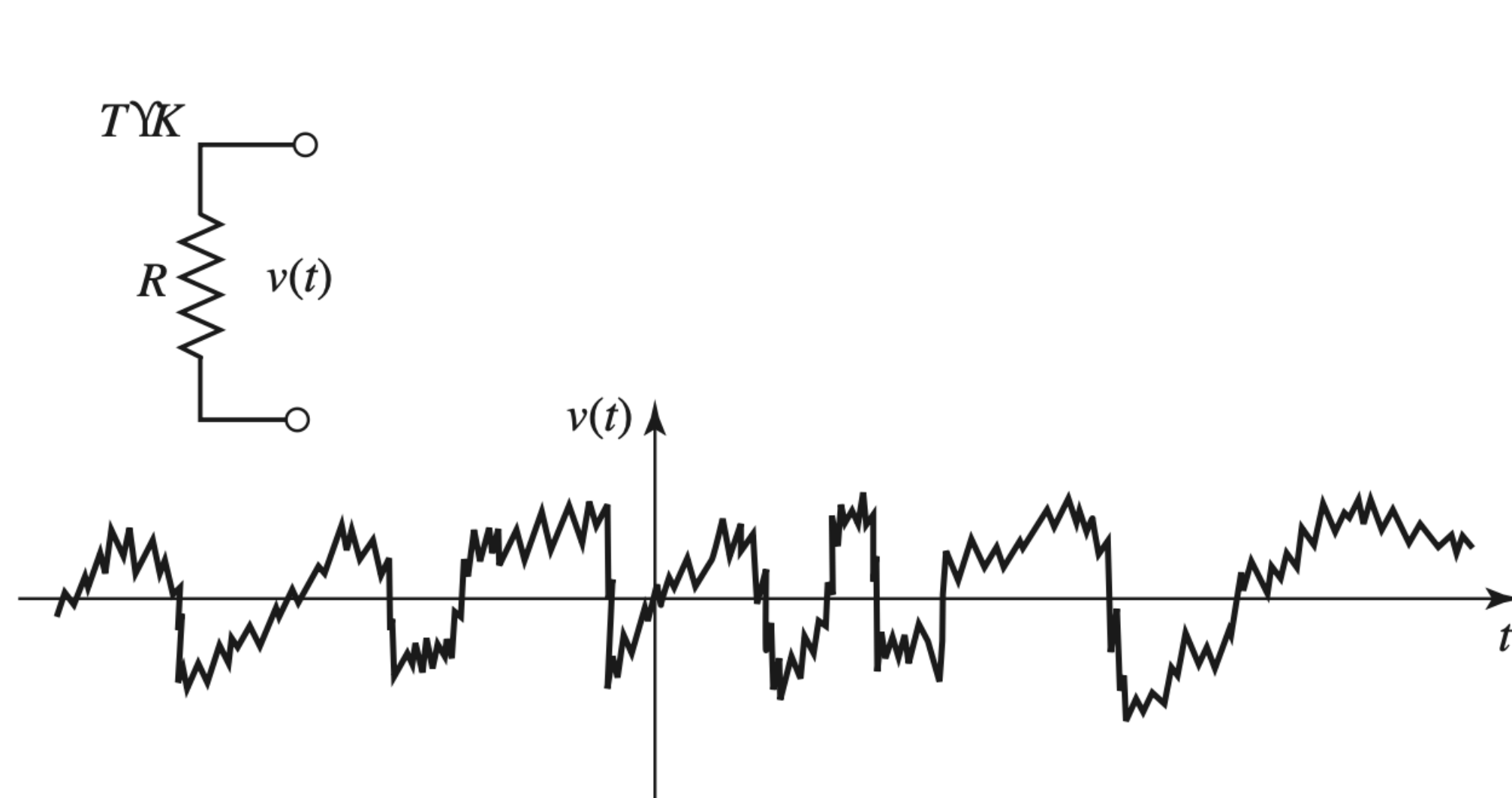


$$V_n = \sqrt{4kTBR}$$

$$P_n = \left(\frac{V_n}{2R} \right)^2 R = \frac{V_n^2}{4R} = kTB$$


link to
stat physics

Effective noise
temperature

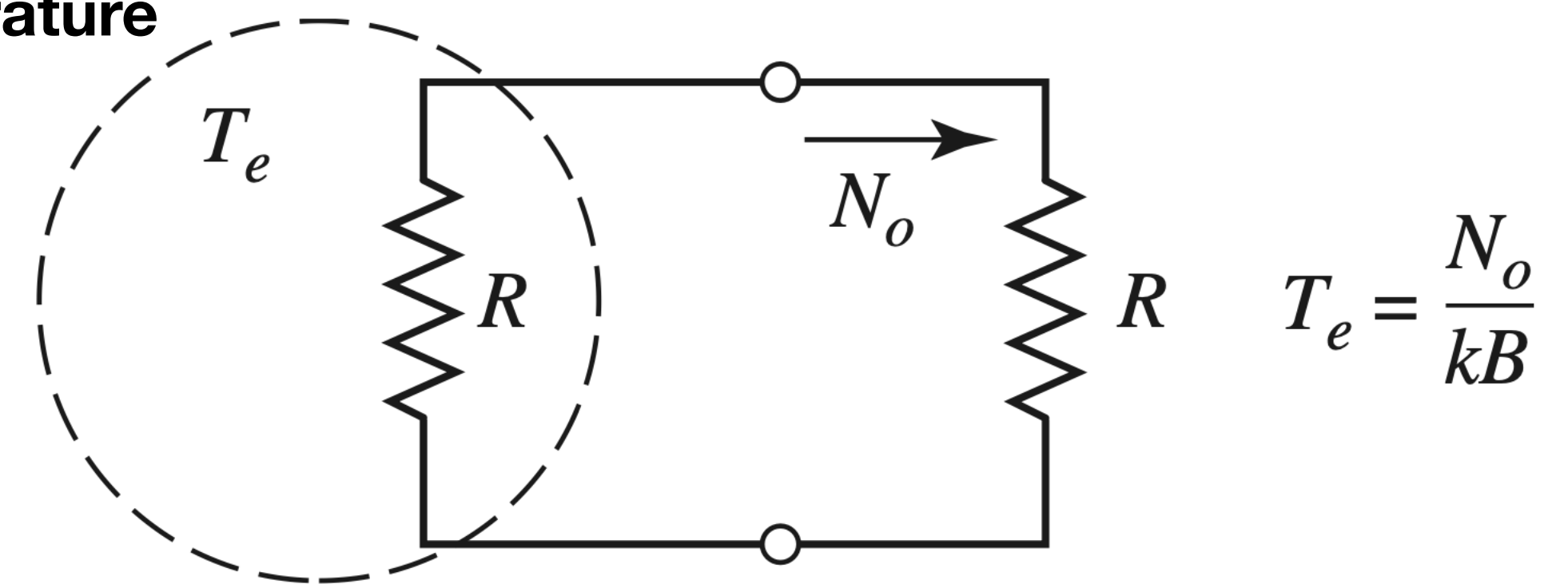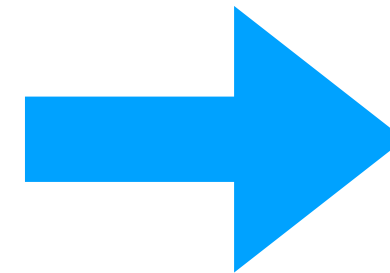


Cascade
$$T_{\text{cas}} = T_{e1} + \frac{T_{e2}}{G_1} + \frac{T_{e3}}{G_1 G_2} + \dots$$

gain of first stage

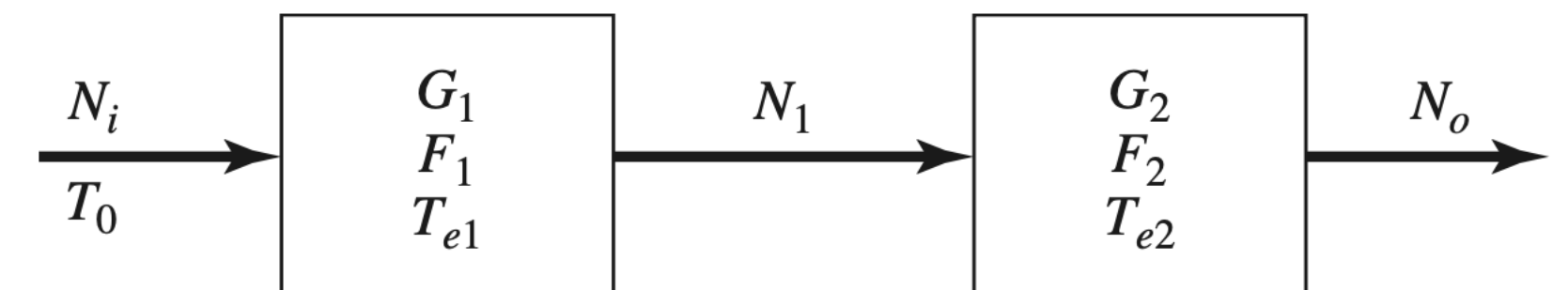


(parametric) Amplification

M. Devoret lecture @ CdF

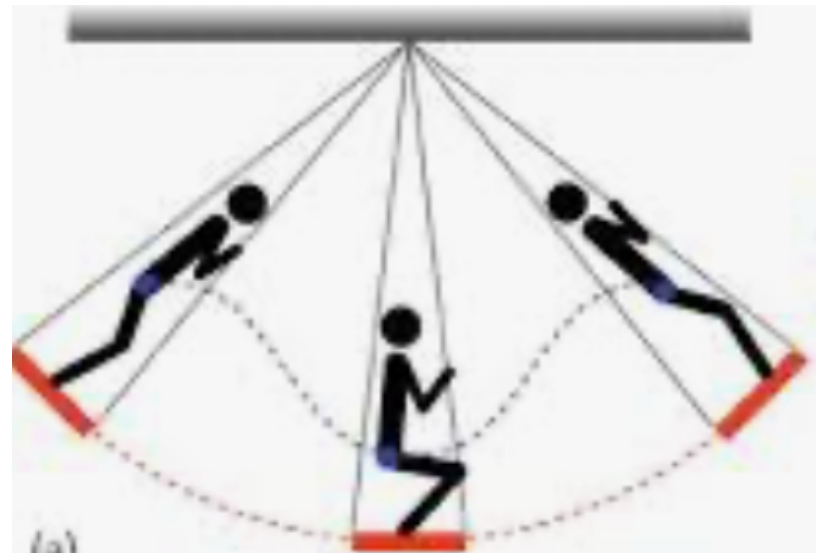


Amplifier
=
negative
load resistance...

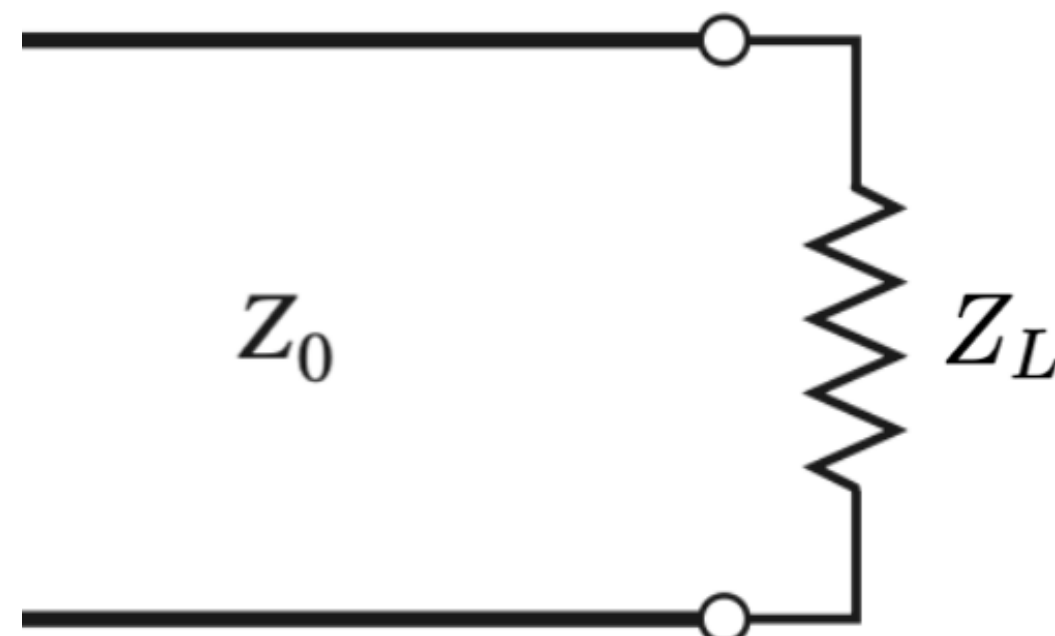

$$|\Gamma| > 1$$

SCATTERING MATRIX OF DPA FOR ARBITRARY ω

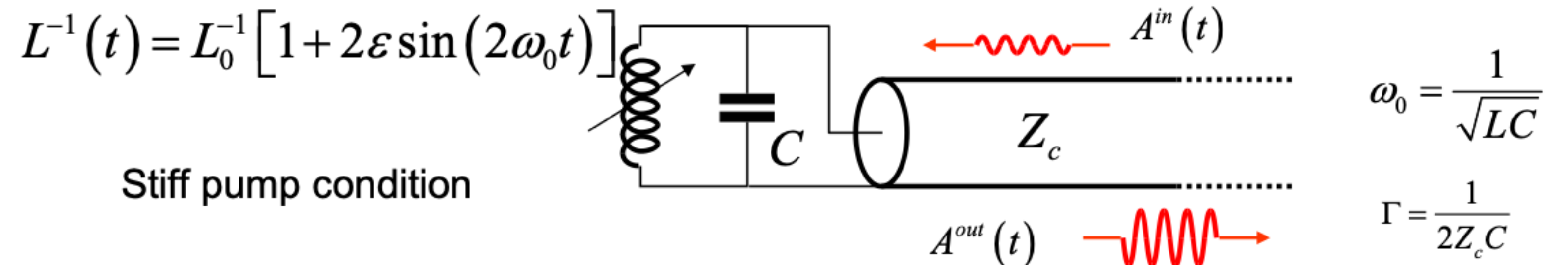

$$\ddot{\Phi} + 2\Gamma \dot{\Phi} + \omega_0^2 \Phi - i\omega_0^2 \varepsilon \Phi (e^{2i\omega_0 t} - e^{-2i\omega_0 t}) = 4\Gamma V^{in}(t) \quad V^{out}(t) = \dot{\Phi} - V^{in}(t)$$

Harmonic balance + RWA $\Rightarrow$

$$i\omega_0 \left[\frac{(\omega_0 - \omega)}{i\Gamma} - 1 \right] \Phi[\omega] - i \frac{\omega_0^2 \varepsilon}{2\Gamma} \Phi[\omega - 2\omega_0] = 2V^{in}[\omega]$$

After a few steps:

$$A = V/\sqrt{Z_c}$$

$$\begin{bmatrix} A^{out}[+\omega_S] \\ A^{out}[-\omega_S] \\ A^{out}[+\omega_I] \\ A^{out}[-\omega_I] \end{bmatrix} = \begin{bmatrix} r & 0 & 0 & s \\ 0 & r^* & s^* & 0 \\ 0 & s^* & r^* & 0 \\ s & 0 & 0 & r \end{bmatrix} \begin{bmatrix} A^{in}[+\omega_S] \\ A^{in}[-\omega_S] \\ A^{in}[+\omega_I] \\ A^{in}[-\omega_I] \end{bmatrix}$$

$$r = \frac{1 + \mathcal{G}^2 + \zeta^2}{(1 - i\mathcal{G})^2 - \zeta^2}$$



$$s = \frac{2\zeta}{(1 - i\mathcal{G})^2 - \zeta^2}$$

$$\zeta = \varepsilon \frac{\omega_0}{2\Gamma} < 1$$

SYMPLECTICITY: $\begin{cases} |r|^2 - |s|^2 = 1 \\ rs^* - r^*s = 0 \end{cases}$

$$\mathcal{G} = \tan \theta = \frac{\omega_S - \omega_0}{\Gamma}$$

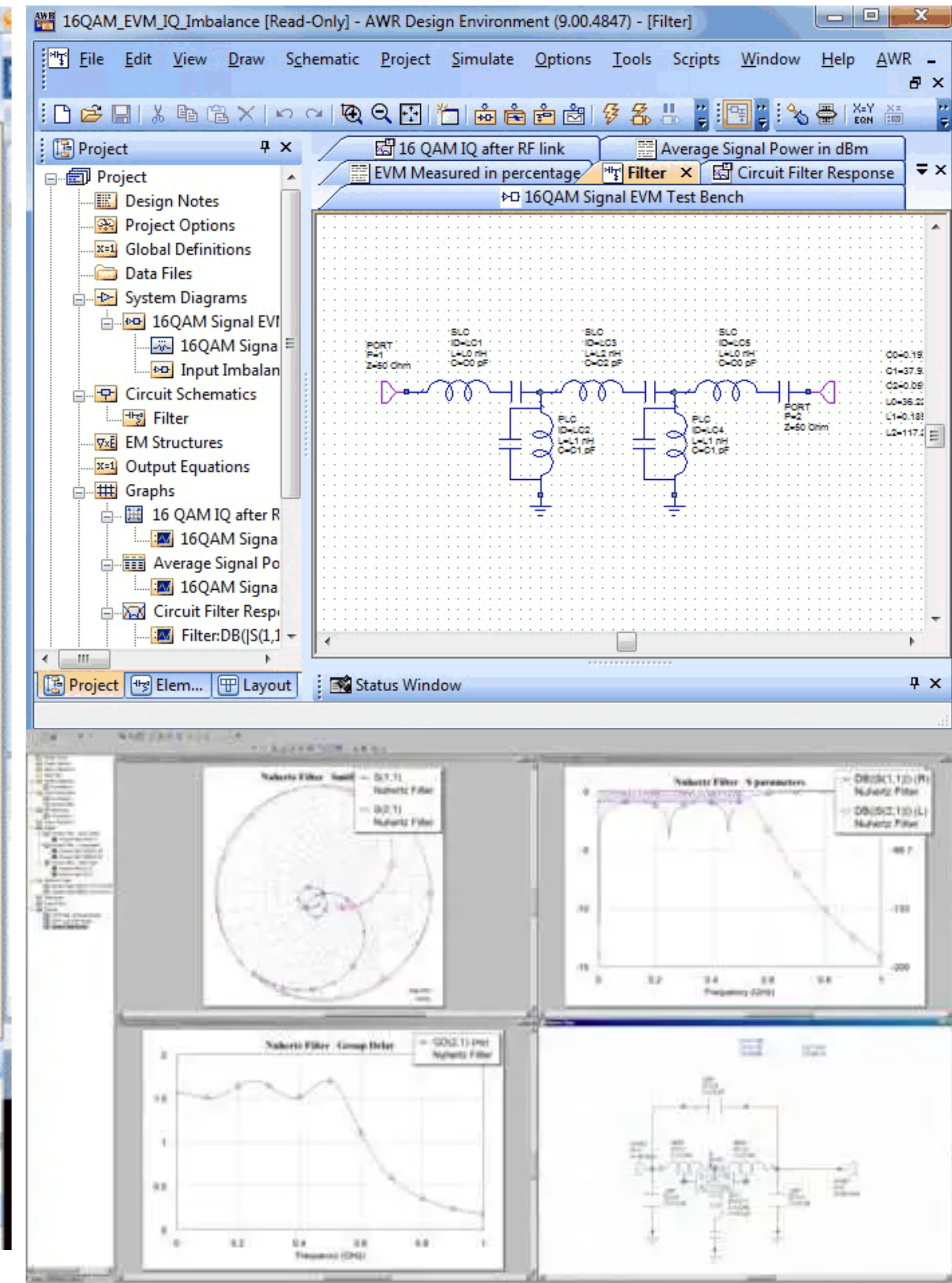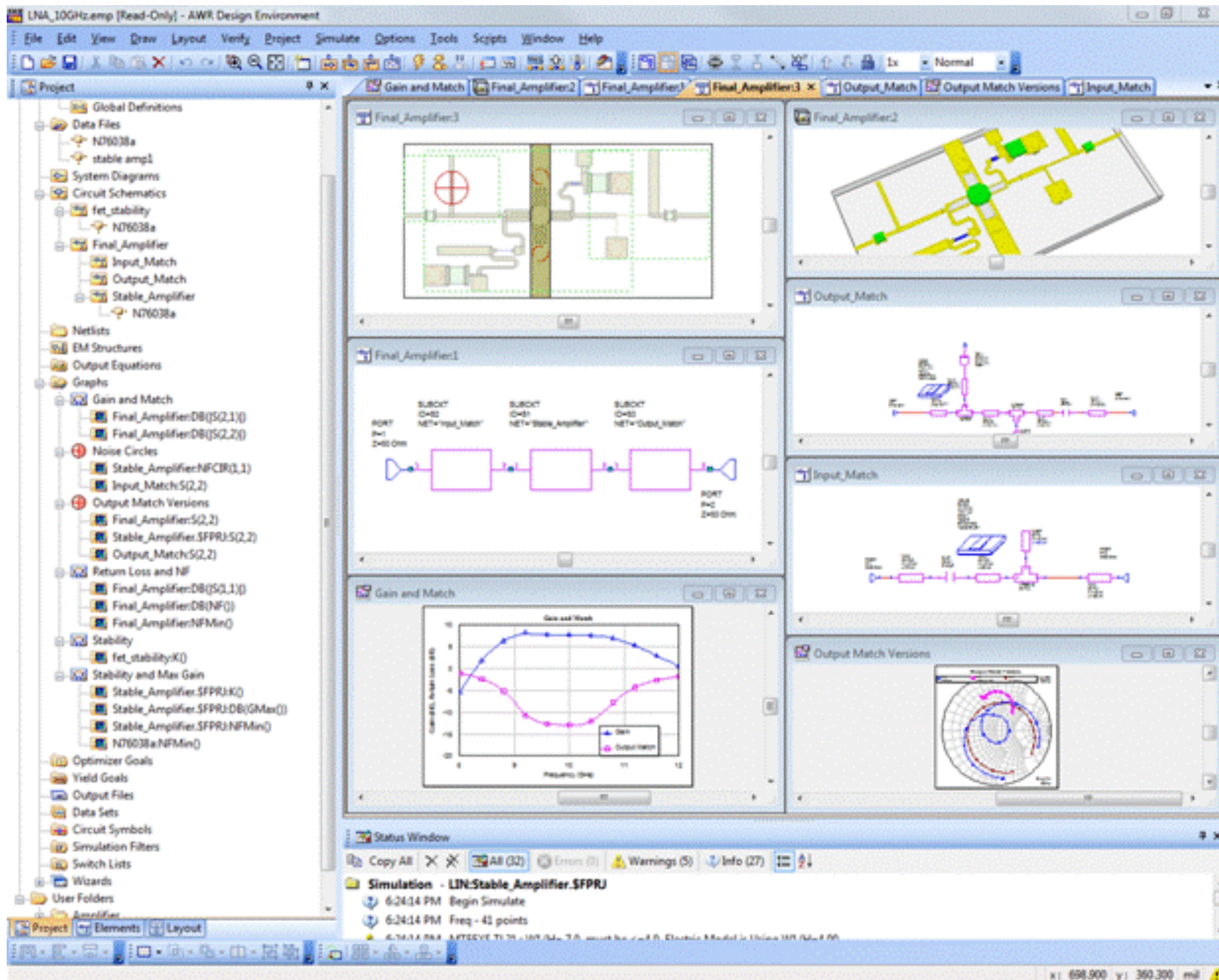Microwave office suite for lumped-element simulations



HFSS suite for distributed systems simulations


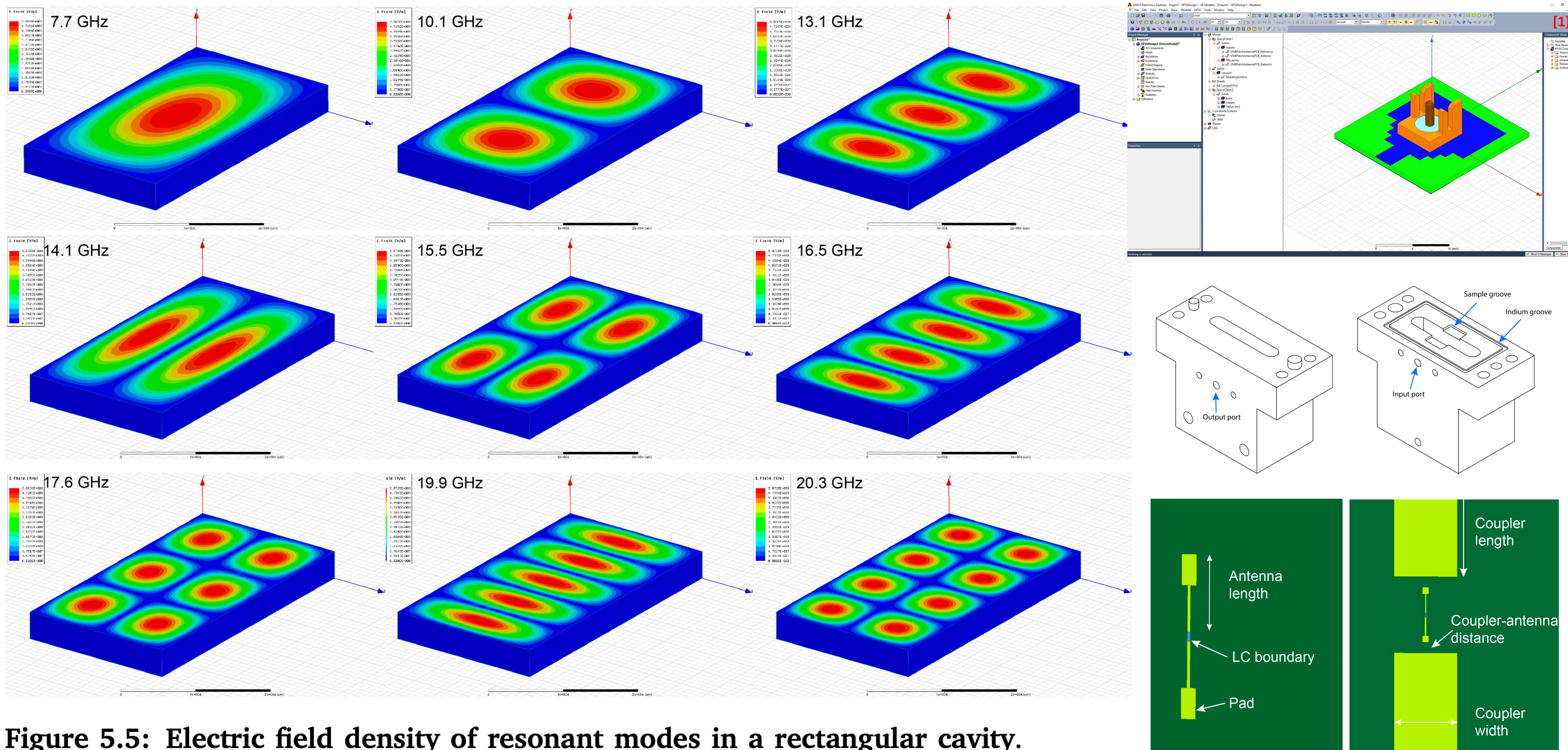


Figure 5.5: Electric field density of resonant modes in a rectangular cavity.




Microwave engineering in physics 2025: what we did not cover

Non-reciprocal devices
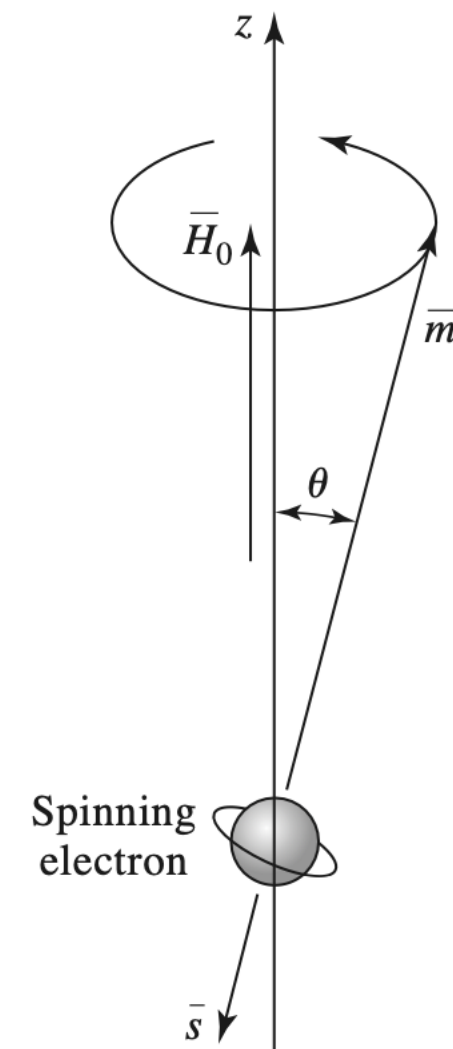
$$\begin{bmatrix} B_\rho \\ B_\phi \\ B_z \end{bmatrix} = [\mu] \begin{bmatrix} H_\rho \\ H_\phi \\ H_z \end{bmatrix}$$



Larmor precession
of magnetization

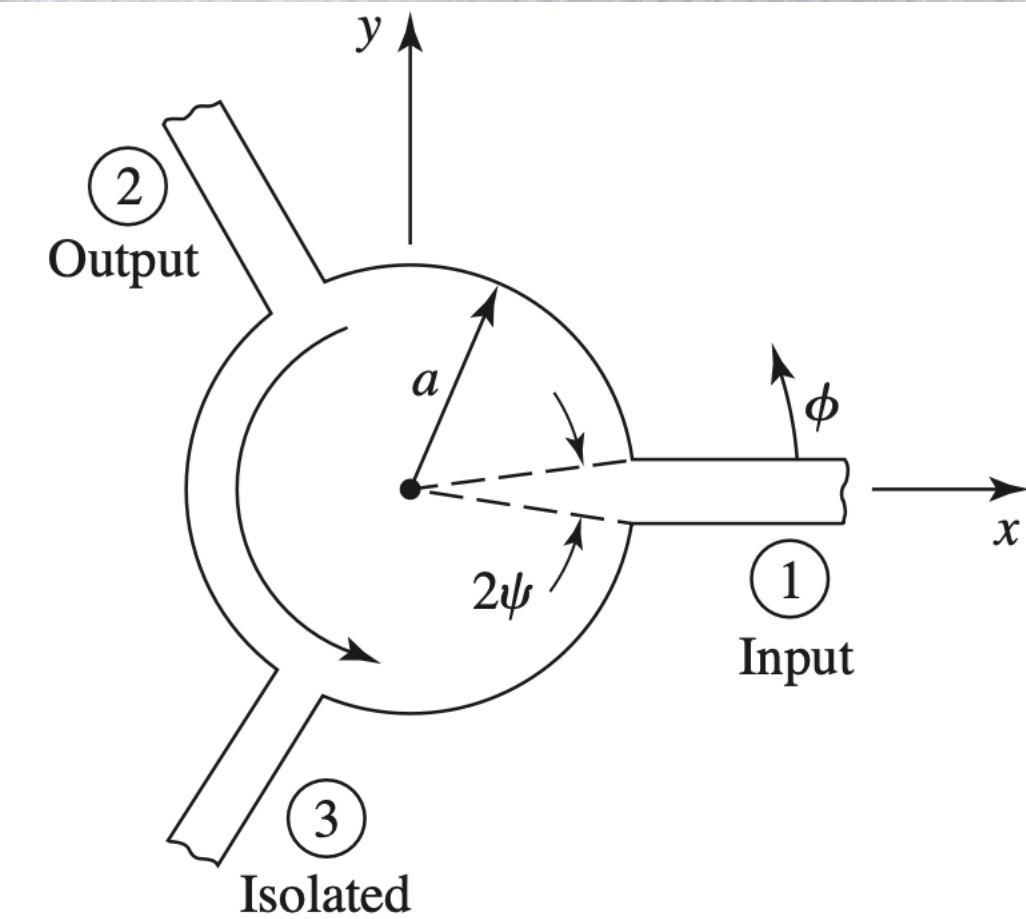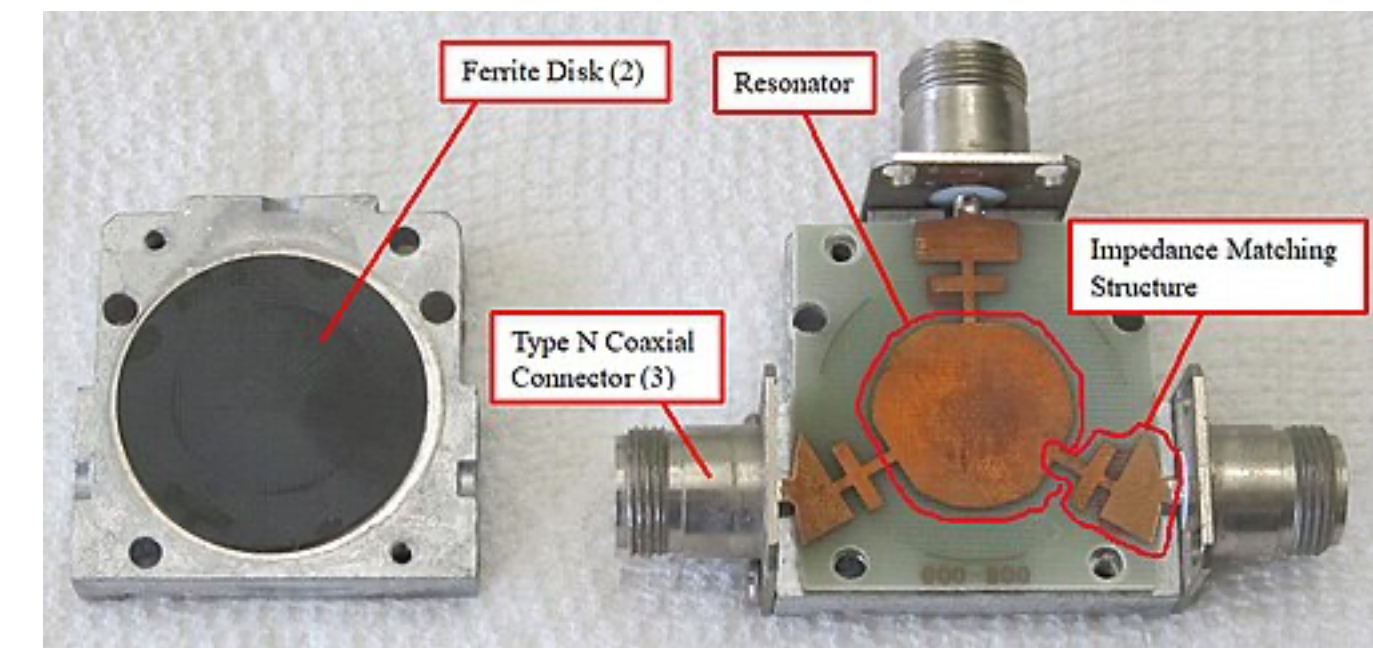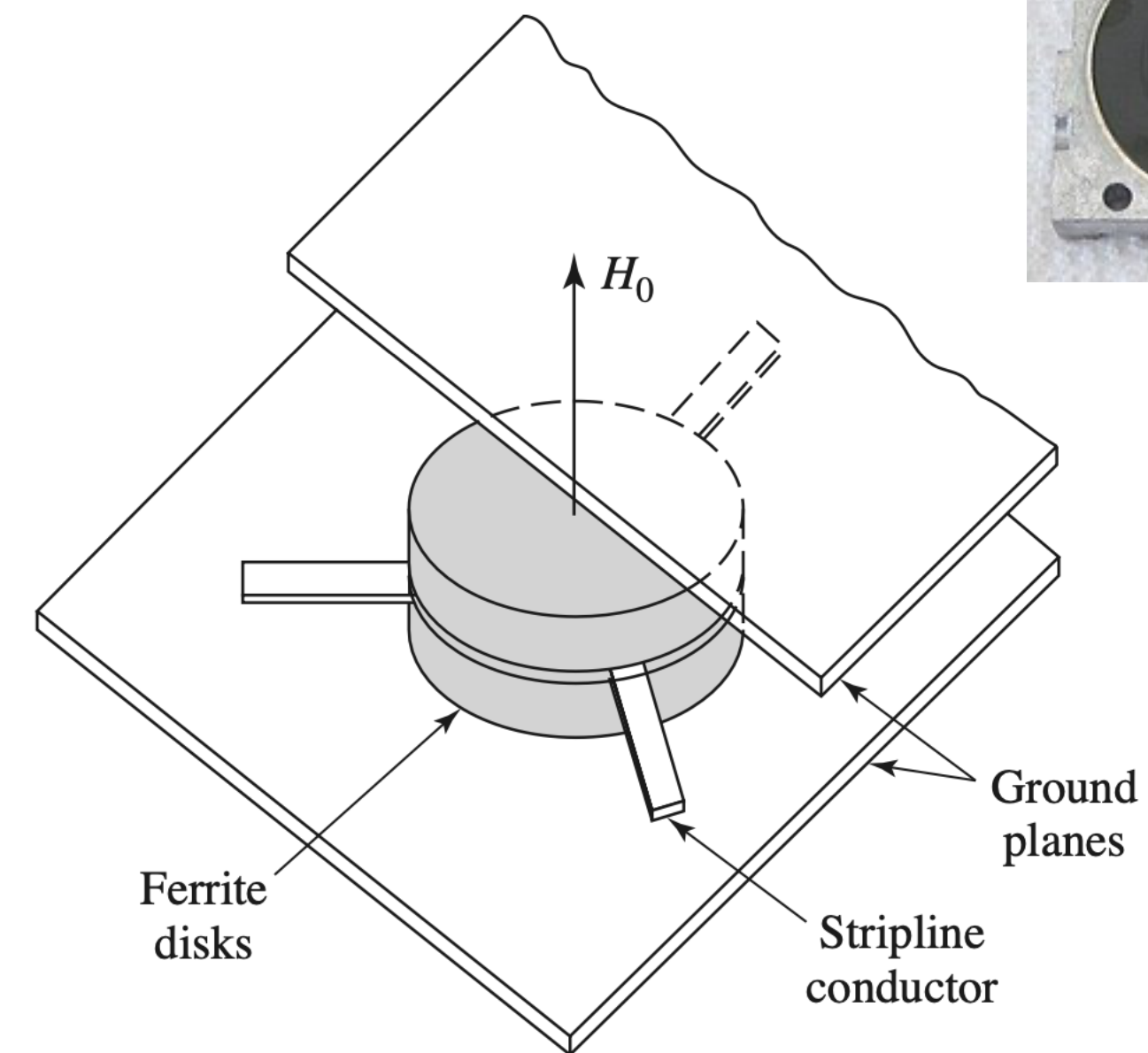


$$[\mu] = \mu_0([U] + [\chi]) = \begin{bmatrix} \mu & j\kappa & 0 \\ -j\kappa & \mu & 0 \\ 0 & 0 & \mu_0 \end{bmatrix} \text{ non-reciprocity}$$

$$\mu = \mu_0(1 + \chi_{xx}) = \mu_0(1 + \chi_{yy}) = \mu_0 \left(1 + \frac{\omega_0 \omega_m}{\omega_0^2 - \omega^2} \right)$$


$$\kappa = -j\mu_0\chi_{xy} = j\mu_0\chi_{yx} = \mu_0 \frac{\omega\omega_m}{\omega_0^2 - \omega^2}$$

Larmor frequency



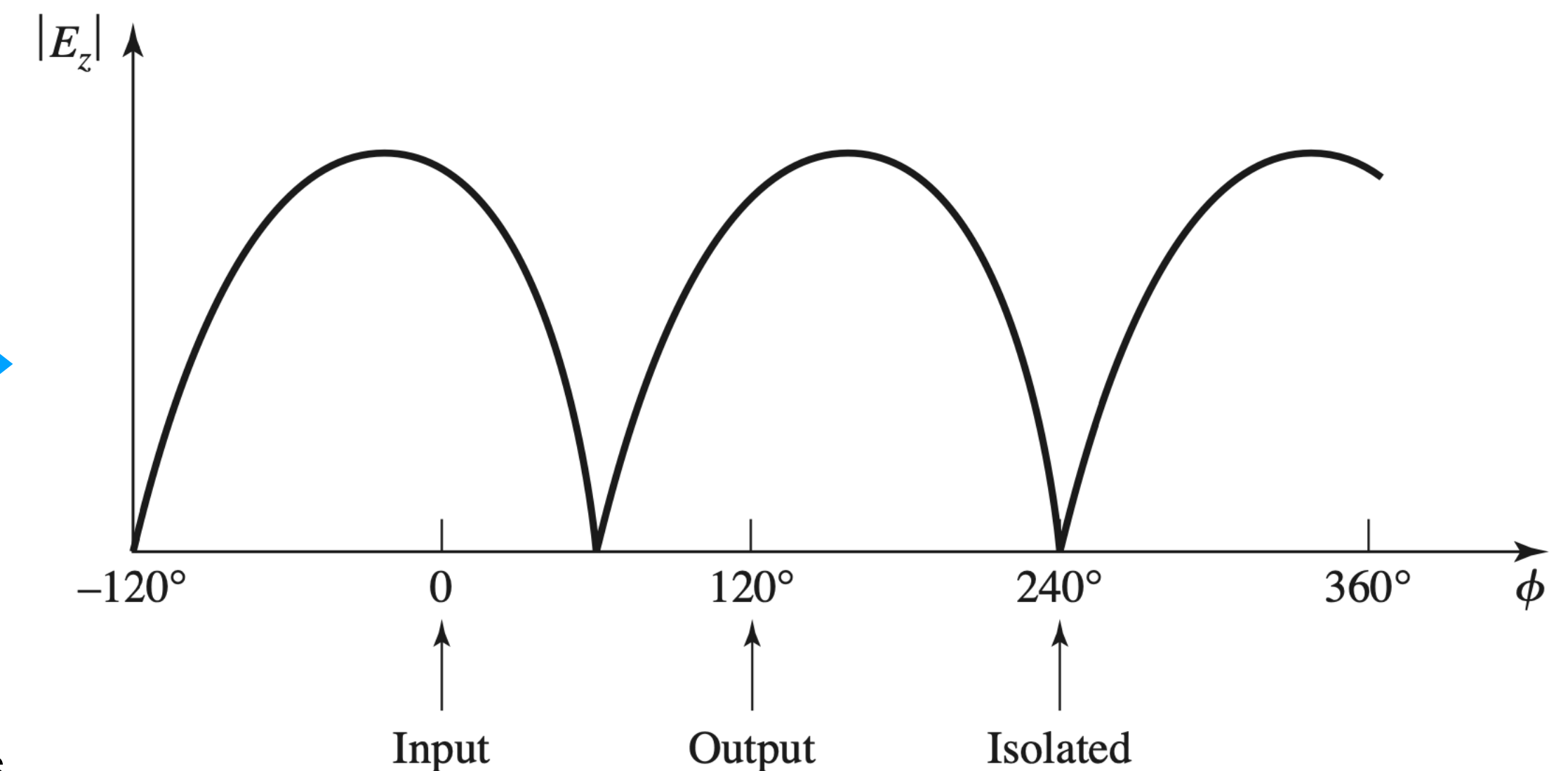
Sets the difference between clockwise and counterclockwise waves



Hybrid couplers

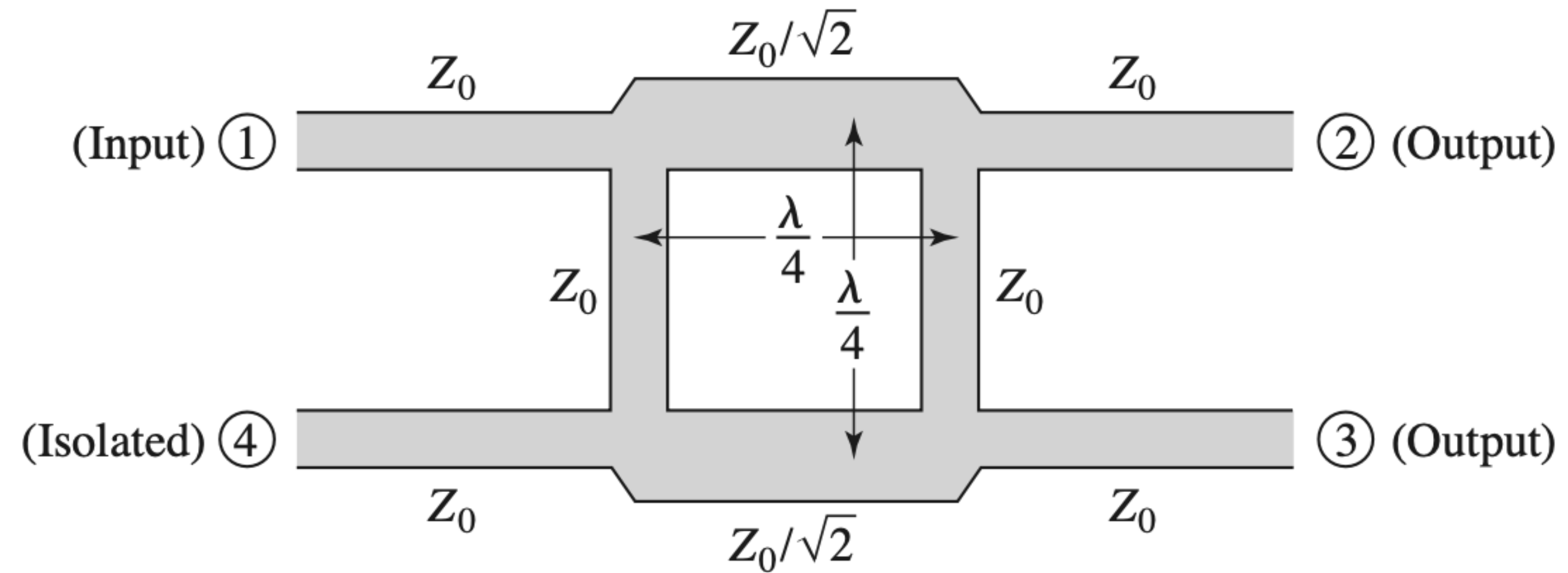


Analogue of optical beam-splitters

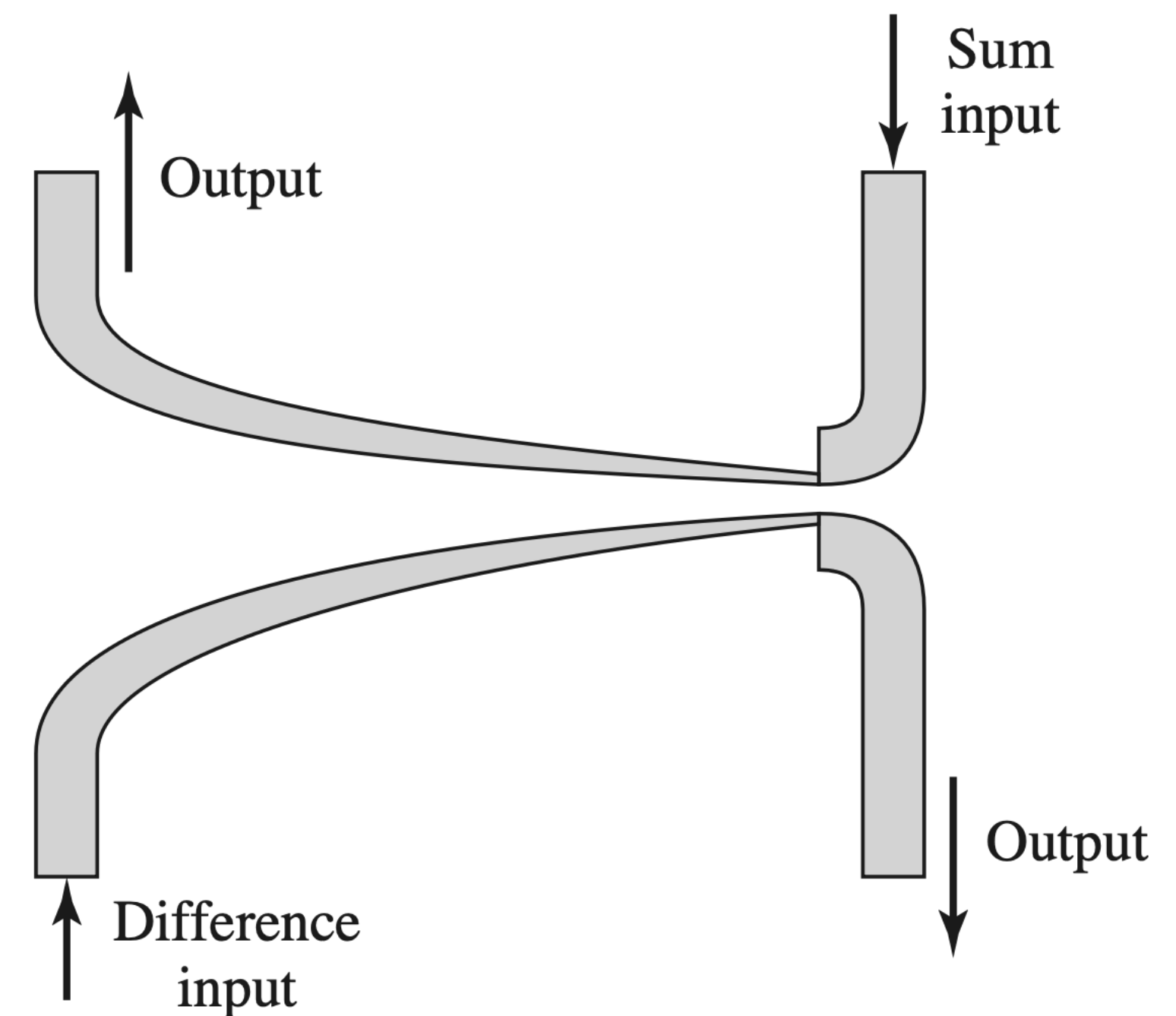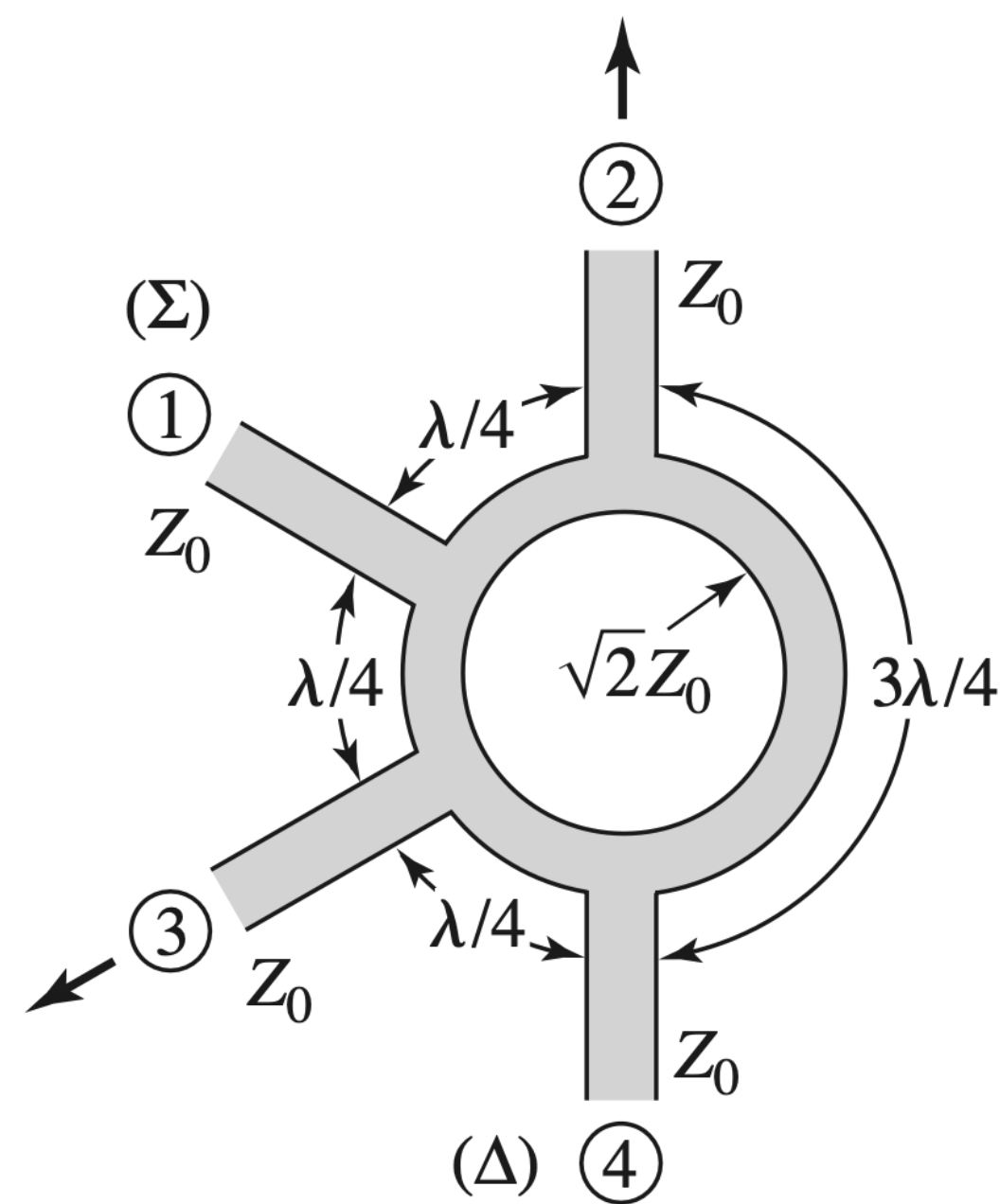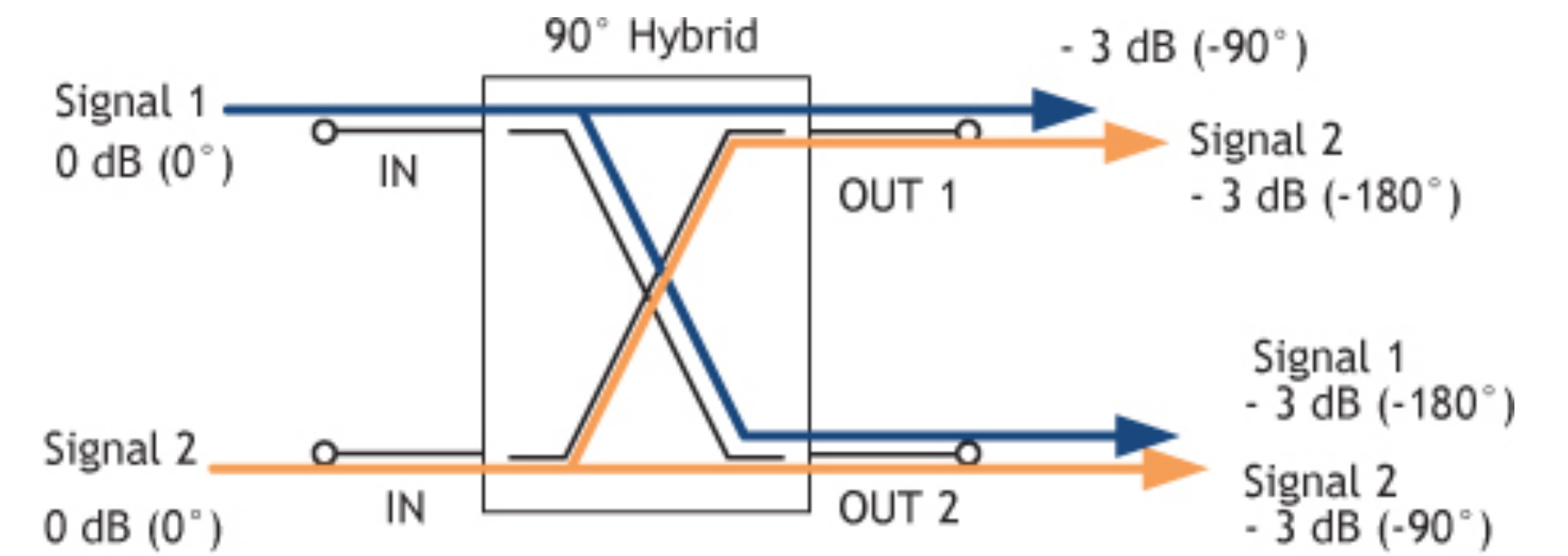

Antenna designs





EM waves
come
from
accelerating
charges
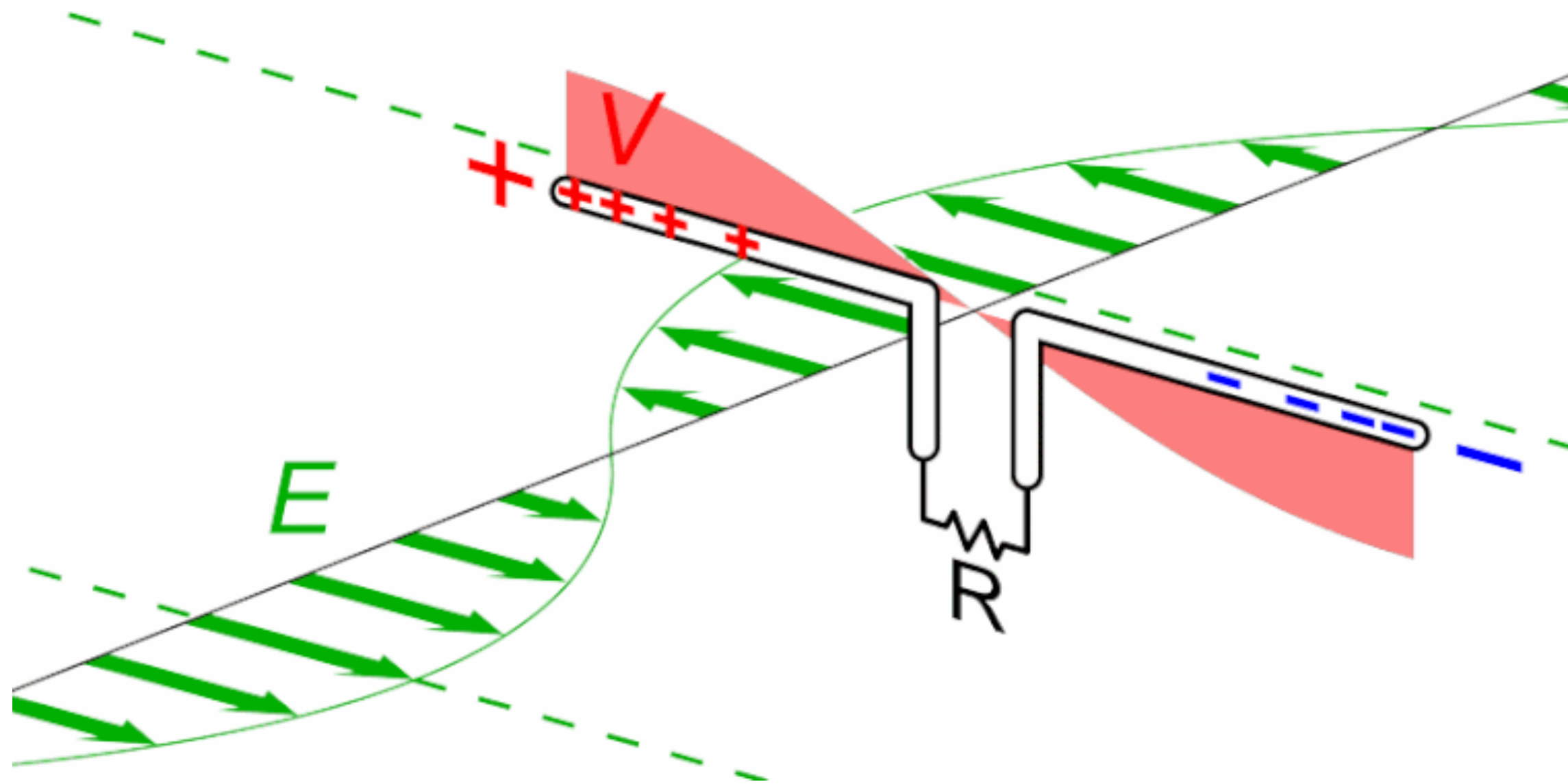
$$P = \frac{2}{3} \frac{q^2}{4\pi\epsilon_0 c} \left(\frac{\dot{v}}{c} \right)^2$$




$$R_{\text{radiation}} = \frac{\pi}{6} \zeta_0 \left(\frac{\ell}{\lambda} \right)^2 \approx \left(\frac{\ell}{\lambda} \right)^2 (197 \, \Omega)$$

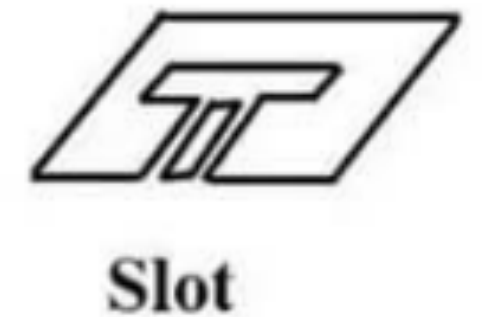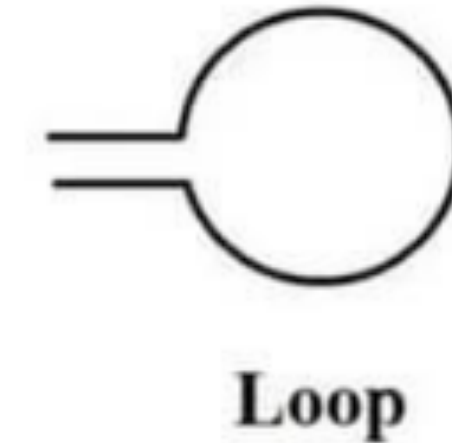
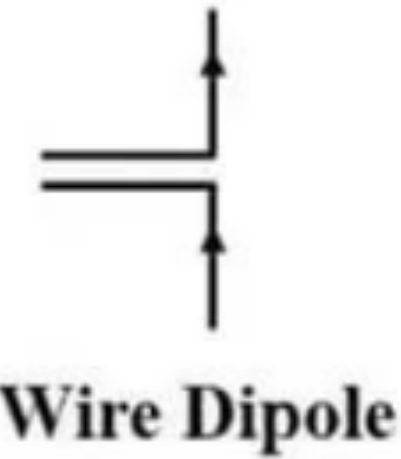
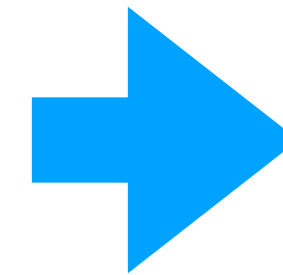
$\swarrow$
 $\sqrt{\mu_0/\epsilon_0} \approx 377 \, \Omega$




Semiconductor electronics

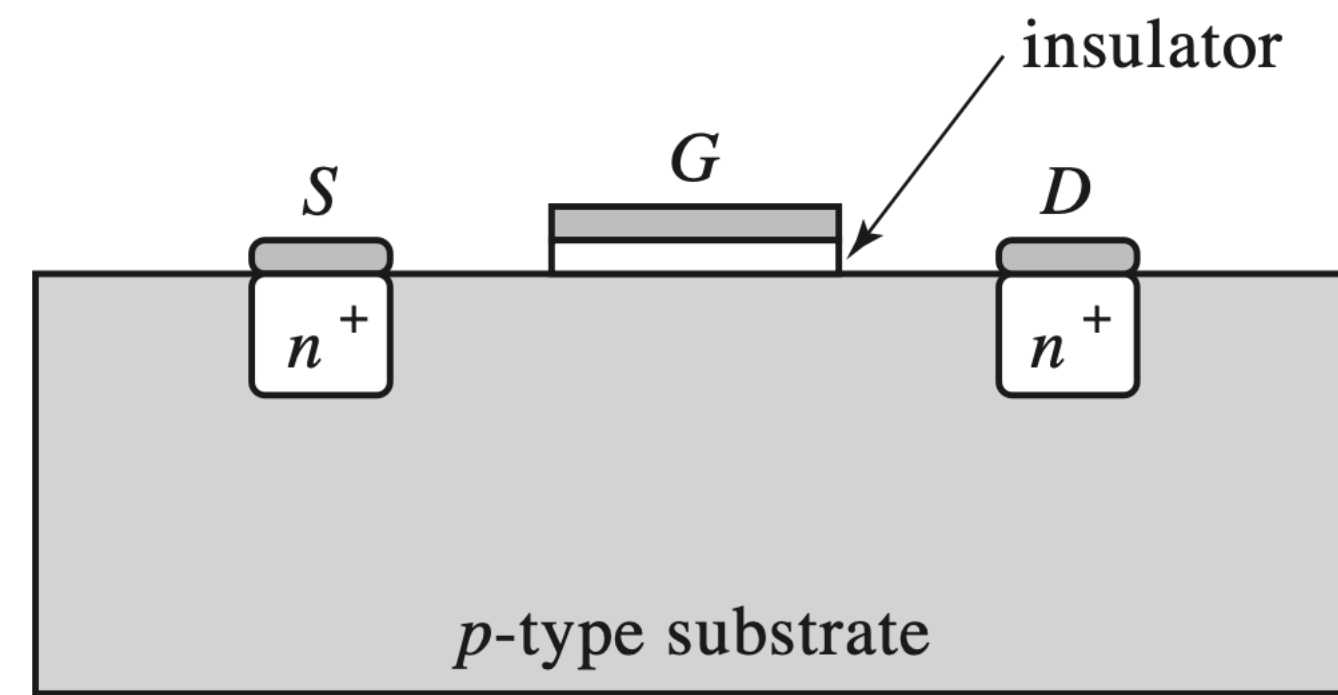






Cross section of an n -channel MOSFET.

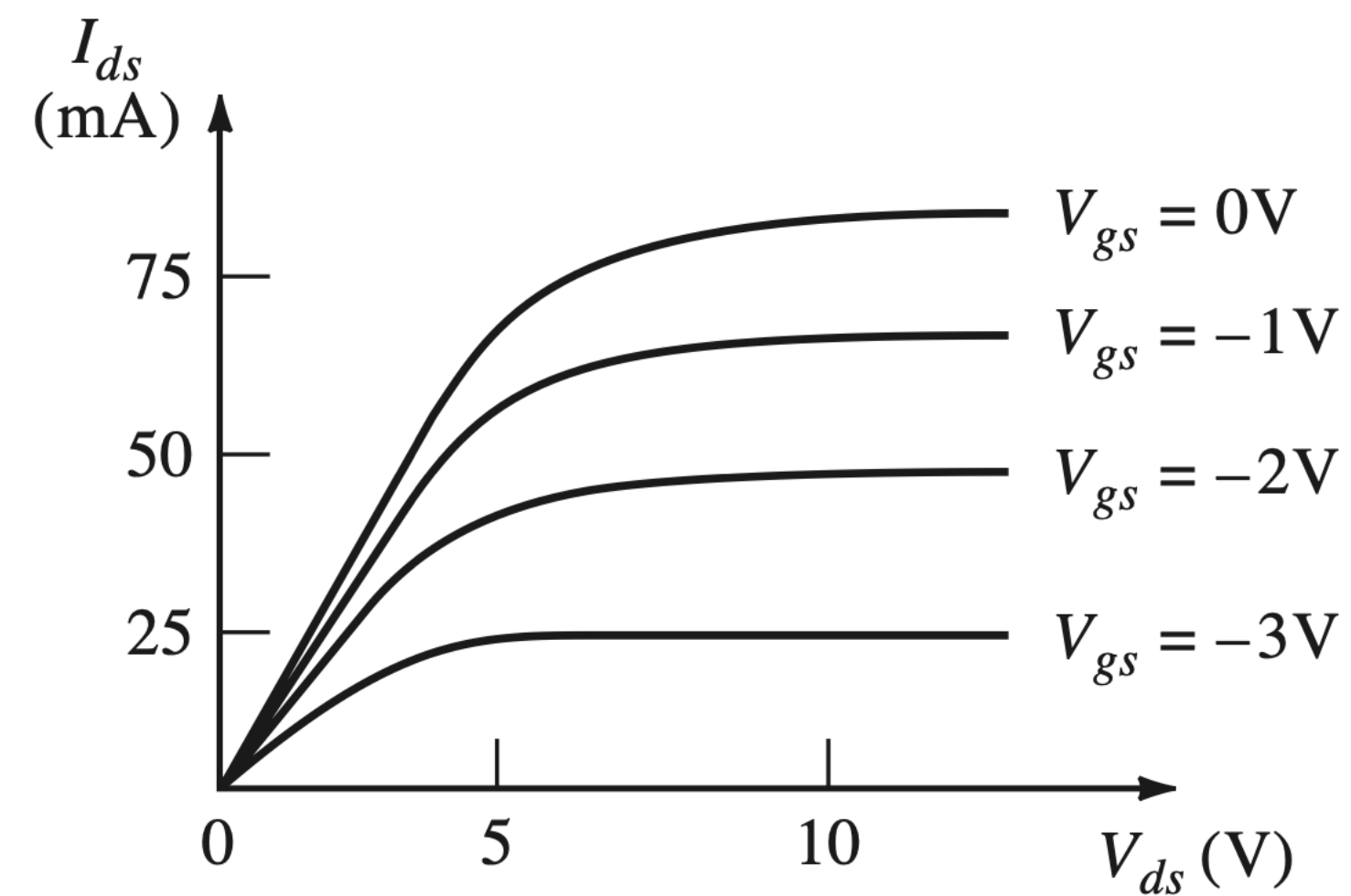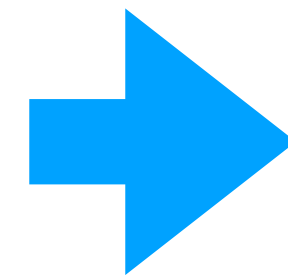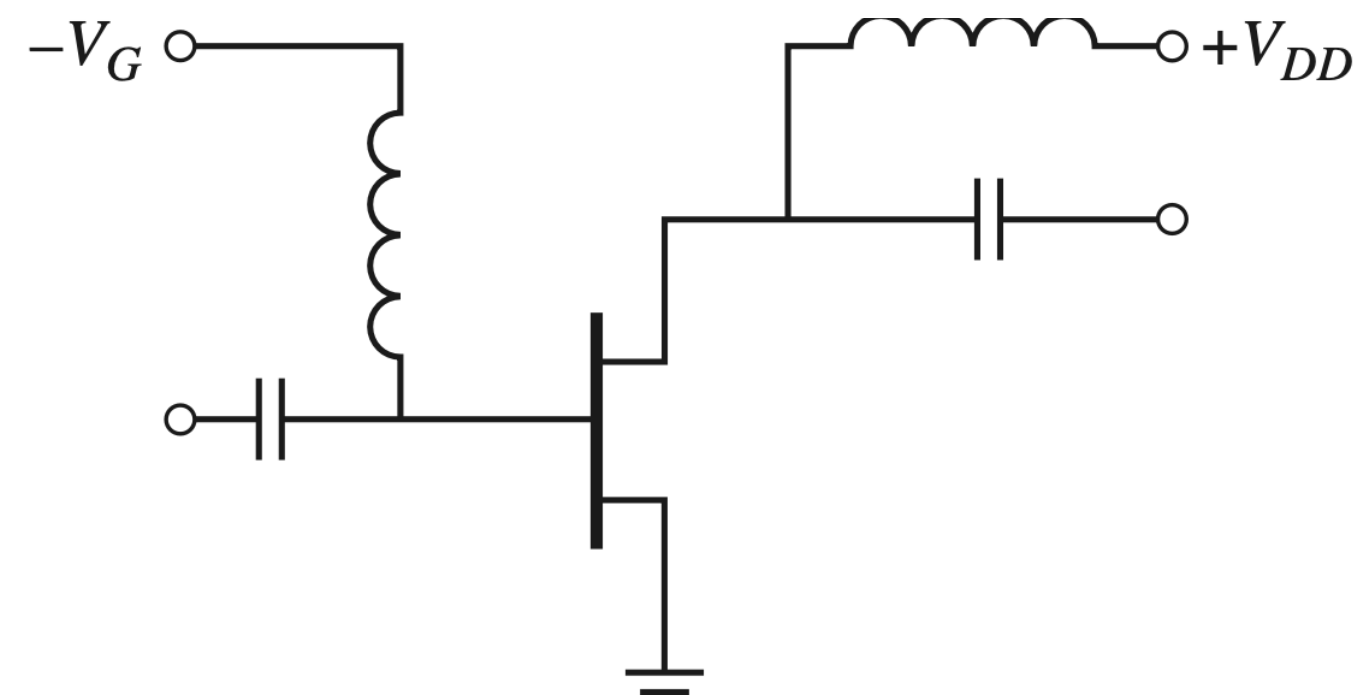


Microwave IC

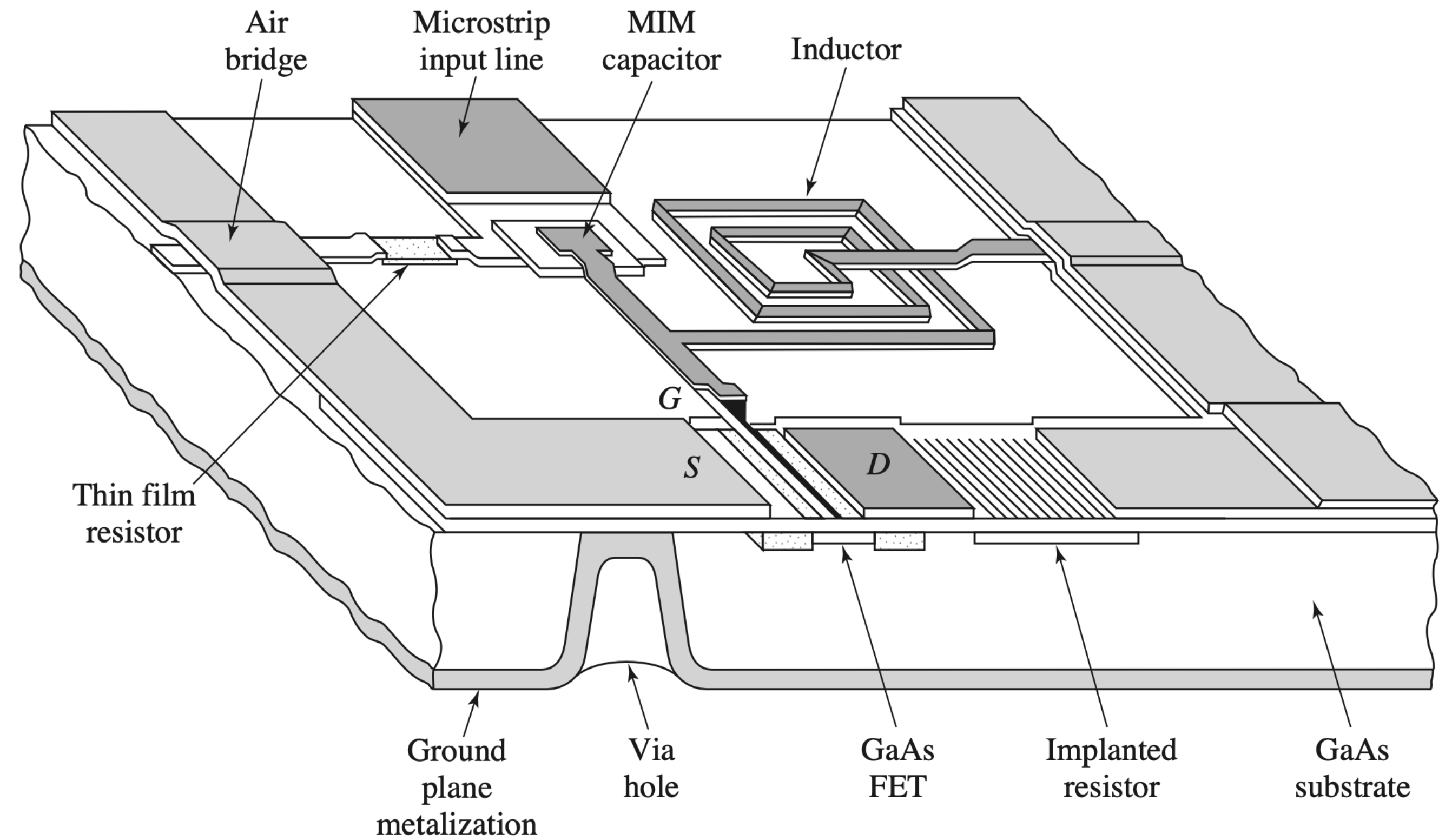

Filter design

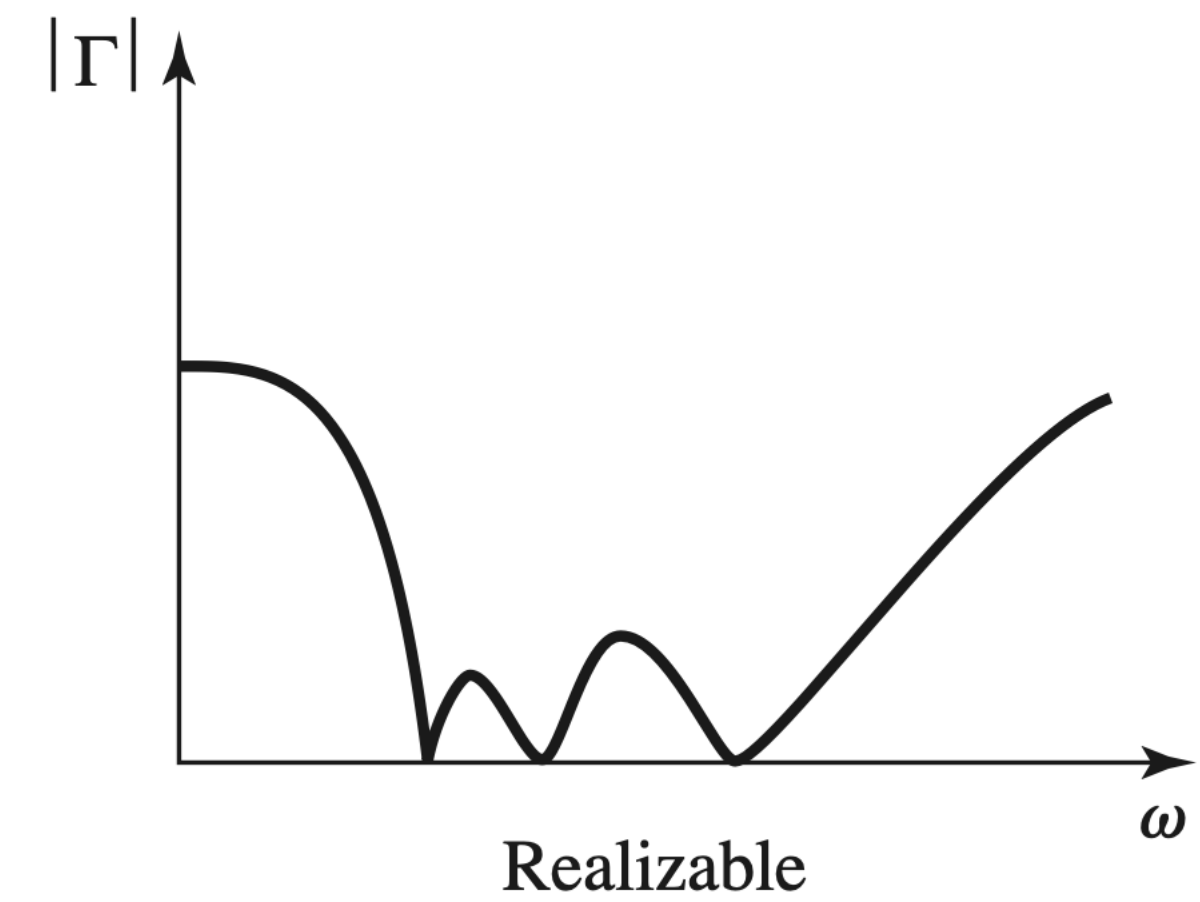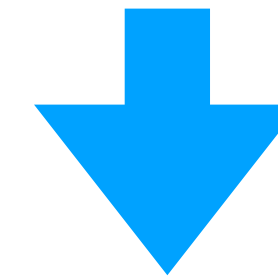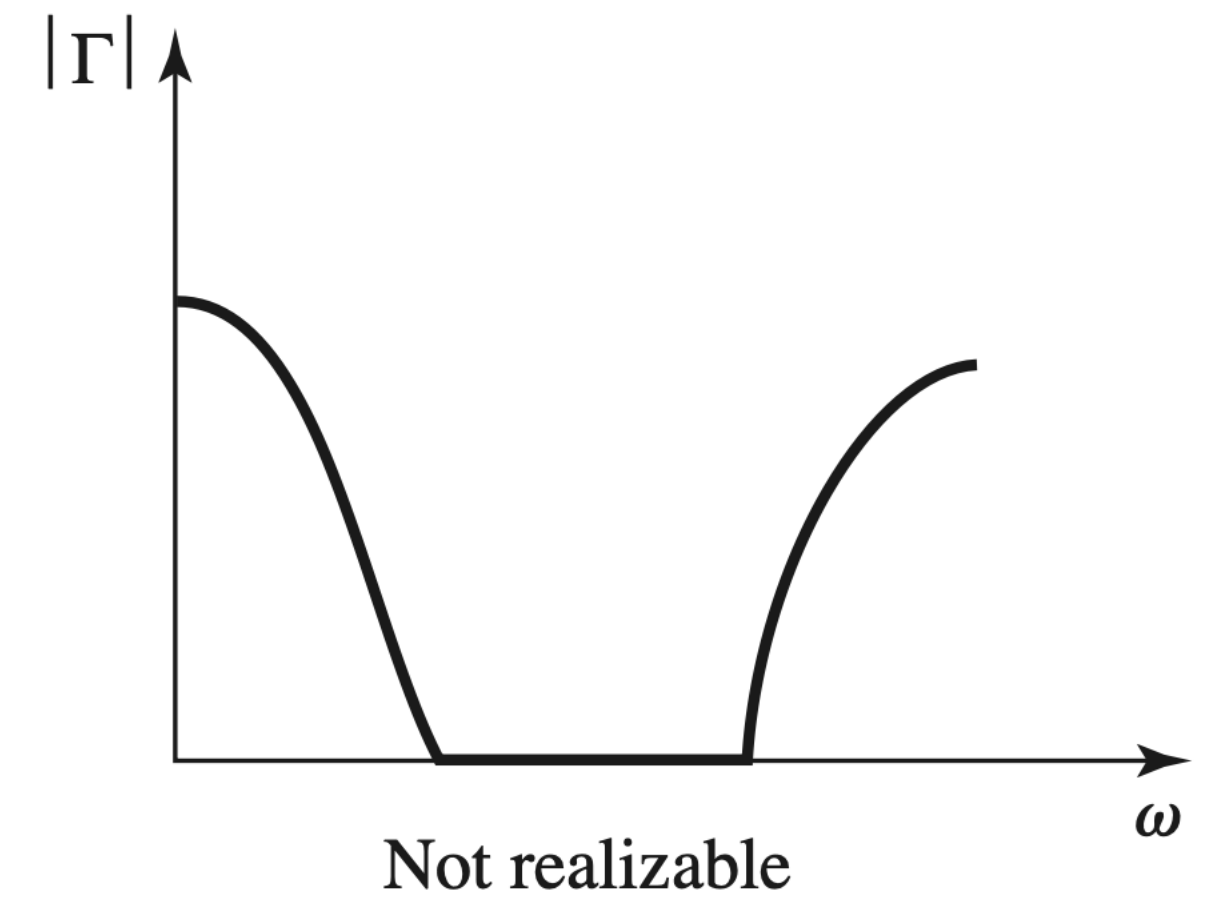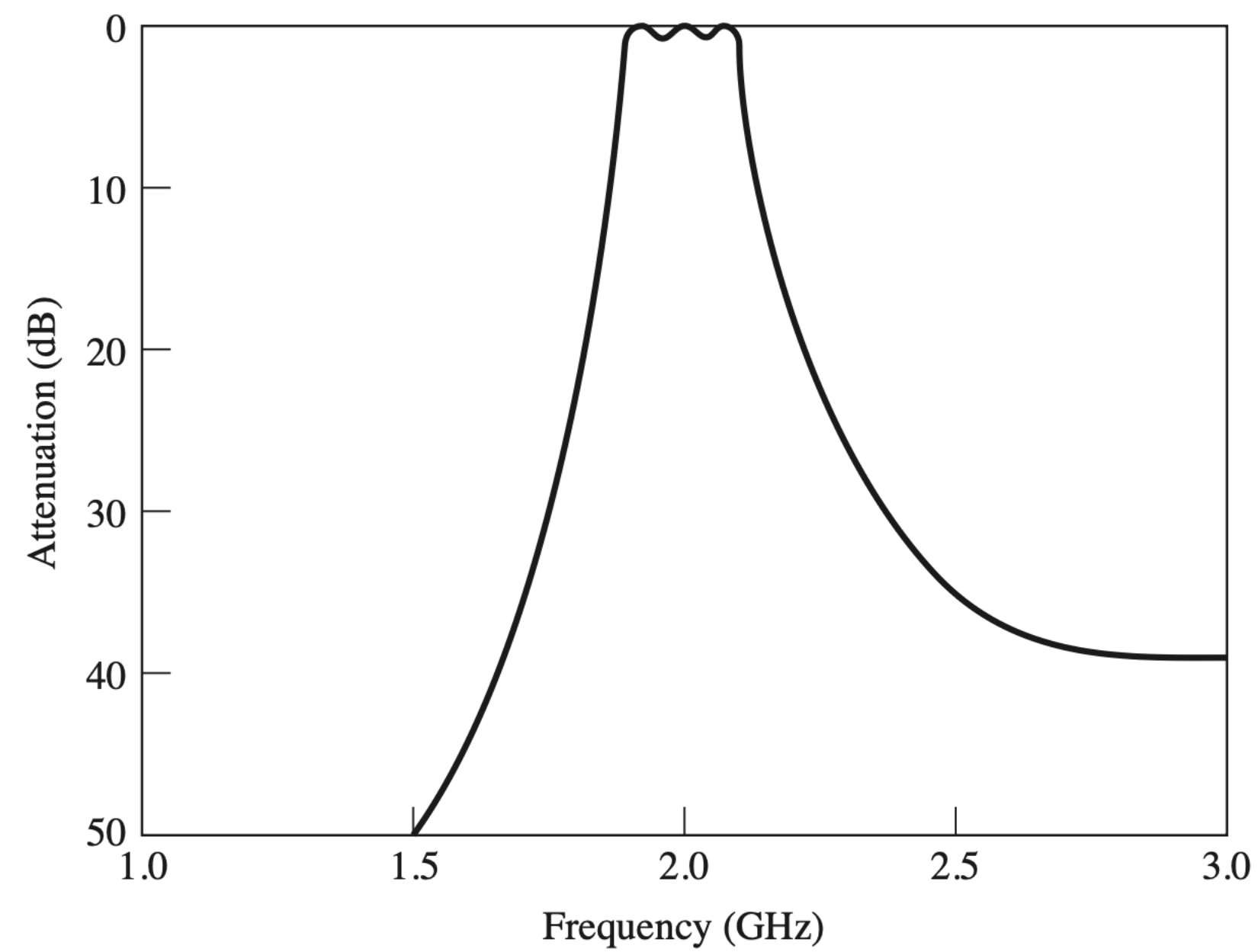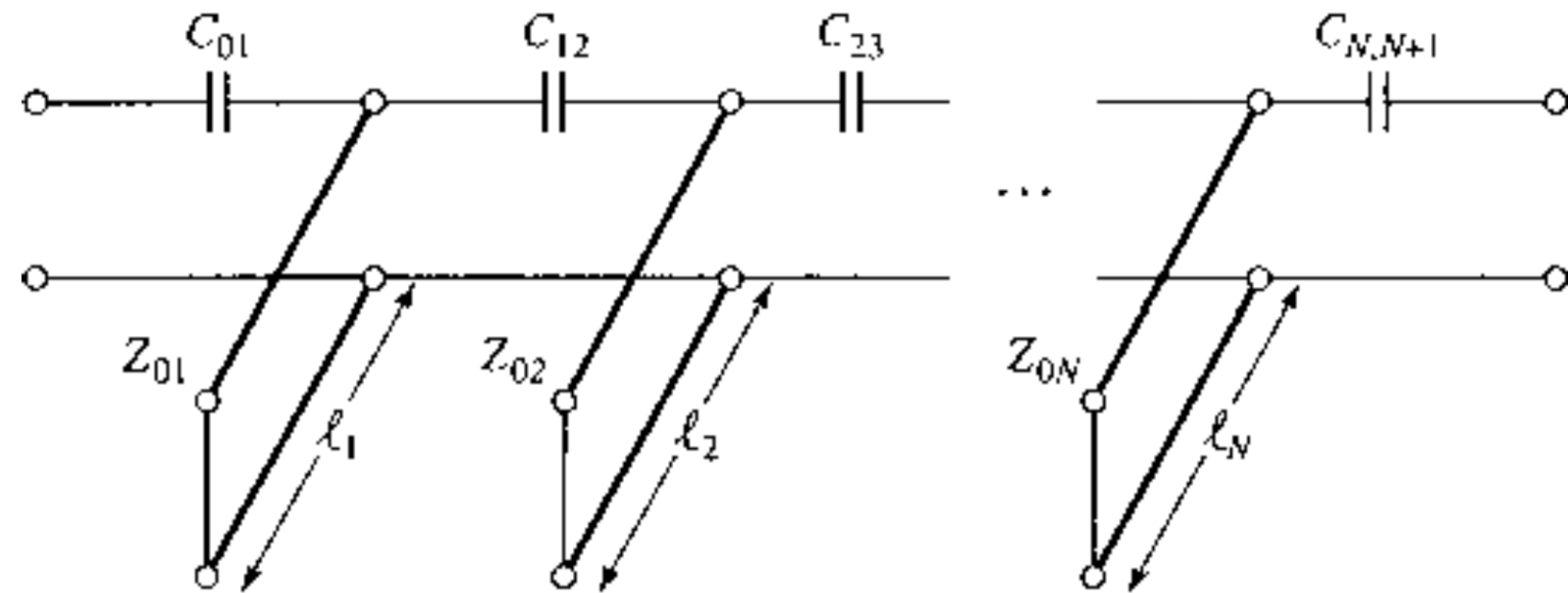

Qubit measurements

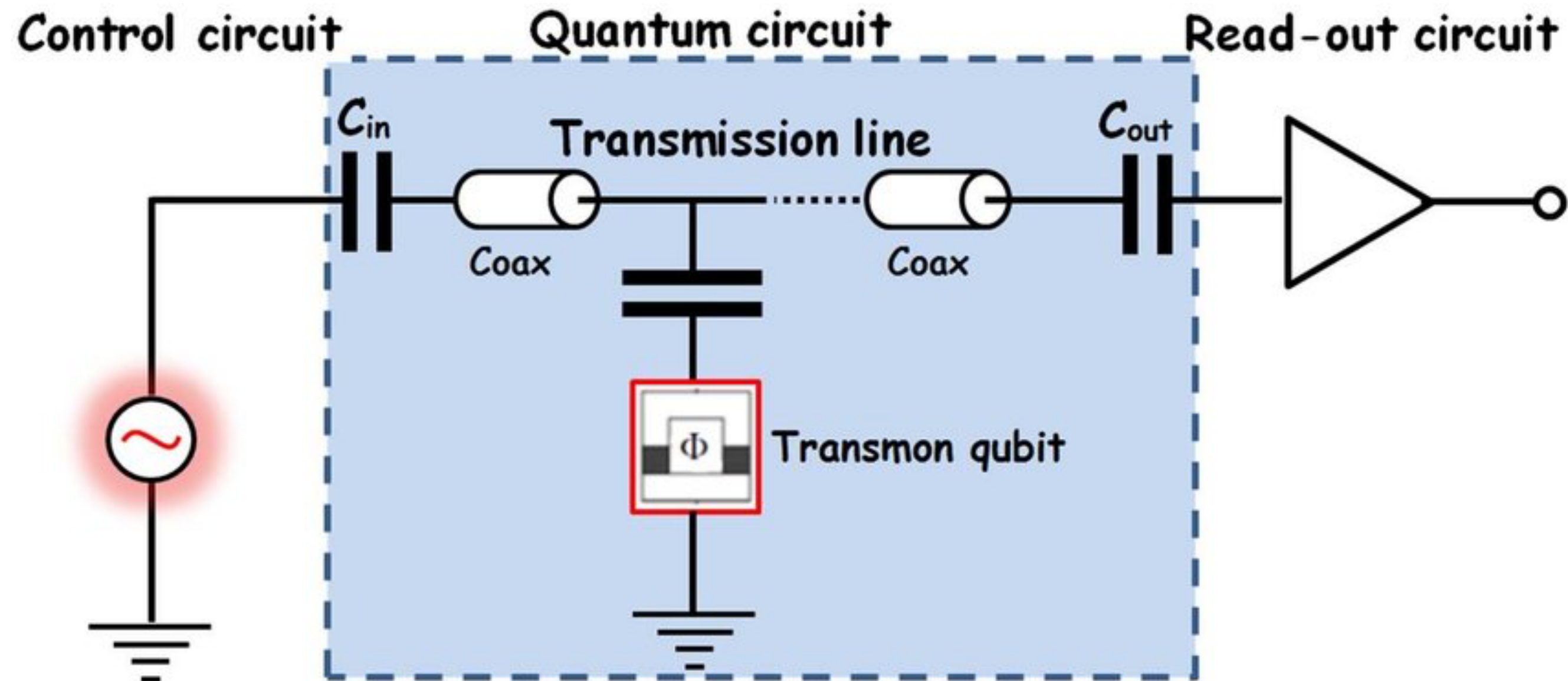

Come do a project in our labs!
(Brantut, Scarlino, Kippenberg, VM, ...)

From cavity QED to circuit QED

